

```
for (i=0 ; i<lnumverts ; i++)
```

# Let Run your Neurons

```
{
    if (lindex > 0)
```

```
    {
        r_pedge = &pedges[lindex]
```

```
        vec = r_pcurrentverthase[r_pedge->r[0]] position
```

```
    }
```

```
else
```

```
{
```

```
    r_pedge = &pedges[-lindex]
```

```
    vec = r_pcurrentverthase[r_pedge->r[1]] position
```

```
}
```

```
s = DotProduct (vec, fa->texinfo->vecs[0]) + fa->texinfo->vecs[0][3]
```

```
s /= fa->texinfo->texture->width
```

```
t = DotProduct (vec, fa->texinfo->vecs[1]) + fa->texinfo->vecs[1][3]
```

```
t /= fa->texinfo->texture->height
```

```
VectorCopy (vec, poly->verts[1])
```

```
poly->verts[1][3] = s
```

```
poly->verts[1][4] = t
```


team  
**LRN**

and use the coordinates

TEAM LRN

```
s = DotProduct (vec, fa->texinfo->vecs[0]) + fa->texinfo->vecs[0][3]
```

```
s -= fa->texturemins[0]
```

 

**EMBEDDED TECHNOLOGY™**  
**SERIES**

# Analog and Digital Circuits for Electronic Control System Applications

## Using the TI MSP430 Microcontroller



**CD-ROM Included Contains**  
source code and software tools

## Jerry Luecke

TEAM LRN



# ***Analog and Digital Circuits for Electronic Control System Applications***

*This page intentionally left blank*

# ***Analog and Digital Circuits for Electronic Control System Applications***

*Using the TI MSP430 Microcontroller*

by  
*Jerry Luecke*



ELSEVIER

AMSTERDAM • BOSTON • HEIDELBERG • LONDON  
NEW YORK • OXFORD • PARIS • SAN DIEGO  
SAN FRANCISCO • SINGAPORE • SYDNEY • TOKYO

Newnes is an imprint of Elsevier

TEAM LRN



Newnes

Newnes is an imprint of Elsevier  
200 Wheeler Road, Burlington, MA 01803, USA  
Linacre House, Jordan Hill, Oxford OX2 8DP, UK

Copyright © 2005, Elsevier Inc. All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.

Permissions may be sought directly from Elsevier's Science & Technology Rights Department in Oxford, UK: phone: (+44) 1865 843830, fax: (+44) 1865 853333, e-mail: [permissions@elsevier.com.uk](mailto:permissions@elsevier.com.uk). You may also complete your request on-line via the Elsevier homepage (<http://elsevier.com>), by selecting "Customer Support" and then "Obtaining Permissions."



Recognizing the importance of preserving what has been written, Elsevier prints its books on acid-free paper whenever possible.

#### **Library of Congress Cataloging-in-Publication Data**

Luecke, Gerald.

Analog and digital circuits for electronic control system applications : using the TI MSP430 microcontroller / by Gerald Luecke.

p. cm.

ISBN 0-7506-7810-0

1. Electronic circuit design. 2. Electronic control. 3. Programmable controllers. I. Title.

TK7867.L84 2004

629.8'9--dc22

2004054669

#### **British Library Cataloguing-in-Publication Data**

A catalogue record for this book is available from the British Library.

For information on all Newnes publications  
visit our Web site at [www.books.elsevier.com](http://www.books.elsevier.com)

04 05 06 07 08 09 10 9 8 7 6 5 4 3 2 1

Printed in the United States of America.

*The book is dedicated to my wife Velma and our grandchildren:*

*From the Luecke side:*

*Cameron, Graham, Andy, Alex, Alyssa,  
Brent, Jacob, Harper, Arielle, Emery.*

*From the Hubbard side:*

*Jared, Garrett, Matthew, Ashton, Audrey.*

*This page intentionally left blank*



# Contents

|                                                            |                    |
|------------------------------------------------------------|--------------------|
| <b>Foreword .....</b>                                      | <b><i>xi</i></b>   |
| <b>Preface .....</b>                                       | <b><i>xii</i></b>  |
| <b>Acknowledgments .....</b>                               | <b><i>xiii</i></b> |
| <b>What's on the CD-ROM? .....</b>                         | <b><i>xiv</i></b>  |
| <b>Chapter 1: Signal Paths from Analog to Digital.....</b> | <b>1</b>           |
| Introduction .....                                         | 1                  |
| A Refresher .....                                          | 1                  |
| Accuracy vs. Speed—Analog and Digital .....                | 5                  |
| Interface Electronics .....                                | 6                  |
| The Basic Functions for Analog-to-Digital Conversion ..... | 6                  |
| Summary .....                                              | 8                  |
| Chapter 1 Quiz .....                                       | 9                  |
| <b>Chapter 2: Signal Paths from Digital to Analog.....</b> | <b>11</b>          |
| Introduction .....                                         | 11                 |
| The Digital-to-Analog Portion .....                        | 11                 |
| Filtering .....                                            | 13                 |
| Conditioning the Signal .....                              | 13                 |
| Transducing the Signal .....                               | 13                 |
| Summary .....                                              | 15                 |
| Chapter 2 Quiz .....                                       | 16                 |
| <b>Chapter 3: Sensors .....</b>                            | <b>18</b>          |
| Introduction .....                                         | 18                 |
| Temperature Sensors .....                                  | 18                 |
| Angular and Linear Position .....                          | 21                 |
| Rotation .....                                             | 24                 |
| Magnetoresistor Sensor .....                               | 24                 |
| Pressure .....                                             | 25                 |
| Light Sensors .....                                        | 27                 |
| Other Sensors .....                                        | 32                 |
| Summary .....                                              | 32                 |
| Chapter 3 Quiz .....                                       | 32                 |
| <b>Chapter 4: Signal Conditioning.....</b>                 | <b>35</b>          |
| Introduction .....                                         | 35                 |
| Amplification .....                                        | 35                 |
| Bipolar NPN Amplifier .....                                | 36                 |
| Amplifier Frequency Response .....                         | 39                 |
| Coupling .....                                             | 40                 |
| Small-Signal vs. Large Signal .....                        | 41                 |
| Classes of Amplifiers .....                                | 42                 |
| Field-Effect Transistor Amplifiers .....                   | 42                 |
| A N-Channel JFET Amplifier Design .....                    | 43                 |
| An NPN MOSFET Amplifier .....                              | 45                 |

|                                                                             |            |
|-----------------------------------------------------------------------------|------------|
| Operational Amplifiers.....                                                 | 47         |
| Conditioning the Output of a Pressure Sensor.....                           | 50         |
| A More Sophisticated Pressure Sensor Amplifier.....                         | 51         |
| Current Mirror.....                                                         | 52         |
| Applications of Op Amps.....                                                | 53         |
| Oscillators .....                                                           | 53         |
| Power Amplifiers .....                                                      | 54         |
| Class B Audio Power Amplifier .....                                         | 56         |
| Special Signals .....                                                       | 56         |
| RC Time Constants .....                                                     | 58         |
| Frequency Selection.....                                                    | 59         |
| Typical Application of Filters .....                                        | 61         |
| Summary .....                                                               | 62         |
| Chapter 4 Quiz .....                                                        | 62         |
| <b>Chapter 5: Analog-to-Digital and Digital-to-Analog Conversions .....</b> | <b>66</b>  |
| Introduction.....                                                           | 66         |
| Decimal Equivalent of a Binary Number.....                                  | 67         |
| Digital Codes of ADC.....                                                   | 67         |
| A Resistor Network DAC .....                                                | 68         |
| A Simple Resistor-String DAC .....                                          | 71         |
| A Simple Current-Steering DAC .....                                         | 72         |
| Analog-to-Digital Converters (ADC) .....                                    | 73         |
| Successive Approximation Register (SAR) ADC.....                            | 74         |
| Capacitor Charge-Redistribution ADC .....                                   | 75         |
| Highest Speed Conversions.....                                              | 78         |
| Sample and Hold and Filters.....                                            | 78         |
| Summary .....                                                               | 79         |
| Chapter 5 Quiz .....                                                        | 80         |
| <b>Chapter 6: Digital System Processing.....</b>                            | <b>82</b>  |
| Introduction.....                                                           | 82         |
| Digital Processor or Digital Computer .....                                 | 82         |
| What is a Microprocessor?.....                                              | 86         |
| What is a Microcomputer?.....                                               | 86         |
| System Clarifications .....                                                 | 86         |
| Digital Signal Representations.....                                         | 90         |
| Clock, Timing and Control Signals.....                                      | 90         |
| Interrupts .....                                                            | 92         |
| Status Bits .....                                                           | 92         |
| More About Software.....                                                    | 93         |
| Sophisticated Programming Languages.....                                    | 95         |
| How Parts of a Processor Perform Their Functions.....                       | 95         |
| Memory and Input/Output .....                                               | 97         |
| Addressing Modes .....                                                      | 97         |
| Summary .....                                                               | 99         |
| Chapter 6 Quiz .....                                                        | 100        |
| <b>Chapter 7: Examples of Assembly-Language Programming .....</b>           | <b>103</b> |
| Introduction.....                                                           | 103        |
| A Processor for the Examples.....                                           | 103        |
| About the MSP430 Family .....                                               | 103        |
| The CPU.....                                                                | 104        |

|                                                 |            |
|-------------------------------------------------|------------|
| Program Memory and Data Memory .....            | 105        |
| Peripherals.....                                | 106        |
| Operation Control and Operating Modes.....      | 106        |
| Watchdog Timer .....                            | 106        |
| System Reset .....                              | 107        |
| Interrupts .....                                | 107        |
| Oscillators and Clock Generators .....          | 107        |
| Timers .....                                    | 109        |
| Addressing Modes .....                          | 109        |
| More on MSP430 Control.....                     | 110        |
| Further Thoughts.....                           | 114        |
| Labels .....                                    | 117        |
| Instructions.....                               | 117        |
| Operands .....                                  | 117        |
| Hexadecimal Numbers.....                        | 117        |
| Comments .....                                  | 118        |
| Programming Examples.....                       | 118        |
| Subprogram No. 1 .....                          | 118        |
| Subprogram No. 2 .....                          | 127        |
| Subprogram No. 3 .....                          | 131        |
| Variation of Threshold .....                    | 137        |
| Summary .....                                   | 137        |
| Chapter 7 Quiz .....                            | 138        |
| <b>Chapter 8: Data Communications.....</b>      | <b>142</b> |
| Introduction.....                               | 142        |
| The Data Transmission System.....               | 142        |
| Parallel and Serial Transmission .....          | 142        |
| Protocols .....                                 | 144        |
| High-Speed Data Transmissions .....             | 145        |
| Serial Data Communications Advances.....        | 145        |
| A Return to the Format .....                    | 145        |
| Shift Registers.....                            | 147        |
| USART Serial Communications .....               | 148        |
| The UART Function with Software.....            | 150        |
| Technology Advances .....                       | 150        |
| I <sup>2</sup> C Protocol.....                  | 150        |
| USB.....                                        | 152        |
| Summary .....                                   | 156        |
| Chapter 8 Quiz .....                            | 157        |
| <b>Chapter 9: System Power and Control.....</b> | <b>160</b> |
| Introduction.....                               | 160        |
| Voltage Regulators .....                        | 161        |
| Load Variations .....                           | 162        |
| Actual Linear Voltage Regulator Circuit.....    | 163        |
| Voltage Regulation.....                         | 163        |
| Power Dissipation .....                         | 164        |
| Switching Voltage Regulators .....              | 165        |
| Summary of Regulators .....                     | 167        |
| Power Supply Distribution.....                  | 168        |
| Power System Supervisors.....                   | 170        |

## Contents

---

|                                                                                                |            |
|------------------------------------------------------------------------------------------------|------------|
| Summary .....                                                                                  | 171        |
| Chapter 9 Quiz .....                                                                           | 171        |
| <b>Chapter 10: A Microcontroller Application .....</b>                                         | <b>174</b> |
| Introduction .....                                                                             | 174        |
| Application Block Diagram .....                                                                | 174        |
| System Schematic .....                                                                         | 177        |
| The Display .....                                                                              | 177        |
| The Microcontroller .....                                                                      | 179        |
| The Analog Circuitry .....                                                                     | 180        |
| JTAG .....                                                                                     | 181        |
| Summary of Schematic .....                                                                     | 182        |
| System Development .....                                                                       | 182        |
| Breadboard Construction—Powered by the PC .....                                                | 185        |
| The Display Board .....                                                                        | 189        |
| The Analog Board .....                                                                         | 190        |
| The Application Program .....                                                                  | 191        |
| Creating a Project in IAR Workbench© .....                                                     | 192        |
| Compiling the Program .....                                                                    | 193        |
| Loading the Program .....                                                                      | 194        |
| Troubleshooting .....                                                                          | 194        |
| The Stand-Alone Breadboard .....                                                               | 194        |
| The PCB Circuit .....                                                                          | 195        |
| Summary .....                                                                                  | 197        |
| Chapter 10 Quiz .....                                                                          | 197        |
| <b>Appendix A: The MSP430 Instruction Set .....</b>                                            | <b>200</b> |
| <b>Appendix B: Standard Register and Bit Definitions for the MSP430 Microcontrollers .....</b> | <b>260</b> |
| <b>Appendix C: Application Program for Use in Chapter 10 .....</b>                             | <b>273</b> |
| <b>Appendix D: A Refresher .....</b>                                                           | <b>290</b> |
| Ohm's Law .....                                                                                | 290        |
| Decibel—A Quantity to Describe Gain .....                                                      | 291        |
| Passive Devices .....                                                                          | 292        |
| The Diode—A One-Way Valve for Current .....                                                    | 294        |
| Active Devices .....                                                                           | 294        |
| Four Common Types .....                                                                        | 297        |
| <b>About the Author .....</b>                                                                  | <b>299</b> |
| <b>Index .....</b>                                                                             | <b>300</b> |

# Foreword

February 2004

The concept of a programmable system-on-chip (SoC) started in 1972 with the advent of the unassuming 4-bit TMS1000 microcomputer—the perfect fit for applications such as calculators and microwave ovens that required a device with everything needed to embed electronic intelligence. Microcomputers changed the way engineers approached equipment design; for the first time they could reuse proven electronics hardware, needing only to create software specific to the application. The result of microcomputer-based designs has been a reduction in both system cost and time-to-market.

More than thirty years later many things have changed, but many things remain the same. The term microcomputer has been replaced with microcontroller unit (MCU)—a name more descriptive of a typical application. Today's MCU, just like yesterday's microcomputer, remains the heart and soul of many systems. But over time the MCU has placed more emphasis on providing a higher level of integration and control processing and less on sheer computing power. The race for embedded computing power has been won by the dedicated digital signal processor (DSP), a widely used invention of the '80s that now dominates high-volume, computing-intensive embedded applications such as the cellular telephone. But the design engineer's most used tool, when it comes to implementing cost effective system integration, remains the MCU. The MCU allows just the right amount of intelligent control for a wide variety of applications.

Today there are hundreds of MCUs readily available, from low-end 4-bit devices like those found in a simple wristwatch, to high-end 64-bit devices. But the workhorses of the industry are still the versatile 8/16-bit architectures. Choices are available with 8 to 100+ pins and program memory ranging from <1 KB to >64 KB. The MCU's adoption of mixed-signal peripherals is an area that has greatly expanded, recently enabling many new SoC solutions. It is common today to find MCUs with 12-bit analog-to-digital and digital-to-analog converters combined with amplifiers and power management, all on the same chip in the same device. This class of device offers a complete signal-chain on a chip for applications ranging from energy meters to personal medical devices.

Modern MCUs combine mixed-signal integration with instantly programmable Flash memory and embedded emulation. In the hands of a savvy engineer, a unique MCU solution can be developed in just days or weeks compared to what used to take months or years. You can find MCUs everywhere you look from the watch on your wrist to the cooking appliances in your home to the car you drive. An estimated 20 million MCUs ship every day, with growth forecast for at least a decade to come. The march of increasing silicon integration will continue offering an even greater variety of available solutions—but it is the engineer's creativity that will continue to set apart particular system solutions.

Mark E. Buccini  
Director of Marketing  
MSP430  
Texas Instruments Incorporated

# Preface

Analog system designers many times in the past avoided the use of electronics for their system functions because electronic circuits could not provide the dynamic range of the signal without severe nonlinearity, or because the circuits drifted or became unstable with temperature, or because the computations using analog signals were quite inaccurate. As a result, the design shifted to other disciplines, for example, mechanical.

Today, young engineers requested by their superiors to design an analog control system, have an entirely new technique available to them to help them design the system and overcome the “old” problems. The design technique is this: sense the analog signals and convert them to electrical signals; condition the signals so they are in a range of inputs to assure accurate processing; convert the analog signals to digital; make the necessary computations using the very high-speed IC digital processors available with their high accuracy; convert the digital signals back to analog signals; and output the analog signals to perform the task at hand.

*Analog and Digital Circuits for Control System Applications: Using the TI MSP430 Microcontroller* explains the functions that are in the signal chain, and explains how to design electronic circuits to perform the functions. Included in this book is a chapter on the different types of sensors and their outputs. There is a chapter on the different techniques of conditioning the sensor signals, especially amplifiers and op amps. There are techniques and circuits for analog-to-digital and digital-to-analog conversions, and an explanation of what a digital processor is and how it works. There is a chapter on data transmissions and one on power control.

And to solidify the learning and applications, there is a chapter that explains assembly-language programming, and also a chapter where the reader actually builds a working project. These two chapters required choosing a digital processor. The TI MSP430 microcontroller was chosen because of its design, and because it is readily available, it is well supported with design and applications documentation, and it has relatively inexpensive evaluation tools.

The goal of the book is to provide understanding and learning of the new design technique available to analog system designers and the tools available to provide system solutions.

# *Acknowledgments*

Mark Buccini, Product Line Marketing Manager for the MSP430 in the Semiconductor Group for Texas Instruments Incorporated and his staff deserve much credit for the project in Chapter 10, and for the thoroughness and accuracy of the MSP430 information. Special thanks go to Neal Frager, an applications expert, for writing the program for the Chapter 10 project, for designing the PCB breadboard, arranging meetings and for researching many inquiries as the book developed. Others that deserve mention for their assistance: Cornelia Huellstrunk, Byron Alsberg who helped develop the initial schematic, Dale Wellborn, Dan Harmon, Rajen Shah, Zack Albus, Modupe Ajibola, Mike Mitchell for his excellent reviews, and Neal Brenner and for helping clean up the last details. A hearty “Thank You” to all!

# ***What's on the CD-ROM?***

- A fully searchable eBook version of the text in Adobe PDF format. It includes:
  - Full text of ten chapters.
  - Appendix A — The MSP430 Instruction Set.
  - Appendix B — Standard Register and Bit Definitions for the MSP430 Microcontrollers.
  - Appendix C — Application Program for Use in Chapter 10.
  - Appendix D — A Refresher.
- A user's guide to the MSP430x1xx family of microcontrollers.
- Layout wiring of PCB interconnection layers.



# Signal Paths from Analog to Digital

## Introduction

Designers of analog electronic control systems have continually faced the following obstacles in arriving at a satisfactory design:

1. Instability and drift due to temperature variations.
2. Dynamic range of signals and nonlinearity when pressing the limits of the range.
3. Inaccuracies of computation when using analog quantities.
4. Adequate signal frequency range.

Today's designers, however, have a significant alternative offered to them by the advances in integrated circuit technology, especially low-power analog and digital circuits. The alternative new design technique for analog systems is to sense the analog signal, convert it to digital signals, use the speed and accuracy of digital circuits to do the computations, and convert the resultant digital output back to analog signals.


The new design technique requires that the electronic system designer interface between two distinct design worlds. First, between analog and digital systems, and second, between the external human world and the internal electronics world. Various functions are required to make the interface. First, from the human world to the electronics world and back again and, in a similar fashion, from the analog systems to digital systems and back again. *Analog and Digital Circuits for Control System Applications* identifies the electronic functions needed, and describes how electronic circuits are designed and applied to implement the functions, and gives examples of the use of the functions in systems.

## A Refresher


Since the book deals with the electronic functions and circuits that interface or couple analog-to-digital circuits and systems, or vice versa, a short review is provided so it is clearly understood what analog means and what digital means.
 
## Analog

Analog quantities vary continuously, and analog systems represent the analog information using electrical signals that vary smoothly and continuously over a range. A good example of an analog system is the recording thermometer shown in *Figure 1-1*. The actual equipment is shown in *Figure 1-1a*. An ink pen records the



 a. Recording thermometer  
Photo courtesy of Taylor Precision Products



b. Plot of daily temperature variations  
Courtesy of Master Publishing, Inc.

Figure 1-1: A recording thermometer is an example of an analog system  
TEAM LRN

temperature in degrees Fahrenheit ( $^{\circ}\text{F}$ ) and plots it continuously against time on a special graph paper attached to a drum as the drum rotates. The record of the temperature changes is shown in *Figure 1-1b*. Note that the temperature changes smoothly and continuously. There are no abrupt steps or breaks in the data.


Another example is the automobile fuel gauge system shown in *Figure 1-2*. The electrical circuit consists of a potentiometer, basically a resistor connected across a car battery from the positive terminal to the negative terminal, which is grounded. The resistor has a variable tap that is rotated by a float riding on the surface of the liquid inside the gas tank.

A voltmeter reads the voltage from the variable tap to the negative side of the battery (ground). The voltmeter indicates the information about the amount of fuel in the gas tank. It represents the fuel level in the tank. The greater the fuel level in the tank the greater the voltage reading on the voltmeter. The voltage is said to be an analog of the fuel level. An analog of the fuel level is said to be a copy of the fuel level in another form—it is *analogous* to the original fuel level. The voltage (fuel level) changes smoothly and continuously so the system is an analog system, but is also an analog system because the system output voltage is a copy of the actual output parameter (fuel level) in another form.


## Digital

Digital quantities vary in discrete levels. In most cases, the discrete levels are just two values—ON and OFF. Digital systems carry information using combinations of ON-OFF electrical signals that are usually in the form of codes that represent the information. The telegraph system is an example of a digital system.


The system shown in *Figure 1-3* is a simplified version of the original telegraph system, but it will demonstrate the principle and help to define a digital system. The electrical circuit (*Figure 1-3a*) is a battery with a switch in the line at one end and a light bulb at the other. The person

 


**Figure 1-2: The simple circuit for an automobile fuel gauge demonstrates how an electrical quantity, a voltage, is an analog of the fuel level. Courtesy of Master Publishing, Inc.**

 

**a. Electrical circuit**

 

**b. International Morse code**

 

**c. Digital information**

**Figure 1-3: The telegraph is a digital system that sends information as patterns of switched signals**

at the switch position is remotely located from the person at the light bulb. The information is transmitted from the person at the switch position to the person at the light bulb by coding the information to be sent using the International Morse telegraph code.

Morse code uses short pulses (dots) and long pulses (dashes) of current to form the code for letters or numbers as shown in *Figure 1-3b*. As shown in *Figure 1-3c*, combining the codes of dots and dashes for the letters and numbers into words sends the information. The sender keeps the same shorter time interval between letters but a longer time interval between words. This allows the receiver to identify that the code sent is a character in a word or the end of a word itself. The T is one dash (one long current pulse). The H is four short dots (four short current pulses). The R is a dot-dash-dot. And the two Es are a dot each. The two states are ON and OFF—current or no current. The person at the light bulb position identifies the code by watching the glow of the light bulb. In the original telegraph, this person listened to a buzzer or “sounder” to identify the code.

Coded patterns of changes from one state to another as time passes carry the information. At any instant of time the signal is either one of two levels. The variations in the signal are always between set discrete levels, but, in addition, a very important component of digital systems is the timing of signals. In many cases, digital signals, either at discrete levels, or changing between discrete levels, must occur precisely at the proper time or the digital system will not work. Timing is maintained in digital systems by circuits called system clocks. This is what identifies a digital signal and the information being processed in a digital system.

Binary

The two levels—ON and OFF—are most commonly identified as 1(one) and zero (0) in modern binary digital systems, and the 1 and 0 are called **binary digits** or **bits** for short. Since the system is binary (two levels), the maximum code combinations  $2^n$  depends on the number of bits,  $n$ , used to represent the information. For example, if numbers were the only quantities represented, then the codes would look like *Figure 1-4*, when using a 4-bit code to represent 16 quantities. To represent larger quantities more bits are added. For example, a 16-bit code can represent 65,536 quantities. The first bit at the right edge of the code is called the *least significant bit* (LSB). The left-most bit is called the *most significant bit* (MSB).


Binary Numerical Quantities

Our normal numbering system is a decimal system. *Figure 1-5* is a summary showing the characteristics of a decimal and a binary numbering system. Note that each system in *Figure 1-5* has specific digit positions with specific assigned values to each position. Only eight digits are shown for each system in *Figure 1-5*. Note that in each system, the LSB is either  $10^0$  in the decimal system or  $2^0$  in the binary system. Each of these has a value of one since any number to the zero power is equal to one. The following examples will help to solidify the characteristics of the two systems and the conversion between them.

| Decimal<br>( $XX_{10}$ ) | Binary<br>( $XXXX_2$ ) | Most significant bit<br>(MSB) | Least significant bit<br>(LSB) |
|--------------------------|------------------------|-------------------------------|--------------------------------|
| 0                        | 0000                   |                               |                                |
| 1                        | 0001                   |                               |                                |
| 2                        | 0010                   |                               |                                |
| 3                        | 0011                   |                               |                                |
| 4                        | 0100                   |                               |                                |
| 5                        | 0101                   |                               |                                |
| 6                        | 0110                   |                               |                                |
| 7                        | 0111                   |                               |                                |
| 8                        | 1000                   |                               |                                |
| 9                        | 1001                   |                               |                                |
| 10                       | 1010                   |                               |                                |
| 11                       | 1011                   |                               |                                |
| 12                       | 1100                   |                               |                                |
| 13                       | 1101                   |                               |                                |
| 14                       | 1110                   |                               |                                |
| 15                       | 1111                   |                               |                                |

Figure 1-4: 4-bit codes to represent 16 quantities

## a. Decimal

 

## b. Binary

 


Figure 1-5: Decimal and binary numbering systems  
Courtesy of Master Publishing, Inc.

### Example 1. Identifying the Weighted Digit Positions of a Decimal Number

Separate out the weighted digit positions of 6524.

**Solution:**

$$6524 = 6 \times 10^3 + 5 \times 10^2 + 2 \times 10^1 + 4 \times 10^0$$

$$6524 = 6 \times 1000 + 5 \times 100 + 2 \times 10 + 4 \times 1$$

$$6524 = 6000 + 500 + 20 + 4$$

Can be identified as  $6524_{10}$  since decimal is a base 10 system. Normally 10 is omitted since it is understood.

Example 2. Converting a Decimal Number to a Binary Number

Convert 103 to a binary number.

Solution:

103<sub>10</sub>/2 = 51 with a remainder of 1  
51/2 = 25 with a remainder of 1  
25/2 = 12 with a remainder of 1  
12/2 = 6 with a remainder of 0  
6/2 = 3 with a remainder of 0  
3/2 = 1 with a remainder of 1  
1/2 = 0 with a remainder of 1 (MSB)  
103<sub>10</sub> = 1100111

Example 3. Determining the Decimal Value of a Binary Number

What decimal value is the binary number 1010111?

Solution:

Solve this the same as Example 1, but use the binary digit weighted position values.

Since this is a 7-bit number:

And since the MSB is a 1, then MSB = 1 × 2<sup>6</sup> = 64  
and (next digit) 0 × 2<sup>5</sup> = 0  
and (next digit) 1 × 2<sup>4</sup> = 16  
and (next digit) 0 × 2<sup>3</sup> = 0  
and (next digit) 1 × 2<sup>2</sup> = 4  
and (next digit) 1 × 2<sup>1</sup> = 2  
and (next digit, LSB) 1 × 2<sup>0</sup> = 1  
87

Binary Alphanumeric Quantities

If alphanumeric characters are to be represented, then Figure 1-6, the ASCII table defines the codes that are used. For example, it is a 7-bit code, and capital M is represented by 1001101. Bit #1 is the LSB and bit #7 is the MSB. As shown, upper and lower case alphabet, numbers, symbols, and communication codes are represented.

Accuracy vs. Speed—Analog and Digital

Quantities in nature and in the human world are typically analog. The temperature, pressure, humidity and wind velocity in our

| Bit Position |   |   |   |   |   |                   |   |   |   |     |   |    |     |     |
|--------------|---|---|---|---|---|-------------------|---|---|---|-----|---|----|-----|-----|
|              |   |   |   |   |   | 0 1 0 1 1 0 0 1   |   |   |   |     |   |    |     |     |
|              |   |   |   |   |   | 0 0 1 1 1 1 0 0 0 |   |   |   |     |   |    |     |     |
| 1            | 2 | 3 | 4 | 5 | 6 | 7                 | 1 | 1 | 1 | 1   | 0 | 0  | 0   | 0   |
| 0            | 0 | 0 | 0 |   |   |                   | @ | P | ' | p   | 0 | sp | NUL | DLE |
| 1            | 0 | 0 | 0 |   |   |                   | A | Q | a | q   | 1 | !  | SOH | DC1 |
| 0            | 1 | 0 | 0 |   |   |                   | B | R | b | r   | 2 | "  | STX | DC2 |
| 1            | 1 | 0 | 0 |   |   |                   | C | S | c | s   | 3 | #  | ETX | DC3 |
| 0            | 0 | 1 | 0 |   |   |                   | D | T | d | t   | 4 | \$ | EOT | DC4 |
| 1            | 0 | 1 | 0 |   |   |                   | E | U | e | u   | 5 | %  | ENQ | NAK |
| 0            | 1 | 1 | 0 |   |   |                   | F | V | f | v   | 6 | &  | ACK | SYN |
| 1            | 1 | 1 | 0 |   |   |                   | G | W | g | w   | 7 | '  | BEL | ETB |
| 0            | 0 | 0 | 1 |   |   |                   | H | X | h | x   | 8 | (  | BS  | CAN |
| 1            | 0 | 0 | 1 |   |   |                   | I | Y | i | y   | 9 | )  | HT  | EM  |
| 0            | 1 | 0 | 1 |   |   |                   | J | Z | j | z   | : | *  | LF  | SUB |
| 1            | 1 | 0 | 1 |   |   |                   | K | [ | k | {   | ; | +  | VT  | ESC |
| 0            | 0 | 1 | 1 |   |   |                   | L | \ | l |     | < | ,  | FF  | FS  |
| 1            | 0 | 1 | 1 |   |   |                   | M | ] | m | }   | = | -  | CR  | GS  |
| 0            | 1 | 1 | 1 |   |   |                   | N | ^ | n | ~   | > | .  | SO  | RS  |
| 1            | 1 | 1 | 1 |   |   |                   | O | _ | o | DEL | ? | /  | SI  | US  |


Figure 1-6: American Standard Code for Information Interchange—ASCII code  
TEAM LRN

environment all change smoothly and continuously, and in many cases, slowly. Instruments that measure analog quantities usually have slow response and less than high accuracy. To maintain an accuracy of 0.1% or 1 part in 1000 is difficult with an analog instrument.

Digital quantities, on the other hand, can be maintained at very high accuracy and measured and manipulated at very high speed. The accuracy of the digital signal is in direct relationship to the number of bits used to represent the digital quantity. For example, using 10 bits, an accuracy of 1 part in 1024 is assured. Using 12 bits gives four times the accuracy (1 part in 4096), and using 16 bits gives an accuracy of 0.0015%, or 1 part in 65,536. And this accuracy can be maintained as digital quantities are manipulated and processed very rapidly, millions of times faster than analog signals.

The advent of the integrated circuit has propelled the use of digital systems and digital processing. The small space required to handle a large number of bits at high speed and high accuracy, at a reasonable price, promotes their use for high-speed calculations.

As a result, if analog quantities are required to be processed and manipulated, the new design technique is to first convert the analog quantities to digital quantities, process them in digital form, reconvert the result to analog signals and output them to their destination to accomplish a required task. The complete procedure is indicated in *Figure 1-7*, and the need for analog circuits, digital circuits and the conversion circuits between them is immediately apparent.

 

**Figure 1-7: A typical system describing the functions in the analog-to-digital and digital-to-analog chain**

## Interface Electronics

The system shown in *Figure 1-7* shows the major functions needed to couple analog signals to digital systems that perform calculations, manipulate, and process the digital signals and then return the signals to analog form. This chapter deals with the analog-to-digital portion of *Figure 1-7*, and *Chapter 2* will deal with the digital-to-analog portion.

## The Basic Functions for Analog-to-Digital Conversion

### Sensing the Input Signal

*Figure 1-8* separates out the analog-to-digital portion of the *Figure 1-7* chain to expand the basic functions in the chain. Most of nature's inputs such as temperature, pressure, humidity, wind velocity, speed, flow rate, linear motion or position are not in a form to input them directly to electronic systems. They must be changed to an electrical quantity—a voltage or a current—in order to interface to electronic circuits.

 


Figure 1-8: The basic functions for analog-to-digital conversion

The basic function of the first block is called sensing. The components that sense physical quantities and output electrical signals are called sensors.

The sensor illustrated in *Figure 1-8* measures pressure. The output is in millivolts and is an analog of the pressure sensed. An example output plotted against time is shown.

Conditioning the Signal

Conditioning the signal means that some characteristic of the signal is being changed. In *Figure 1-8*, the block is an amplifier that increases the amplitude of the signal by 1,000 times so that the output signal is now in volts rather than millivolts. The amplification is linear and the output is an exact reproduction of the input, just changed in amplitude. Other signal conditioning circuits may reduce the signal level, or do a frequency selection (filtering), or perform an impedance conversion. Amplification is a very common signal conditioning function. Some electronic circuits handle only small-signal signals, while others are classified as power amplifiers to supply the energy for outputs that require lots of joules (watts are joules/second).


Analog-to-Digital Conversion

In the basic analog-to-digital conversion function, as shown in *Figure 1-7*, the analog signal must be changed to a digital code so it can be recognized by a digital system that processes the information. Since the analog signal is changing continuously, a basic subfunction is required. It is called a *sample-and-hold* function. Timing circuits (clocks) set the sample interval and the function takes a sample of the input signal and holds on to it. The sample-and-hold value is fed to the analog-to-digital converter that generates a

digital code whose value is equivalent to the sample-and-hold value. This is illustrated in *Figure 1-8* as the conditioned output signal is sampled at intervals 0, 1, 2, 3, and 4 and converted to the 4-bit codes shown. Because the analog signal changes continually, there may be an error between the true input voltage and the voltage recorded at the next sample.

 Example 4. A to D Conversion

For the analog signal shown in the plot of voltage against time and the 4-bit codes given for the indicated analog voltages, identify the analog voltage values at the sample points and the resultant digital codes and fill in the following table.



| Sample Interval | Signal Value | Digital Code |   |   |   |
|-----------------|--------------|--------------|---|---|---|
|                 |              | 4            | 3 | 2 | 1 |
| 0               |              |              |   |   |   |
| 1               |              |              |   |   |   |
| 2               |              |              |   |   |   |
| 3               |              |              |   |   |   |
| 4               |              |              |   |   |   |
| 5               |              |              |   |   |   |
| 6               |              |              |   |   |   |

| Answer:         |              |              |   |   |   |
|-----------------|--------------|--------------|---|---|---|
| Signal Interval | Signal Value | Digital Code |   |   |   |
| 0               | 0.3V         | 0            | 0 | 1 | 1 |
| 1               | 0.7V         | 0            | 1 | 1 | 1 |
| 2               | 1.5V         | 1            | 1 | 1 | 0 |
| 3               | 1.25V        | 1            | 1 | 0 | 0 |
| 4               | 0.95V        | 1            | 0 | 0 | 1 |
| 5               | 0.8V         | 1            | 0 | 0 | 0 |
| 6               | 1.1V         | 1            | 0 | 1 | 1 |

Obviously, one would like to increase the sampling rate to reduce this error. However, depending on the code conversion time, if the sample rate gets to large, there is not enough time for the conversion to be completed and the conversion function fails. Thus, there is a compromise in the analog-to-digital converter between the speed of the conversion process and the sampling rate. Output signal accuracy also plays a part. If the output requires more bits to be able to represent the magnitude and the accuracy required, then higher-speed conversion circuits and more of them are going to be required. Thus, design time, cost, and all the design guidelines enter in. *Chapter 5* is a complete chapter on the conversion techniques to explore this function in detail. As shown in *Figure 1-8*, the bits of the digital code are presented all at the same time (in parallel) at each sample point. Other converters may present the codes in a serial string. It depends on the conversion design and the application.

Summary

This chapter reviewed analog and digital signals and systems, digital codes, the decimal and binary number systems, and the basic functions required to convert analog signals to digital signals. The next chapter will complete the look at the basic functions required to convert digital signals to analog signals. It will be important to have these basic functions in mind as the electronic circuits that perform these functions are discussed in the upcoming chapters.



**Chapter 1 Quiz**

1. A new design technique available to analog system designers is:
  - a. Sense the analog, compute using analog, output analog.
  - b. Sense the analog, convert to digital, compute digitally, convert to analog, output analog.
  - c. Sense the analog, convert to digital, compute digitally, output digitally.
  - d. Sense digitally, compute digitally, output digitally.
2. Analog quantities:
  - a. vary smoothly, then change abruptly to new values.
  - b. consist of codes of high-level and low-level signals.
  - c. vary smoothly continuously.
  - d. have periods of high-level and low-level signals, then change to continuous signals.
3. Digital signals:
  - a. vary smoothly, then change abruptly to new values.
  - b. consist of codes of high-level and low-level signals.
  - c. vary smoothly continuously.
  - d. have periods of high-level and low-level signals, then change to continuous signals.
4. Electronic system designers must interface between:
  - a. the human world and the electronic world.
  - b. the wholesale world and the retail world.
  - c. the private business world and the government business world.
  - d. the analog world and the digital world.
  - e. a and d above.
  - f. none of the above.
5. In analog electronic systems, analog quantities are:
  - a. not analogous to the original quantity.
  - b. are not a copy of the original quantity in another form.
  - c. are output in digital form.
  - d. are a copy of the analog physical quantity in another form.
6. Binary digital systems:
  - a. have two discrete levels—1 or 0, high level or low level.
  - b. have three or more discrete levels.
  - c. have a level that varies continuously with time.
  - d. have binary digits, or bits for short.
  - e. none of the above.
  - f. d and a above.
7. Decimal numbering systems have:
  - a. weighted digit positions that vary randomly.
  - b. weighted digit positions varying by powers of 10.
  - c. weighted digit positions varying by powers of 2.
  - d. weighted digit positions that remain constant at one value.
8. Decimal numbering systems have:
  - a. weighted digit positions that vary randomly.
  - b. weighted digit positions varying by powers of 10.
  - c. weighted digit positions varying by powers of 2.
  - d. weighted digit positions that remain constant at one value.

9. Physical quantities in the human world are typically:
  - a. digital and analog.
  - b. analog and digital.
  - c. digital.
  - d. analog.
10. Digital systems represent quantities:
  - a. using combinations of binary digits in codes.
  - b. using more bits in its binary codes as the quantity value increases.
  - c. using more bits in its binary code as more accuracy is required.
  - d. using binary codes with just two levels – 1 or 0, high level or low level.
  - e. none of the above.
  - f. all of the above.
11. Analog quantities:
  - a. usually have slow response and less than high accuracy.
  - b. can be maintained at very high accuracy at very high computing speeds.
  - c. are impossible to compute.
  - d. either have slow response or very high accuracy.
12. Digital quantities:
  - a. usually have slow response and less than high accuracy.
  - b. can be maintained at very high accuracy at very high computing speeds.
  - c. are impossible to compute.
  - d. either have slow response or very high accuracy.
13. The basic functions for A-to-D (analog-to-digital) conversions are:
  - a. Sense, compute digitally, convert to analog.
  - b. compute as analog, sense, convert to digital.
  - c. convert to digital, sense, condition to analog.
  - d. sense, condition, convert to digital.
14. Sensing:
  - a. computes analog quantities in nature.
  - b. separates out analog quantities into different categories.
  - c. changes quantities in nature to electrical signals.
  - d. detects analog quantities by their magnitude.
15. Conditioning signals:
  - a. means that the signals are being exercised.
  - b. means that some characteristic of the signal is being changed.
  - c. means that the input signal may be increased or decreased in amplitude, filtered or its impedance changed.
  - d. means that nothing is done to the input signal.
  - e. b and c above.
  - f. a and d above.

Answers: 1.b, 2.c, 3.b, 4.e, 5.d, 6.f, 7.b, 8.c, 9.d, 10.f, 11.a, 12.b, 13.d, 14.c, 15.e.

# Signal Paths from Digital to Analog

## Introduction

Refer back to *Figure 1-7*. In *Chapter 1*, the basic functions used for the analog-to-digital portion of *Figure 1-7* were discussed. In this chapter, the basic functions of the digital-to-analog portion will be discussed.

## The Digital-to-Analog Portion

The digital-to-analog portion is separated out from *Figure 1-7* in *Figure 2-1*. After the digital processing system completes its manipulation of the signal, the output digital codes are coupled to a digital-to-analog converter that changes the digital codes back to an equivalent analog signal. From the output of the digital-to-analog converter, the analog signal is coupled to a signal conditioner that changes the characteristics of the signal. Just as in *Chapter 1*, as the application demands, the amplitude of the signal may be increased with amplification, or decreased with attenuation. Or maybe the power level of the signal is changed, or there may be an impedance transformation to fit the transducer to which the output signal couples.

The output of the system is to some real-world quantity external to the electronic system. As shown in *Figure 2-1*, the output might be a meter, a gauge, a motor, a lever arm to produce motion, a heater, or other similar output.

 



Figure 2-1: Digital-to-analog portion of the signal chain

## Digital-to-Analog Conversion

*Figure 2-2* illustrates the basic digital-to-analog function. The digital processing system outputs digital information in the form of digital codes, and as shown, the digital codes are usually presented to the input of the digital-to-analog converter in one of two ways.

### Parallel Transfer of Data

The first way—parallel bit transfer—means that all bits of the digital code are outputted at the same time. In *Figure 2-2*, a 4-bit code is used as an example. The 4-bit codes are coupled out in sequence as they are processed by the digital processor. They arrive at a preset data interval. In *Figure 2-2*, the 4-bit code 1000 is outputted first, followed by 1011, 1001, 0110, 1010, and 1100, respectively. The digital-to-analog converter

 

**Figure 2-2: The basic function of digital-to-analog conversion**

accepts all bits at the same time. It must have four input lines, the same number of input lines as the 4-bit code. In most modern day digital-to-analog converters the 4-bit codes of *Figure 2-2* are really 8-bit, or most likely 16-bit codes.

### Example 1. Parallel Output

Refer to *Figure 2-2*. If the output of the digital-to-analog converter were an 8-bit code, what would the parallel bit codes be that are coupled out in sequence. Use the same value of analog signal.

#### Solution:

The analog values and the 4-bit codes are listed first. Since an 8-bit code can represent 256 segments, its codes for the same analog value are shown with the maximum analog signal of 1.5V equal to 255. Notice that the 8-bit code is two groups of 4-bit codes, which are also expressed in hexadecimal form.

| Analog value | 4-bit code | Hex | 8-bit code | Hex |
|--------------|------------|-----|------------|-----|
| 0            | 0000       | 0   | 0000 0000  | 00  |
| 0.1          | 0001       | 1   | 0001 0001  | 11  |
| 0.2          | 0010       | 2   | 0010 0010  | 22  |
| 0.3          | 0011       | 3   | 0011 0011  | 33  |
| 0.4          | 0100       | 4   | 0100 0100  | 44  |
| 0.5          | 0101       | 5   | 0101 0101  | 55  |
| 0.6          | 0110       | 6   | 0110 0110  | 66  |
| 0.7          | 0111       | 7   | 0111 0111  | 77  |
| 0.8          | 1000       | 8   | 1000 1000  | 88  |
| 0.9          | 1001       | 9   | 1001 1001  | 99  |
| 1.0          | 1010       | A   | 1010 1010  | AA  |
| 1.1          | 1011       | B   | 1011 1011  | BB  |
| 1.2          | 1100       | C   | 1100 1100  | CC  |
| 1.3          | 1101       | D   | 1101 1101  | DD  |
| 1.4          | 1110       | E   | 1110 1110  | EE  |
| 1.5          | 1111       | F   | 1111 1111  | FF  |

### Serial Transfer of Data

The second way is serial transfer of data. As shown in *Figure 2-2*, the 4-bit codes are outputted one bit at a time, each following the other in sequence, and each group of four bits following each other in sequence. A clock rate determines the rate at which the bits are transferred. The digital-to-analog converter accepts the bits in sequence and reassembles them into the respective bit groups and then acts on them.

#### Example 2. Bit Rate

Refer to *Figure 2-2*. If the clock that outputs the bits in a serial output is 1 MHz, what are the serial bit transfer rate and the parallel bit transfer rate for a 4-bit and an 8-bit code?

**Solution:**

| Clock (Hz) | Serial |       | Parallel |       |
|------------|--------|-------|----------|-------|
|            | 4-bit  | 8-bit | 4-bit    | 8-bit |
| 1 MHz      | 1 MHz  | 1 MHz | 4 MHz    | 8 MHz |

### The Conversion

The digital codes received by the digital-to-analog converter are equivalent to a particular analog value. As shown in *Figure 2-2*, the input code is converted to and outputted as the equivalent analog value and held as this value until the next code equivalent value is outputted. Thus, as shown, the output of the digital-to-analog converter is a stair-step output that stays constant at a particular level until the next input digital code is received. The output resembles an analog signal but further processing is required in order to arrive at the final analog signal.

### Filtering

A basic function required after the digital-to-analog conversion is filtering, or in more general terms, smoothing. As shown in *Figure 2-2*, such filtering produces an analog signal more equivalent to an analog signal that changes smoothly and continuously. The filter physically may be in the digital-to-analog converter or in the signal conditioner that follows it as shown in *Figure 2-2*. It was placed in the signal conditioner in *Figure 2-2* because it really is a signal conditioning function.

### Conditioning the Signal

The function of conditioning the signal for the digital-to-analog portion can be the same as for the analog-to-digital portion. A most common function is amplification of the signal, but in like fashion, there is often the need to attenuate the signal; that is, to reduce the amplitude instead of increasing the amplitude. That is the function chosen for *Figure 2-3*. The output signal is attenuated to one-half the value of the input. No other characteristics of the signal are changed. The shape of the amplitude variations of the waveform with time are not changed, so the signal appears the same except its amplitude values are reduced.

### Transducing the Signal

The output of the analog systems discussed is a human world parameter external to the electronic system. As mentioned previously several times, it may be a temperature, or a pressure, or a measure of humidity, or a linear motion, or a rotation. Thus, the electronic output of the signal conditioning function, in many cases, must be changed in form. It may be a voltage or a current out of the electronic system and must be changed to another form of energy.

A device to change or convert energy from one form to another is called a transducer. In *Figure 2-4*, the transducer is a meter that shows the amplitude of the output voltage on a voltage scale. The voltage output from the electronic system is converted to the rotation of a needle in front of a scale marked on the material

 


Figure 2-3: Signal conditioning function

behind the needle. The scale is calibrated so particular needle deflections represent specific voltage values. Thus, any deflection of the needle as a result of the electronic circuit output can be read as a particular voltage value at any instant of time. The electronic system output has been converted to a meter reading, and the meter reading can be calibrated into the type of parameter the system is measuring. It could be a fluid level, a rate of flow, a pressure, and so forth.

Similar changes in energy form occur in other types of transducers. The voltage or current output from the electronic system gets converted to all forms of human world parameters just by the choice of the transducer.

 


Figure 2-4: The transducer function

### Examples of Transducers

Figure 2-5 shows examples of various types of transducers. Figure 2-5a is a picture of a speaker enclosure. Inside is what is called a driver. It is a common transducer that takes electrical audio signals and converts them into sound waves. The driver is placed inside a box to make it into a very good sounding speaker enclosure. Many times the driver only handles the low and mid-frequency audio signals, so another driver for the high frequencies, called a tweeter, is inserted into the speaker enclosure to allow the speaker to reproduce a broader range of audio frequencies.

 


Figure 2-5: Examples of transducers

There is a counterpart transducer to the speaker—a microphone—that is used as an input device for sensing the signal. It is shown in *Figure 2-5b*. The microphone converts sound signals into electrical signals so they may be inputted into an electronic system.

*Figure 2-5c* shows a motor. Normally a motor is not classified as a transducer, but it is. A motor takes electrical energy and converts it into rotational torque. Motors are used everywhere, from running machinery, to trimming grass, to providing transportation.

*Figure 2-5d* shows a solenoid. A solenoid is a transducer that converts electrical energy into linear motion. It consists of a coil of wire with a soft iron core inside of it. When current is passed through the coil, a magnetic field is produced that pulls on the soft iron core and draws it inside the core. The movement of the core can be used to move a lever arm, to close a door, to operate a shutter, and so forth.

There are many more examples of transducers that convert electrical energy into a pressure, a valve for controlling fluid flow, a temperature gauge, and so forth. As various applications are described in subsequent chapters many will use various types of transducers.

## Summary

The discussion in this chapter covered the functions necessary to convert a digital signal into an analog output and then into a human world parameter. It completed the signal chain from an input analog signal, to a digital conversion, to computation in digital form, to a conversion back to an output analog signal, to an output human world parameter. The next chapter will examine the sensing function in detail.

## Chapter 2 Quiz

1. A digital-to-analog converter:
  - a. outputs a digital signal in serial form.
  - b. outputs an analog signal in stair-step form.
  - c. outputs a smooth and continuous analog signal.
  - d. outputs one digital code after another.
2. The output of the digital-to-analog chain is:
  - a. a serial digital code string.
  - b. a parallel digital code stream.
  - c. a real-world quantity.
  - d. always a meter reading.
3. An input to a digital-to-analog converter may be:
  - a. a parallel transfer of digital codes.
  - b. an analog signal of suitable amplitude.
  - c. an analog signal of discrete values.
  - d. a serial transfer of digital codes.
  - e. a and d above.
  - f. b and c above.
4. In a parallel transfer of bits:
  - a. all bits of a digital code are transferred at the same time.
  - b. all bits of a digital code are transferred in a sequential string.
  - c. all bits are filtered into an analog signal.
  - d. all bits are signal conditioned one at a time.
5. In a serial transfer of bits:
  - a. all bits of a digital code are transferred at the same time.
  - b. all bits of a digital code are transferred in a sequential string.
  - c. all bits are filtered into an analog signal.
  - d. all bits are signal conditioned one at a time.
6. The output of the digital-to-analog converter is:
  - a. a stair-step output that varies until the next input digital code is received.
  - b. a stair-step output that changes between 1 and 0 until the next digital code is received.
  - c. a stair-step output that stays constant at a particular level until the next digital code is received.
  - d. a stair-step output that changes from maximum to minimum until the next digital code is received.
7. The digital-to-analog output must be filtered to:
  - a. clarify the digital steps in the output.
  - b. keep the stair-step digital output.
  - c. make the analog output change smoothly and continuously.
  - d. make the analog output more like a digital output.
8. A transducer is:
  - a. a device to change or convert energy from one form to another.
  - b. a device that maintains the analog output in digital steps.
  - c. a device that converts analog signals to digital signals.
  - d. a device that converts digital signals to analog signals.



9. A motor is:
  - a. a transducer that changes digital signals into analog signals.
  - b. a transducer that changes analog signals into digital signals.
  - c. a transducer that raises the analog voltage output to a higher voltage.
  - d. a transducer that changes electrical energy into rotational torque.
10. A meter is:
  - a. a transducer that converts the analog output to the rotation of a needle in front of a scale.
  - b. a transducer that changes analog signals into digital signals.
  - c. a transducer that raises the analog voltage output to a higher voltage.
  - d. a transducer that changes digital signals into analog signals.

Answers: 1.b, 2.c, 3.e, 4.a, 5.b, 6.c, 7.c, 8.a, 9.d, 10.a.

# Sensors

## Introduction

In *Chapter 1*, *Figure 1-8* shows the basic functions needed when going from an analog quantity to a digital output. The first of these is sensing the analog quantity. The device used in the function to sense the input quantity and convert it to an electrical signal is called a *sensor*—the main subject of this chapter.


A sensor is a device that detects and converts a natural physical quantity into outputs that humans can interpret. Examples of outputs are meter readings, light outputs, linear motions and temperature variations. *Chapter 1* indicated that a majority of these physical quantities are analog quantities; i.e., they vary smoothly and continuously. Sensors, in their simplest form, are devices that contain only a single element that does the necessary transformation. Although today, more and more complicated sensors are being manufactured; they cover more than the basic function, containing sensing, signal conditioning and converting all in one package.

In this chapter, in order to clearly communicate the sensing function, the majority of sensors will be single element sensors that output electrical signals—voltage, current or resistance. But also, closely coupled to sensors with electrical outputs, sensors are included that use magnetic fields for their operation.


## Temperature Sensors

### Oral Temperature

Everyone, sometime or another, has had the need to find out their body temperature or the body temperature of a member of their family. An oral thermometer like the one shown in *Figure 3-1* was probably used. Liquid mercury inside of a glass tube expands and pushes up the scale on the tube as temperature increases. The scale is calibrated in degrees (°F—Fahrenheit in this case) of body temperature; therefore, the oral thermometer converts the physical quantity of temperature into a scale value that humans can read. The oral thermometer is a temperature sensor with a mechanical scale readout.

 

**Figure 3-1: Oral thermometer**

 


**Figure 3-2: Rear-view of bimetal strip thermometer**

### Indoor/Outdoor Thermometer

Another temperature sensor is shown in *Figure 3-2*. It is a bimetal strip thermometer. Two dissimilar metals are bonded together in a strip that is formed into a spring. The metals expand differently with temperature; therefore, a force is exerted between them that expands the spring and rotates the needle as the temperature increases. The thermometer scale is calibrated to known temperatures—boiling water and freezing water. These points establish a scale and the device is made into a commercial thermometer with Fahrenheit (°F) and/or Celsius (Centigrade—°C) scales. The one shown in *Figure 3-2* is for °F. The outdoor thermometer is another type of temperature sensor that converts the physical quantity of temperature into a meter reading easy for humans to see and interpret.

## Thermocouples


A thermocouple is another common temperature sensor. A place to find one is in a natural gas furnace in a home similar to that shown in *Figure 3-3*. It controls the pilot light for the burners in the furnace. The thermocouple is a closed tube system that contains a gas. The gas expands as it is heated and expands a diaphragm at the end of the tube that is in the gas control module.

 

**Figure 3-3: A residential furnace pilot light control**

The system works as follows: A button on the pilot light gas control module is pressed to open valve A to initially allow gas to flow to light the pilot light. The expanded diaphragm of the thermocouple system controls valve A; therefore, the button for the pilot light must be held until the thermocouple is heated by the pilot light so that the gas expands and expands the diaphragm. The expanded diaphragm holds valve A open; therefore, the pilot light button can be released because the pilot light heating the thermocouple keeps the gas expanded. Since the pilot light is burning, any demand for heat from the thermostat will light the burners and the house is heated until the demand by the thermostat is met.


A thermocouple that puts out an electrical signal as temperature varies is shown in *Figure 3-4*. It is constructed by joining two dissimilar metals. When the junction of the two metals is heated, it generates a voltage, and the result is a temperature

 

**Figure 3-4: A bimetal thermocouple**

sensor that generates millivolts of electrical signal directly. The total circuit really includes a cold-junction reference, but the application uses the earth connection of the package as the cold reference junction.

There may be a need to amplify the output signal from the sensor, as shown in *Figure 3-5*, because the output voltage amplitude must be increased to a useful level. This is the subject of *Chapter 4*, signal conditioning.

 

**Figure 3-5: A sensor output signal may have to be increased to a useful level by amplification**

## Silicon-Junction Diode

Another sensor that produces a voltage directly as temperature varies is a silicon-junction diode.

The characteristic curves for its forward and reverse voltage with current are shown in *Figure 3-6*. The forward current versus forward voltage for positive voltages increases little until the forward voltage reaches +0.7V, then it increases rapidly. Here the forward resistance is very small—in the order of 50  $\Omega$  to 80  $\Omega$ .

The reverse current for negative reverse voltage is 1,000 times and more smaller than the forward current. It stays relatively flat with reverse voltage until the magnitude reaches the reverse breakdown voltage. When

the junction is reversed biased below the breakdown voltage, the reverse resistance is very large—in the order of megohms. The forward voltage and reverse breakdown voltage decrease as temperature is increased; thus, the diode junction has a negative temperature coefficient. The forward voltage has a much smaller voltage variation with temperature than does the reverse breakdown voltage. The reverse current below the breakdown region can also be used for a temperature sensor. A rule of thumb for the reverse current is that it doubles for every 10°C rise in temperature. The reverse conditions are used for temperature sensors, but the most common is to use the forward voltage change.

 


Figure 3-6: Silicon P-N junction characteristics

**Example 1. Temperature Coefficient**

Using Figure 3-6, calculate the temperature coefficient of the forward voltage of the diode and show that it is negative. The forward current  $I_F = 5 \text{ mA}$ .

**Solution:**

| T °C   | V <sub>F</sub> |
|--------|----------------|
| 25     | 1.02V          |
| 50     | 0.70V          |
| Δ = 25 | −0.32V         |

Temp Coefficient =  $\Delta V_F / \Delta T = -0.32\text{V} / 25^\circ\text{C} = -0.0128\text{V}/^\circ\text{C}$

**Thermistor**

A thermistor is a resistor whose value varies with temperature. Figure 3-7a shows the characteristics of a thermistor readily available at RadioShack. Two circuits for the use of thermistors are shown in Figure 3-7. Figure 3-7b uses the thermistor in a voltage divider to produce a varying voltage output. Figure 3-7c uses a transistor to amplify the current change provided by the thermistor as

 


Figure 3-7: Thermistor temperature sensor  
TEAM LRN  
20

temperature changes. In some micromachined thermistors, the resistance at 25°C is of the order of 10 kΩ. One of the disadvantages of using a thermistor is that its characteristics with temperature are not linear. As a result, in order to produce linear outputs, the nonlinearity must be compensated for.

## Angular and Linear Position

### Position Sensor—Fuel Level

In *Chapter 1, Figure 1-2*, an automobile fuel gauge was used to demonstrate an analog quantity. That same example will be used, as shown in *Figure 3-8a*, to demonstrate the sensing function. The complete sensor consists of a float that rides on the surface of fuel in a fuel tank, a lever arm connected to the float at one end, and, at the other end, connected to the shaft of a potentiometer (variable resistor). As the fuel level changes, the float moves and rotates the variable contact on the potentiometer. The schematic of *Figure 3-8b* shows that the potentiometer is connected across the automobile battery from +12V to ground. The variable contact on the potentiometer moves in a proportional manner. When the contact is at the end of the potentiometer that is connected to ground, the output voltage will be zero volts from the variable contact to ground. At the other end, the one connected to +12V, there will be +12V from the variable contact to ground. For any position of the variable contact in between the end points, the voltage from the variable contact to ground will be proportional to the amount of the shaft rotation.

Calibrating it as shown in *Figure 3-8c* completes the liquid-level sensor. At a full tank, the float, lever arm and potentiometer shaft rotation are designed so that the variable contact is at the +12V end of the potentiometer. When the tank is empty, the same combination of elements results in the variable contact at the ground level (0V). Other positions of the float result in proportional output voltages between the variable contact and ground. As *Figure 3-8c* shows, a three-quarter full tank gives an output of 9V, a half-full tank will give an output of 6V, and a one-quarter full tank will give an output of 3V. Thus, adding a voltmeter to measure the voltage from the variable contact to ground, marked in liquid level, completes the automotive fuel gauge. Sensors that convert a physical quantity into an electrical voltage output are very common. The output voltage can be anywhere from microvolts to tens of volts.

 


Figure 3-8: Position sensor—fuel level gauge  
TEAM LRN

## Hall Effect—Position Sensor


The Hall effect is shown in *Figure 3-9a*. E.H. Hall discovered it. If there is current in a conductor and a magnetic field is applied perpendicular to the direction of the current, a voltage will be generated in the conductor that has a direction perpendicular to both the direction of the current and the direction of the magnetic field. This property is very useful in making sensors, especially when a semiconductor chip is used for the conductor. Not only can the semiconductor be used to generate the Hall voltage, but additional circuitry can be built into the semiconductor to process the Hall voltage. As a result, not only are there linear sensors that generate an output voltage that is proportional to the magnitude of the magnetic flux applied, but, because circuitry can be added to the chip, there are sensors that have switched logic-level outputs, or latched outputs, or outputs whose level depends on the difference between two applied magnetic fields.

## Hall Effect—Switch

*Figure 3-9b* shows a Hall-effect switch and its output when used as a sensor. When the magnetic flux exceeds  $\beta_{ON}$  in maxwells, the output transistor of the switch is ON, and when the field is less than  $\beta_{OFF}$  the output transistor is OFF. There is a hysteresis curve as shown. When the output transistor is OFF, the magnetic field must be greater than zero by  $\beta_{ON}$  before the transistor is ON, but will stay ON until the magnetic field is less than zero by  $B_{OFF}$ . The zero magnetic field point can be “biased” up to a particular value by applying a steady field to make  $\beta_0 = B_{STEADY-STATE}$ .
 
## Hall Effect—Linear Position

A linear Hall-effect sensor is shown in *Figure 3-9c*. Its output voltage varies linearly as the magnetic field varies. When the field is zero, there is a quiescent voltage  $= V_{OQ}$ . If the field is  $+\beta$  (north to south), the voltage  $V_o$  increases from  $V_{OQ}$ ; if the field is  $-\beta$  (south to north), the voltage  $V_o$  decreases from  $V_{OQ}$ . The supply voltage is typically 3.8V to 24V for Hall-effect devices.



The Hall Effect:  
If a conductor has a current in it, and a magnetic field is applied perpendicular to the direction of the current, a voltage (the Hall voltage) is generated in a direction perpendicular to both the current and the magnetic field.

 
 
 
 


Figure 3-9: Hall-effect sensors

### Hall Effect—Brake Pedal Position

A brake pedal position sensor is shown in *Figure 3-10a*. A Hall-effect switching sensor is used. Stepping on the brake moves a magnet away from the Hall-effect sensor and its output switches to a low voltage level turning on the brake light. When the brake is released, the magnetic field is again strong enough to switch the output  $V_O$  to a high level, turning off the brake light.

### Hall Effect—Linear Position Sensor


In *Figure 3-10b*, as the magnet is moved over the sensor the magnetic field produces an output  $V_O$  that is proportional to the strength of the field. The linear output voltage can be converted to a meter reading that indicates the linear position of the assembly that moves the magnet. Amplifying  $V_O$  can increase the sensitivity of the measurement.

### Hall Effect—Angular Position Sensor


A round magnet, half North pole and half South pole, is rotated in front of a linear Hall-effect sensor as shown in *Figure 3-10c*. As the magnet turns the magnetic field varies and produces an output  $V_O$  that is proportional to the angular rotation.  $V_O$  can be converted to a meter reading calibrated in degrees of rotation.
 
### Hall Effect—Current Sensor


Current in a wire produces a magnetic field around the wire as shown in *Figure 3-10d*. If the wire is passed through a soft-iron yoke, the soft iron collects the magnetic field and directs it to a linear Hall-effect sensor. The magnetic field varies as the amplitude of the current varies, which produces a corresponding proportional  $V_O$  from the linear sensor, and, thus, a sensor that detects the amplitude of the current. An alternating current is shown in *Figure 3-10d*; therefore, the voltage  $V_O$  will be an alternating voltage.  $V_O$  is detected in *Figure 3-10d* using an oscilloscope.




a. Hall-effect position sensor (switch)

 

b. Linear position sensor

 

c. Angular position sensor

 

d. Current sensor

Figure 3-10: Hall-effect sensor applications

## Rotation

### Variable Reluctance Sensor

Figure 3-11a shows the physical setup of an electromagnetic sensor that produces a continuous series of voltage pulses as a result of time-varying changes of magnetic flux. The magnetic flux path in Figure 3-11a, called the reluctance path, is through the iron core of the wound coil, through the cog on the rotating wheel and back to the coil. When the cog on the wheel is aligned with the iron core, the concentration of flux is the greatest. As the cog moves toward or away from the core of the coil, the concentration of flux is much less. Anytime magnetic flux changes and cuts across wires, it generates a voltage in the wires. The voltage produces a current in the circuit attached to the wires. As a result of the rotation of the wheel and the cog past the coil, a series of voltage pulses, as shown in Figure 3-11b, is generated. The time,  $t$ , between the pulses varies as the speed of the cogged wheel varies. Counting the pulses over a set period of time, say, a second, the speed (velocity) of the cogged wheel can be calculated. The variations of the speed can be calculated for acceleration, and of course, the presence of pulses means the wheel is in motion. The disadvantage of such a sensor is that there is no signal at zero speed, and the air gap between the mechanical moving part and the coil core must be small, usually equal to or less than 2–3 centimeters.

 


Figure 3-11: Variable reluctance rotation sensor

### Example 2. RPM

A variable reluctance sensor outputs 120 pulses in a time period of 3 seconds. What is the rpm (revolutions per minute)?

**Solution:**


$$\text{rps (revolutions per sec)} = 120/3 = 40 \times 60 \text{ sec} = 2400 \text{ rpm}$$

### Magnetoresistor Sensor


A magnetoresistor sensor changes its resistance proportional to the magnetic flux density to which it is exposed. It is made of a nickel-iron (Permalloy) which is deposited as a thin film onto a semiconductor surface. It requires special fabrication of conducting strips on high-carrier mobility semiconductors such as Indium-Antimonide or Indium Arsenide. The basic principle is shown in Figure 3-12a. The thin film is deposited in a strong magnetic field that orients the magnetization  $M$  in a direction parallel to the length of the resistor. A current is then made to pass through the thin film at an angle  $\theta$  to the  $M$  direction. If the angle is zero, the thin film will have the highest resistance. At an angle  $\theta$ , it will have a lower resistance. When an external magnetic field is applied perpendicular to  $M$ , then  $\theta$  changes and the resistance changes. This is the basic principle that produces a resistance change when a magnetic field is applied and allows the use of the thin film device as a sensor.




Figure 3-12b shows the change in resistance as the angle  $\theta$  of the current in relationship to  $M$  varies. One of the advantages of using magnetoresistor is that other semiconductor circuits can be fabricated on and in the same semiconductor substrate. The resistor element is usually placed in a Wheatstone bridge circuit in order to make a more sensitive measurement.

 

a. Basic principle

 

 b. Change of resistance with  $\theta$  angle



c. Physical construction (Wheatstone bridge)

Figure 3-12: Magnetoresistor sensor

Such a physical layout is shown in Figure 3-12c.


There are shorting bars deposited over the film to direct the bias current at an angle equal to  $45^\circ$ . This is to put the quiescent point in the center of the linear region of operation of the response curve of Figure 3-12b. When  $V_{CC} = 5V$ , the bridge sensitivity can be as much as 15 mV per Oersted of an applied field.

## Pressure
 
### Piezoresistive Diaphragm


The physical construction of a pressure sensor is shown in Figure 3-13a. A fluid or gas under pressure is contained within a tube the end of which is covered with a thin, flexible diaphragm. As the pressure increases the diaphragm deflects. The deflection of the diaphragm can be calibrated to the pressure applied to complete the pressure sensor characteristics.

Modern day semiconductor technology has been applied to the design and manufacturing of pressure sensors. A descriptive diagram is shown in Figure 3-13b. The thin diaphragm is micromachined from a silicon substrate on which a high-resistivity epitaxial layer has been deposited. The position of the diaphragm and its thickness on and in the substrate is defined using typical semiconductor techniques—form a silicon dioxide on the surface, coat it with photoresist, expose the photoresist with ultraviolet light through a mask to define the diaphragm area, and etch away the oxide and silicon to the correct depth for the thin diaphragm. The assembly is then packaged to allow pressure to deflect the diaphragm.



a. Sensor principle

b. Micromachined silicon resistor

 

c. Wheatstone bridge

Figure 3-13: Micromachined pressure sensor

Using integrated circuit metallization techniques, the thin diaphragm, which changes resistance as it deflects, is connected into a Wheatstone bridge circuit as shown in *Figure 3-13c*. This provides a very sensitive, temperature compensated, measuring circuit.  $R_X$  in the circuit is the thin diaphragm resistance exposed to pressure.  $R_1$ ,  $R_2$ , and  $R_3$  are similarly micromachined resistors but they are not exposed to pressure. As temperature changes all the resistors change in like fashion because they are located very close together on the small semiconductor surface and have the same temperature coefficient. As a result, the sensor is temperature compensated. And since the resistors are very close together on the substrate, and are machined at the same time, they are very uniform in value.

### The Wheatstone Bridge

How does the Wheatstone bridge of *Figure 3-13c* work? The sensing voltage,  $V_O$ , is measured across the bridge from point A to point B.  $V_O = 0$  when the bridge is balanced and is at its most sensitive measuring point. The circuit is analyzed as follows:

The voltage from point A to ground is:

$$V_A = R_X / (R_X + R_3) \times V$$

The voltage from point B to ground is:

$$V_B = R_1 / (R_1 + R_2) \times V$$

When the bridge is balanced,  $V_A = V_B$  and

$$R_X / (R_X + R_3) \times V = R_1 / (R_1 + R_2) \times V$$

Cancelling  $V$  on both sides of the equation,

$$R_X / (R_X + R_3) = R_1 / (R_1 + R_2)$$

and transposing,

$$R_X(R_1 + R_2) = R_1(R_X + R_3)$$

or

$$R_X R_2 = R_1 R_3 \text{ because } R_1 R_X \text{ cancels on each side of the equation.}$$

Therefore,

$$R_X = R_3 \times R_1 / R_2$$

At balance, the unknown resistance is equal to  $R_3$  times the ratio of  $R_1$  to  $R_2$ .

As  $R_X$  changes, the bridge will become unbalanced and a voltage,  $V_O$ , other than zero results. The voltage,  $V_O$ , is calibrated to the pressure to complete the sensor characteristics. Pressures from 0–500 psi (pounds per square inch) can be measured with such a pressure sensor. If  $R_1$ ,  $R_2$ , and  $R_3$  all equal 10 k $\Omega$ , when  $R_X$  varies from 10 k $\Omega$  to 20 k $\Omega$ , the output voltage will be approximately from 10 mV to 20 mV per 1 k $\Omega$  of resistance change. One of the advantages of the silicon substrate sensors is that other integrated circuits can be in and on the silicon to provide signal conditioning to the voltage output,  $V_O$ .

#### Example 3. Wheatstone Bridge Characteristic Curve

In the Wheatstone bridge of *Figure 3-13c*,  $R_1 = R_2 = R_3 = 10 \text{ k}\Omega$  and  $R_X$  varies with pressure from 10 k $\Omega$  to 15 k $\Omega$ . Plot the change in voltage,  $V_O$ , against the change in resistance,  $R_X$ . Make  $V = 1 \text{ V}$ .

**Solution:**


$$V_O = V_A - V_B = V(R_X / (R_X + R_3) - R_1 / (R_1 + R_2)) = V(R_X / (R_X + 10 \text{ k}\Omega) - 0.5)$$

| $R_X$ | $R_X + 10\text{ k}\Omega$ | $R_X/(R_X + 10\text{ k}\Omega)$ | $V_O$  |
|-------|---------------------------|---------------------------------|--------|
| 10k   | 20k                       | 0.5                             | 0      |
| 11k   | 21k                       | 0.524                           | 0.024  |
| 12k   | 22k                       | 0.545                           | 0.045  |
| 13k   | 23k                       | 0.5652                          | 0.065  |
| 14k   | 24k                       | 0.5833                          | 0.0833 |
| 15k   | 25k                       | 0.600                           | 0.100  |


Plot these numbers on an X and Y axis with  $X = V$  and  $Y = \Omega$  and the characteristic curve of output voltage against resistance is obtained. The output voltage can then be calibrated to pressure to give a characteristic curve of voltage against pressure.
 
### Capacitive Touch Diaphragm

The capacitive touch diaphragm sensor has the same micromachined structure as that shown in *Figure 3-13b*. However, its sensor principle, shown in *Figure 3-14a*, is different. The thin micromachined diaphragm is deflected as previously, but now the deflected diaphragm is designed to touch against a dielectric layer attached to a metal electrode. It forms a capacitor and as pressure increases, the capacitance between the diaphragm and the metal electrode, separated by the dielectric, increases linearly with pressure. The characteristic curve is shown in *Figure 3-14b*.



a. Sensor principle

 

b. Capacitance vs. pressure

Figure 3-14: Capacitive touch pressure sensor

Both of the micromachined sensors fabricated from silicon have  $-40^\circ$  to  $+135^\circ$  operation. For very extreme operating conditions of aircraft and automotive applications, there is a capacitive sensor with a ceramic diaphragm that deflects into a cavity. Its capacitance again increases with pressure.

### Light Sensors

#### Light Basics (Review)

A brief review is presented of the principles of light and detection by photodiodes and phototransistors. For a more thorough review refer to *Basic Electronics*<sup>1</sup>, Chapter 11. *Figure 3-15* shows how a reverse-biased photodiode has its reverse leakage increased by light shining on it. Photons,

 


Figure 3-15: A reversed-biased photodiode light sensor  
Courtesy of Master Publishing, Inc.

<sup>1</sup> *Basic Electronics*, G. McWhorter, A.J. Evans, © 1994, Master Publishing, Inc.

which are particles of light that are high-frequency electromagnetic waves, are absorbed in the reverse-biased diode depletion layer. They produce free electrons and holes that increase the reverse current. The more photons, the higher the intensity of light, the more energy is absorbed, and the larger the reverse current. Thus, the photodiode is a light sensor with a variable current output.


## The Electromagnetic Spectrum

The electromagnetic spectrum is divided into radio waves and light waves by frequency. Light waves are further divided by into infrared, visible, ultraviolet and X-rays. The spectrum is either expressed in frequency or wavelength. Wavelength is the distance that an electromagnetic wave travels through space in one cycle of its frequency. Since distance is velocity multiplied by time, wavelength can be expressed as the velocity of electromagnetic waves multiplied by the time of one cycle of frequency  $f$ . Since the accepted speed of light is 186,000 miles per second or 300,000,000 meters per second, this is:

$$\lambda(\text{in meters}) = 300,000,000 \text{ meters/sec} \times 1/f(\text{in seconds})$$

or, 
$$\lambda(\text{in meters}) = 300/f(\text{in MHz})$$

If visible light (white light) is passed through a prism, as shown in *Figure 3-16*, the visible light separates into its color components. The frequency of visible light is from 400 million megahertz to 750 million megahertz. The wavelength is from 750 nanometers ( $10^{-9}$ ) to 400 nanometers. Light sensors extend into the infrared frequency range below visible light and into the ultraviolet light frequency range above visible light. Cadmium sulfide sensors are most sensitive in the green light region of visible light, while solar cells and phototransistor sensors are most sensitive in the infrared region.

 

**Figure 3-16: Visible light—its frequency and wavelength**  
Courtesy of Master Publishing, Inc.

## Photoresistor Sensor


A sensor that changes resistance as light is shined on it is made from Cadmium Sulfide (CdS), a semiconductor that is light sensitive. The characteristics of one available at RadioShack are shown in *Figure 3-17a*. In the dark with no light shining on it its resistance is greater than 0.5 M $\Omega$ . With one footcandle of light shining on it, its resistance is 1700  $\Omega$ , and the resistance is reduced to 100  $\Omega$  when 100 footcandles of light shine on it. Circuit applications are shown in *Figure 3-17b*. It can be used to change resistance values, to provide a sensor with a voltage output, or as a sensor supplying current to a load.

### Example 4. Photoresistor Application

Use the circuit of *Figure 3-17b* that provides a voltage output. The resistor  $R_1 = 200 \Omega$ . What is the voltage out,  $V_o$ , when the supply voltage is 10V and the light shining on the sensor is 15 Ftc and 100 Ftc?


**Solution:**

| Ftc | $R_L$        | $R_1$        | $R_1 + R_L$   | $V_o$                       |
|-----|--------------|--------------|---------------|-----------------------------|
| 15  | 800 $\Omega$ | 200 $\Omega$ | 1000 $\Omega$ | $200/1000 \times 10 = 2V$   |
| 100 | 100 $\Omega$ | 200 $\Omega$ | 300 $\Omega$  | $200/300 \times 10 = 6.67V$ |

 

a. Characteristics

Figure 3-17: Photoresistor sensor

 


b. Circuit applications
 
## Solar Cell


The solar cell is again a semiconductor PN junction that is light sensitive. It is made up of an N-type substrate, as shown in *Figure 3-18a*, with a very thin P region over the top surface. Most of the thin P surface is covered with narrow strips of metal that form the anode of the PN diode. A whole network of the narrow strips are interconnected on a silicon wafer to provide increased current output at the PN-junction voltage. The back of the silicon wafer is coated with metal to form the cathode of the diode. Light shining on the surface of the solar cell generates a maximum voltage of about 0.55V. Under load, the average voltage output is approximately 0.5V. A common characteristic curve of voltage plotted against current is shown in *Figure 3-18b*.

Solar cells can be applied in circuits, as shown in *Figure 3-18c*, by paralleling the cells for increased current output, or by connecting the cells in series for increased voltage output. Individual 2 × 4 cm solar cells are available at RadioShack that provide 300 mA at 0.55V, or there are enclosed modules that provide up to 6V at 50 mA.




a. Physical structure

*Courtesy of Master Publishing, Inc.*

 


b. V-I characteristics

 

c. Circuit applications

**Figure 3-18: Solar cell light sensors**

 

d. Trickle charge for RV coach batteries

A very common application for RV motorhomes is shown in *Figure 3-18d*. A solar panel is mounted on the roof of a motorhome and connected as shown to trickle charge the coach batteries when the RV is parked and under light load. Sunlight generates the voltage to supply the trickle current, which helps keep the batteries from discharging. Many units are available with power ratings from 2 to 50 watts.

### Phototransistors

*Figure 3-19* allows a quick review of the operation of bipolar transistors, both NPN and PNP. Recall that for an NPN grounded emitter stage shown in *Figure 3-19a* the emitter is tied to ground, and for active operation, the base voltage is at +0.7V above ground and forward-biases the base-emitter junction. The collector voltage is at a positive voltage above ground (+5V) so the collector-base junction is reverse biased. When there is a current into the base,  $I_B$ , across the forward-biased base-emitter junction, a higher collector current,  $I_C$ , flows across the reverse-biased collector-base junction. There is a current gain through the transistor equal to the collector current divided by the base current,  $I_C/I_B$ . As shown in *Figure 3-19*, the current gain is  $h_{FE}$ . Everything is the same for the operation of the PNP transistor except the voltages are all negative with the emitter tied to ground. The  $h_{FE}$  is the same parameter as for the NPN.

 


Figure 3-19: Bipolar transistor operation

A phototransistor, a transistor designed to be activated by light, has the same basic operation as the NPN and PNP transistor described except it has no base connection. Its wide base junction is left exposed to light. Phototransistors are most sensitive to infrared light. The symbols and voltages are shown in *Figure 3-20a*. Light rays that impact the base-emitter junction effectively produce base current that activates the phototransistor. Through transistor action a larger collector current is produced. As shown by the characteristic curves of *Figure 3-20b*, more light intensity produces more collector current.

A phototransistor can be coupled to the base of a driver transistor, as shown in *Figure 3-20c*, in order to make a linear


 


Figure 3-20: Phototransistor light sensor

driver or a logic-level driver. If a logic-level driver for ON-OFF applications is needed,  $R_{BIAS}$  and  $R_E$  are eliminated and the  $R_{ADJUST}$  used to set the desired sensitivity.  $R_{BIAS}$  and  $R_E$  set the operating point for  $Q_2$  to obtain linear operation of the driver. *Figure 3-20d* shows a phototransistor sensing the presence of light to make a logic-level driver for a relay. The presence of light closes the normally-open contact to the center terminal to activate a connected circuit.
 
## LED Light Source

Even though a light-emitting diode (LED) is not a sensor, it is a very important light source for light sensors. An LED is a forward-biased semiconductor diode as shown in *Figure 3-21a*. LEDs are made from special semiconductor materials other than silicon, but still have the same type of junction characteristics. When a rated amount of current is passed through the forward-biased diode it emits light. The amount of current,  $I$ , through the diode can be adjusted by choosing the value of  $R$  when a given voltage,  $V$ , is used. The forward-biased voltage across the diode is approximately 0.5V, positive (+) on the anode and minus (–) on the cathode.



a. Schematic

| Material                   | $\lambda$ (Å) | Color    |
|----------------------------|---------------|----------|
| Indium Phosphide           | 9850          | Infrared |
| Gallium Arsenide           | 8980          | Infrared |
| Gallium Arsenide Phosphide | 6500          | Orange   |
| Gallium Phosphide          | 5650          | Green    |
| Gallium Nitride            | 4000          | Purple   |

b. Typical LEDs

Figure 3-21: LED light sources

Various LEDs, the materials used to make them, and the color of their light output are shown in *Figure 3-21b*. The wavelength in this case is given in Angstroms (Å), where an Angstrom is  $10^{-10}$  meters. When LEDs are used for light sources for phototransistors, the LED wavelength should be matched to the phototransistor. For example, *Figure 3-22* shows the relative output from a phototransistor using an LED as a source. An infrared LED with a wavelength of 898 nanometers (8980Å) provides almost three times as much output from the phototransistor as an LED with an orange light output of 650 nanometers (6500Å).

 


Figure 3-22: LEDs as light sources for a phototransistor sensor

### Example 5. Wavelengths of LEDs

What is the wavelength in meters of the LEDs whose wavelength is given in Angstroms (Å)?

**Solution:** (a millionth of a meter (micron) equals  $10,000\text{Å}$ )

| Å    | microns (divide by $10^4$ ) | meters (divide by $10^6$ ) | nanometers( $10^{-9}$ ) |
|------|-----------------------------|----------------------------|-------------------------|
| 9850 | 0.9850                      | $0.9850 \times 10^{-6}$    | 985                     |
| 8980 | 0.8980                      | $0.8980 \times 10^{-6}$    | 898                     |
| 6500 | 0.6500                      | $0.6500 \times 10^{-6}$    | 650                     |
| 5650 | 0.5650                      | $0.5650 \times 10^{-6}$    | 565                     |
| 4000 | 0.4000                      | $0.4000 \times 10^{-6}$    | 400                     |



## Other Sensors

The expansion of the types of sensors into modern day applications is almost mind boggling. The advent of micromachining using semiconductors and semiconductor fabrication techniques, and the ability to provide a sensor and its associated circuitry to signal condition the signal all in one package has expanded the types and variety of types of sensors. For example, in automotive and aircraft, there are sensors for mass air flow, exhaust gas and its properties, engine knock, linear acceleration, just to name a few. In fact, in the modern automobile there are over 100 sensors per car<sup>2</sup>. Such application explosions testify to the importance of the sensor in electronic circuitry.

## Summary

Sensors of all types have been described in this chapter. The devices that convert an analog physical quantity into forms of energy that humans can understand and interpret. The sensors in this chapter had outputs of electrical signals—voltage, current, resistance, capacitance. Because the output signals are going to be used in other electronic circuitry to provide signals that can be converted to digital signals, changes must be made to the sensor output signals to adapt them to further use. That is the subject of the next chapter—signal conditioning.

### Chapter 3 Quiz

1. A sensor:
  - a. senses an output quantity and inputs an electrical signal.
  - b. senses an output electrical signal and inputs a physical quantity.
  - c. senses an input quantity and outputs an electrical signal.
  - d. senses an output physical quantity and outputs a physical quantity.
2. Magnetic fields:
  - a. are not important to the operation of sensors.
  - b. play an important part in the operation of many sensors.
  - c. are harmful to the operation of sensors.
  - d. are generated by all sensors.
3. A thermocouple:
  - a. senses temperature.
  - b. senses voltage.
  - c. senses current.
  - d. senses impedance.
4. Silicon P-N junctions:
  - a. use the reverse voltage variations to sense current.
  - b. use both forward junction current variations for sensing voltage.
  - c. don't use the junction voltage variations to sense temperature.
  - d. use the forward voltage variations to sense temperature.
5. A thermistor:
  - a. is a sensor that varies temperature as voltage is applied.
  - b. is a sensor whose resistance varies with temperature.

---

<sup>2</sup> *Sensorsysteme für das Auto*, Klaus-Dieter Linsmeier, ©1999, verlage moderne industrie.



- c. is a sensor that has a linear variation with temperature.
  - d. is a sensor that varies temperature as current is applied.
6. In a Hall-effect sensor:
- a. a voltage is generated that is in the same direction as a current and a magnetic field.
  - b. a voltage is generated that has no relationship to the direction of an applied current or magnetic field.
  - c. a voltage is generated perpendicular to the direction of a current and perpendicular to the direction of a magnetic field.
  - d. needs only a magnetic field for its operation.
7. Semiconductors are particularly useful for Hall-effect sensors because:
- a. other circuits useful for processing the sensor signal can be built into the semiconductor.
  - b. they are isolated from the sensor.
  - c. they can be manufactured in one step.
  - d. there is no other way to make the sensor.
8. Hall-effect sensors can be used to sense:
- a. linear position.
  - b. angular position.
  - c. current.
  - d. all of above.
9. A variable reluctance sensor:
- a. has zero output when the magnetic field is not changing.
  - b. depends on time varying changes of a magnetic field.
  - c. has high output when the magnetic field is not changing.
  - d. doesn't need a magnetic field.
  - e. a and b above.
  - f. c and d above.
10. A magnetoresistor sensor:
- a. changes its resistance proportional to the magnetic field flux density to which it is exposed.
  - b. changes its voltage output as a result of a magnetic field.
  - c. changes its current output as a result of a magnetic field.
  - d. doesn't require a magnetic field.
11. Micromachined sensors:
- a. are processed with micro machines.
  - b. are machined using computer-controlled machines.
  - c. are processed using semiconductor manufacturing techniques.
  - d. don't need accurate machining techniques.
12. Micromachined sensors:
- a. measure pressure by applying a magnetic field.
  - b. measure pressure by changing resistance.
  - c. measure pressure by removing a magnetic field.
  - d. measure pressure by changing capacitance.
  - e. a and c above.
  - f. b and d above.
13. The photo diode:
- a. is not sensitive to any light.

- b. is a light sensor whose output does not vary with light intensity.
  - c. is a light sensor with a variable current output.
  - d. is a light sensor with a variable voltage output.
14. The light spectrum:
- a. is below 400 megahertz.
  - b. extends from infrared on the low end to ultraviolet on the high end.
  - c. is above 1,000 million megahertz.
  - d. is variable, not constant.
15. Wavelength:
- a. is the distance that an electromagnetic wave travels through space in one cycle of its frequency.
  - b. is not a distance but a speed.
  - c. is not a speed but a velocity.
  - d. is a measure of time.
16. A sensor that changes resistance when light is illuminates it is:
- a. photo current sensor.
  - b. photo voltage sensor.
  - c. photo impedance sensor.
  - d. photo resistor sensor.
17. Solar cells:
- a. are semiconductor PN junctions that are sensitive to light.
  - b. can be connected in parallel to increase current output.
  - c. can be connected in series to increase voltage output.
  - d. a above.
  - e. all of above.
18. A phototransistor, a light sensitive transistor:
- a. has normal base, collector, emitter connections.
  - b. has the base and collector connected together.
  - c. has no base connection.
  - d. has the base and emitter connected together.
19. Phototransistors:
- a. are most sensitive to infrared light.
  - b. are most sensitive to ultraviolet light.
  - c. are most sensitive to 100 MHz light.
  - d. are most sensitive to 10 MHz light.
20. LEDs (light emitting diodes) when used as light sources:
- a. may be used as random light sources for phototransistors.
  - b. should be matched to their phototransistor sensor.
  - c. are not important to phototransistor sensor applications.
  - d. are not reliable light sources.

20.b.

Answers: 1.c, 2.b, 3.a, 4.d, 5.b, 6.c, 7.a, 8.d, 9.e, 10.a, 11.c, 12.f, 13.c, 14.b, 15.a, 16.d, 17.e, 18.c, 19.a,

# Signal Conditioning

## Introduction

Signal conditioning, as the name implies, means modifying the signal, changing its characteristics, adjusting it to the needs of the application. This may mean an increase or decrease in the magnitude of the voltage signal, or an increase (or decrease) in the magnitude of the current signal, or a change in the ability of the signal to provide power. As shown in *Figure 4-1*, the signal conditioning function fits in two places in the chain from analog input to analog output. First, it is in the chain from sensor to the analog-to-digital conversion, second, it is in the chain from the digital-to-analog conversion to transducer. One of the most important electronic circuits to satisfy the signal conditioning function is the amplifier.

## Amplification

An electronic circuit called an amplifier is used when a voltage or current signal needs to be increased in amplitude. An amplifier can be a single circuit with a single active device (transistor), or it can be a combination of circuits with many active devices. Recall that in *Chapter 3*, *Figure 3-19a*, the bipolar NPN transistor operation was dis-

cussed, and in *Figure 3-19b*, the operation of a bipolar PNP transistor was discussed. There are also various types of field-effect transistors as shown in *Figure 4-2a*. These are called MOSFETs (metal-oxide semiconductor field-effect transistors). There are N-channel and P-channel devices that operate in the depletion mode or the enhancement mode. The characteristic curve of a field-effect transistor (FET) is shown in *Figure 4-2b*. A voltage from gate to source controls current from source to drain. Recall that for the bipolar transistors of *Figure 3-19*, a current into the base-emitter junction controls the collector-to-emitter current,

 


Figure 4-1: Signal conditioning function

 
 


Figure 4-2: MOS (metal-oxide semiconductor) field-effect transistor  
Courtesy of Master Publishing, Inc.

while for field-effect transistors, a *voltage* from gate to source controls the *current* from drain to source. To understand the operation of an amplifier and how it might be used, an amplifier will be designed, and its characteristics examined, using a single NPN bipolar transistor in a common-emitter circuit. Common-emitter means the input signal is applied between base and emitter, and the output signal is taken between collector and emitter. The emitter is a common point between the two.

## Bipolar NPN Amplifier


The design begins by choosing a device and looking at its characteristics shown in *Figure 4-3a*. The amplifier is going to be a “small-signal” linear amplifier. “Small-signal” means that the operating point will be set so that amplified output signals will be exactly the same as the input, with minimal distortion, but increased in amplitude. “Small-signal” means that the input signal amplitude only deviates the signal a small portion away from the steady-state operating point. As a result the amplification properties do not lose their linear qualities. The operating point—the no-signal steady-state operating point around which the small-signal ac signals vary—is chosen by some simple guidelines<sup>1</sup>.

1. The operating point should be within the linear portion of the characteristic curves.
2.  $V_{CE}$  should be approximately  $0.5V_{CC}$ .
3. Emitter-to-ground voltage should be 10% to 15% of  $V_{CC}$ .
4. Base-to-ground voltage will be approximately 0.7V greater than the emitter-to-ground voltage.

The amplifier is going to be used in automotive applications so the supply voltage,  $V_{CC}$ , will be equal to +12V. The operating point is going to be set at point A, the biased operating point shown on the characteristic curves of *Figure 4-3a*. When there is no signal, point A says that the collector current will be 6 mA and the  $V_{CE}$  (voltage from collector to emitter) will be 6V.

### Characteristic Curves

Look at the characteristic curves of *Figure 4-3a*. What do they mean? They were taken using the measuring circuit of *Figure 4-3c*. In this circuit, the base current,  $I_B$ , can be set to different values. The voltage  $V_{CE}$  can be varied, and the collector current,  $I_C$ , can be measured.  $I_B$  is set to 0.02 mA (20 microamperes) and  $V_{CE}$  is

 

**Figure 4-3: Point “A” is steady-state operating point set by bias**  
*Courtesy of Master Publishing, Inc.*

<sup>1</sup> *Basic Communications Electronics*, J.W. Hudson, G. Luecke, ©1999, Master Publishing, Inc., Lincolnwood, IL.

varied from 0 to 20V. The heavy-line characteristic curve marked  $I_B = 0.02 \text{ mA}$  is traced as  $I_C$  is measured during the variation of  $V_{CE}$ . As  $I_B$  is increased in 0.02mA steps and  $V_{CE}$  is varied, the other characteristic curves will be plotted.

The transistor will operate across these characteristic curves as driven by a signal that varies its base current and as regulated by the value of  $V_{CE}$ . At the operating point chosen (A),  $I_C = 6 \text{ mA}$  and  $I_B = 0.06 \text{ mA}$ , thus, as shown in *Figure 4-3b*, the steady-state common-emitter current gain ( $h_{FE}$ ) equals 100 at this point. Small  $I_B$  changes produce  $I_C$  changes that are 100 times greater. The current gain,  $h_{FE}$ , is called a large-signal or DC current gain. There is an AC current gain,  $h_{fe}$ , that is used for small-signal AC circuit analysis. It may vary from the  $h_{FE}$  value because the variation of  $I_B$  is in very small increments.

## Biasing

The operating point A is set at its operating characteristics by biasing the circuit. There are a number of biasing circuits: fixed-current  $I_B$  bias, voltage-divider bias, collector-feedback bias. This design will use voltage-divider bias. The circuit looks like the one in *Figure 4-4*. The resistor  $R_E$  is placed in the circuit to provide negative feedback. This feedback and its effect on circuit performance will be discussed when op amps and oscillators are discussed. For now, the presence of  $R_E$  in the circuit gives the circuit more stability against changes in temperature or parameter values.

## The Actual Design

Here are the design parameters that have been set:

$$V_{CC} = 12\text{V}$$

$$I_C = 6 \text{ mA}$$

$$h_{FE} = \text{The NPN transistor chosen has a specified minimum of 50; its actual } h_{FE} \text{ is 100.}$$

$$V_{BE} = 0.7\text{V for a silicon transistor}$$

$$V_E = 1.0\text{V (about 10\% of } V_{CC}\text{)}$$

$$V_{CE} = 6\text{V}$$

1. The first step is to solve for  $R_L$ :

Since  $V_{CE} = 6\text{V}$ ,

$$V_{CC} - I_C R_L = V_{CE}$$

$$12 - (6 \text{ mA} \times R_L) = 6\text{V}$$

therefore,

$$12 - 6 = 6 \text{ mA} \times R_L$$

$$\text{and } R_L = 6\text{V}/6 \text{ mA} = 6\text{V}/6 \times 10^{-3}$$

$$R_L = 1 \times 10^3 = 1000 \Omega = 1\text{k} \Omega$$

2. The next step is to solve for  $R_E$ :

Since in any transistor with reasonable gain,  $I_B$  is a small fraction of  $I_C$ , and since  $I_E = I_C + I_B$ , the approximation that  $I_E$  is equal to  $I_C$  is reasonably accurate.


Therefore,

$$V_E = R_E I_C$$

Therefore,

$$R_E = V_E / I_C$$

$$\text{or } R_E = 1\text{V}/6 \text{ mA} = 1\text{V}/6 \times 10^{-3} = 0.166 \times 10^3 = 166 \Omega$$

 

**Figure 4-4: NPN common-emitter small signal amplifier**

Resistors are manufactured in standard values of 150  $\Omega$  or 180  $\Omega$ . For this design  $R_E = 150 \Omega$ , and the actual  $V_E = 0.9V$  that is:  $(6 \times 10^{-3} \times 0.15 \times 10^3 = 0.9V)$ .

3. The next step is to solve for  $R_2$ :

One of the rules for voltage-divider bias is that the current,  $I_2$ , through the divider should be at least 10 times the maximum base current. The maximum base current,  $I_{B_{max}}$  is:

$$I_{B_{max}} = I_C / h_{FE(min)} = 6 \text{ mA} / 50 = 0.12 \text{ mA}$$

Thus,  $I_2 = 1.2 \text{ mA}$  and the value of  $R_2$  can be calculated since:

$$V_{R_2} = V_{BE} + V_E = 0.7V + 0.9V = 1.6V$$

and

$$R_2 = V_{R_2} / I_2 = 1.6V / 1.2mA = 1.33 \times 10^3 = 1330 \Omega$$

A standard value is 1300  $\Omega$ , so  $R_2 = 1.3 \text{ k}\Omega$

4. The next step is to solve for  $R_1$ :

$R_1$  in the voltage divider bias circuit will have the following current:

$$I_1 = I_2 + I_{B_{max}} = 1.2 \text{ mA} + 0.12 \text{ mA} = 1.32 \text{ mA}$$

Since  $V_{R_2} = 1.6V$ , the voltage across  $R_1$  is:

$$V_{R_1} = 12V - V_{R_2} = 12 - 1.6 = 10.4V$$

Therefore,

$$R_1 = V_{R_1} / I_1 = 10.4V / 1.32 \text{ mA} = 7.88 \times 10^3 = 7880 \Omega$$

8,200  $\Omega$  is a standard value, so  $R_1 = 8.2 \text{ k}\Omega$

The designed amplifier circuit using a 2N2222A transistor is shown in *Figure 4-5*. Its operating points are on the “load line” shown in *Figure 4-3a*.

5. The next step is to calculate the voltage gain.

The voltage gain<sup>2</sup> of the common-emitter amplifier circuit shown in *Figure 4-5* is:

$$A_v = (R_L \times I_E) / 0.026$$

where:  $R_L$  = total load resistance ( $R_L$  in parallel with any load across  $R_L$ )

$I_E$  = DC emitter current in mA.

$I_E = I_C$  (approximately)

Substituting in the equation:

$$A_v = (1 \times 10^3 \times 6 \times 10^{-3}) / 2.6 \times 10^{-2} = (6 \times 10^2) / 2.6 = 2.3 \times 10^2 = 230$$

The voltage gain in dB is:


$$DB = 20 \log_{10} A_v = 20 \log_{10} 230 = 20 \times 2.76 = 47.2 \text{ dB}$$

The voltage gain is 230 or 47.2 dB.

<sup>2</sup> Ibid.


## Amplifier Frequency Response

Not only must an amplifier amplify the voltage or current changes of an input signal, but it must be able to accurately reproduce these signals as the signal frequency changes. The capability of an amplifier to handle the signal over different frequencies is called its frequency response. An example of the frequency response of a common-emitter amplifier similar to the one in *Figure 4-5* is shown in *Figure 4-6*. It is a graph of an amplifier's gain,  $A_v$ , plotted against frequency with the input signal amplitude held constant as the signal frequency is varied. With the input signal amplitude constant, the output signal should remain constant if the gain,  $A_v$ , remains constant. The gain does remain constant in the midband as shown in *Figure 4-6*. However, for frequencies greater than  $f_H$ , the so called high-frequency corner frequency, the gain reduces as the signal frequency increases. This is due to circuit and device capacitance that is in parallel with  $R_L$ .  $A_v$  is reduced by 3 dB from its mid-band value at frequency  $f_H$ . The 3 dB point is also the frequency at which  $A_v$  has reduced to 0.707 of its midband value. For the amplifier in *Figure 4-6*,  $f_H$  is about 5 to 7 MHz.

 

**Figure 4-5: 2N2222A common-emitter small-signal amplifier**

When the amplifier is a DC amplifier, the midband value of  $A_v$  will extend down to zero frequency; however, if the amplifier only amplifies AC signals,  $A_v$  will reduce as the signal frequency is lowered below  $f_L$ , the low-frequency corner. Like  $f_H$ ,  $f_L$  is the frequency where  $A_v$  is  $-3$  dB (or 0.707) of its midband value. This reduction in gain is due to the coupling capacitors and capacitors across the emitter resistors used in AC amplifiers. For *Figure 4-6*,  $f_L$  is about 30 to 40 Hz.

 

**Figure 4-6: Common-emitter amplifier frequency response**

### Example 1. Corner Frequencies

Show that the  $-3$  dB point on a frequency response curve with a mid-band gain of 40 dB is the same point where the gain is 0.707 of the mid-band gain.

#### Solution:

Since the mid-band gain in dB is  $A_v = 20 \log_{10} V_O/V_{IN}$ , then

$$40 = 20 \log_{10} V_O/V_{IN}$$

$$2 = \log_{10} V_O/V_{IN}$$

$$10^2 = V_O/V_{IN}$$

$$100 = V_O/V_{IN}, \text{ the mid-band gain equals } 100$$

If the  $-3$  dB point is  $0.707 A_v$ , then the point is at  $A_v = 70.7$

$$\text{Therefore, } A_v = 20 \log_{10} 70.7$$

$$A_v = 20 \times 1.85$$

$$A_v = 37 \text{ dB}$$

37 dB is  $-3$  dB down from the mid-band gain of 40 dB.

For amplifier applications, it is very important to know the frequency range of the input signals that are to be handled and to examine the mid-band frequency range from  $f_L$  to  $f_H$  so that the proper amplifier can be used for an application.

## Coupling

### DC Coupling


When one circuit, such as the one in *Figure 4-5*, does not provide enough gain, circuits can be cascaded—coupled together—to provide more gain. The means of coupling are shown in *Figure 4-7*. *Figure 4-7a* shows a DC amplifier using two amplifier stages. The overall gain is equal to the first stage gain times the second stage gain. That is one advantage of expressing the amplifier gain in dB. The dB values of gain of each stage can be added to get the total gain in dB. The effect on frequency response is also shown. With DC coupling the amplifier has constant gain down to zero frequency. Special care must be taken in the design because the DC voltages couple from stage to stage so the proper operating voltages on the base, collector and emitter must be incorporated in the design.

### AC Coupling

*Figure 4-7b* is AC coupling. A capacitor,  $C_C$  is used to couple the signal from the first stage to the second stage. There also is a capacitor,  $C_E$ , that is used to bypass the emitter resistor of second stage. The coupling capacitor prevents the DC

voltages of stage 1 to couple through to stage 2, as they do in the DC case of *Figure 4-7a*. AC coupling allows the use of identical stages, makes the design easier, and even provides higher AC gain because the effect of the negative feedback of  $R_E$  is eliminated at frequencies above  $f_L$ . Below  $f_L$ , using  $R_E$  and  $C_C$  coupling causes a reduction in gain.

*Figure 4-7c* shows how inductance can be used to reduce the high-frequency response because of the increase in inductive reactance, and yet still maintain response at the low end down to zero frequency. *Figure 4-7d* shows transformer coupling. Transformer coupling provides DC isolation, but needs the AC time varying signal for its operation. The frequency response is like a capacitor-coupled amplifier.

 

**Figure 4-7: Types of coupling between amplifier stages**  
*Courtesy of Master Publishing, Inc.*



## Coupling Using Light

Figure 4-7e shows coupling using light. There is complete isolation between stage 1 and stage 2 using light coupling. The case shown uses a transistor to modulate the current through the LED, whose light emission is detected by a photo transistor. The light media can very easily be a fiber-optic cable.

When choosing an amplifier for an application, examine the transistor characteristic curves, know the type frequency response required and whether operation is required down to zero frequency, and determine if more than small-signal operation is needed.

### Example 2. Cascaded Gain

Show that an amplifier with three stages each with a gain of 20dB per stage has an overall gain of 1000.

#### Solution:

A gain of 20 dB is

$$20 \text{ dB} = 20 \log_{10} A_v$$

$$1 = \log_{10} A_v$$

$$A_v = 10$$

Three stages have overall gain of  $10 \times 10 \times 10 = 1000$ . It is interesting to note that the dB addition of  $20 + 20 + 20 = 60 \text{ dB}$  for the overall gain. Therefore,

$$60 = 20 \log_{10} A_v$$

$$3 = \log_{10} A_v$$

$$10^3 = A_v$$

$$1000 = A_v$$

## Small-Signal vs. Large Signal

Return to Figure 4-3a, the common-emitter characteristic curves for the NPN transistor. The straight line plotted on the characteristic curves is a “load line” for the  $1 \text{ k}\Omega$  load resistor used in the design of the amplifier stage of Figure 4-5. It represents the variation in collector voltage that occurs when collector current changes due to variations in base current. The operating point A is on the load line. If base current increases, the voltage drop across the  $1 \text{ k}\Omega$  load resistor increases and the collector voltage is decreased. If the collector voltage is reduced to zero, the transistor would be shorted, and the operating point would be at point C. If the collector current is zero, the transistor is cutoff, and the operating point is at B. The operating point A is the no-signal steady-state operating point. When an input signal is applied that varies the base current a small-signal increment of  $0.010 \text{ mA}$  each side of the operating point A, the changes in the collector current will be 100 times (minimum of 50) greater or  $1 \text{ mA}$ . The collector voltage will swing  $1 \text{ V}$  each side of the operating point A.

As shown in Figure 4-3a, an input signal is applied that varies  $I_B$  from  $0.04 \text{ mA}$  to  $0.08 \text{ mA}$ . The collector current varies from  $4 \text{ mA}$  to  $8 \text{ mA}$  as a result, and the collector voltage varies from  $4 \text{ V}$  to  $8 \text{ V}$ . There is a much larger output voltage swing, but the signal is still linear and not distorted. As the operation of the amplifier changes to a “large-signal” mode and more input base current change is supplied, the operating point on the load line runs into the nonlinear portion of the characteristic curves, point D, and distortion of the output waveform occurs. The distortion is shown in Figure 4-8. It is very important to the application, if linear operation is what is required, that the input signal does not drive the output of the amplifier into the distortion region.

 


Figure 4-8: Linear small-signal and large-signal, and large-signal distorted operation

The signal range from small-signal until distortion at the output occurs is called the *dynamic range* of the amplifier. Unless the circuit is designed to operate outside the linear region, make certain amplifiers have enough dynamic range for the application.

## Classes of Amplifiers

Figure 4-9 is the same sort of plot of characteristic curves as Figure 4-3a, but it defines the classes of amplifier circuits that can be designed. The operating points on the load line and the operating waveforms are shown. The small-signal amplifier of Figure 4-5 at point A is called a Class A amplifier because the operation is totally linear—exact reproduction of the input at the output.

A Class B amplifier operates at point B on the load line. It is linear when it operates, but it operates only for 180° of the input cycle. This is a very important class for power amplifiers—amplifiers that must supply large amounts of current and have, at the same time, significant voltage swings.

A Class AB amplifier, as shown in Figure 4-9, has an operating point on the load line that is between Class A and Class B. It is used to eliminate crossover distortion in linear power amplifiers and in tuned amplifiers for communications circuits.

A Class C amplifier operates on the load line at a point where the transistor is cutoff and must be driven into conduction by the input signal. As shown in Figure 4-9, collector current flows for only a small portion of an input cycle. Class C amplifiers are used extensively in resonant tuned circuit amplifiers to provide outputs over a narrow band of frequencies, usually radio frequencies and above.

## Field-Effect Transistor Amplifiers

Amplifiers are also designed using field-effect transistors. The symbols for MOS transistors were shown in Figure 4-2. There are also JFETs (junction field-effect transistors) that are made from semiconductor junctions rather than a layer of metal over oxide over silicon. They come in P-channel or N-channel devices operating in the depletion or enhancement mode. Depletion mode transistors have current from drain to source without any gate-to-source voltage; while enhancement mode transistors do not have any drain-to-source current unless a gate-to-source voltage is applied. Depletion mode JFETs are the most common type used for individual transistor amplifier stages. Most MOS transistors are enhancement mode devices.

## JFET Characteristic Curves

Figure 4-10 shows characteristic curves of a depletion mode N-channel. The changes in drain-to-source current,  $I_D$ , are plotted against drain-to-source voltage,  $V_{DS}$ , as the gate-to-source voltage,  $V_{GS}$ , is varied. The curves are developed the same way as the bipolar transistor curves of Figure 4-3; however, note that for these curves, that a change in *voltage* from gate to source causes the change in *current* from drain to source.

To design an amplifier, a load line is plotted on these characteristic curves just as for the bipolar transistor. Before the amplifier is designed several important points are noted. There is a gate-to-source voltage that is called the “pinch-off” voltage. It is the gate-to-source voltage that starts conduction of drain-to-source current for enhancement mode transistors, and it is the gate-to-source voltage that causes zero drain-to-source current in depletion mode devices. Anytime the drain-to-source voltage is above the gate-to-source voltage by the pinch-off voltage, the transistor is operating in the pinch-off mode. The pinch-off mode


 


Figure 4-9: Bias points of various classes of transistorized amplifiers Courtesy of Master Publishing, Inc.

 

a. Characteristic curves

Figure 4-10: An NPN JFET transistor (depleting mode)

means the channel within the field-effect transistor is pinched off and the drain-to-source current,  $I_{DS}$ , remains essentially constant for further large variations of drain-to-source voltage,  $V_{DS}$ . For depletion mode JFETs, when  $V_{GS}$  equals zero, the device will be operating at point X, and the drain current will be  $I_{DSS}$ . The pinch-off voltage and  $I_{DSS}$  are important parameters specified by FET manufacturers.

### A N-Channel JFET Amplifier Design

The JFET amplifier design is again for an automotive small-signal amplifier. The device is an N-channel transistor operating in the depletion mode and the supply voltage is +12V. The design begins by plotting a load line on the characteristic curves of Figure 4-10. The point A is chosen as the operating point because it is in a nice linear region. At point A,  $I_D = 4.6$  mA,  $V_{GS} = -1.5$  V and  $V_{DS} = 6.5$  V. The load line follows the equation:

$$I_D = V_{DD}/R_D - (1/R_D) \times V_{DS}$$


derived from  $V_{DS} = V_{DD} - I_D R_D$  as follows:

$$I_D R_D = V_{DD} - V_{DS}$$

$$I_D = V_{DD}/R_D - V_{DS}/R_D = V_{DD}/R_D - (1/R_D) \times V_{DS}$$

Substituting in the values for  $I_D$  and  $V_{DS}$ ,  $R_D = 1,196$  ohms.

TEAM LRN

 


b. Schematic symbols

| $V_{GS}$ | $V_{DS}$ | $I_D$  |
|----------|----------|--------|
| -1.75V   | 7.5      | 3.75mA |
| -1.25V   | 5.5      | 5.5mA  |
| 0.5V     | 2.0      | 1.75mA |

$\Delta$

$gm = \frac{1.75mA}{0.5V} = 3500\mu mhos$

c. Gain &amp; gm

 a. Choosing  $R_D$  at the operating point

b. Fixed bias

c. Self bias

d. Fixed and self bias

Figure 4-11: An NPN JFET amplifier design

The slope of the load line is  $1/R_D$ , and the circuit corresponds to *Figure 4-11a*.  $R_D$  is chosen as  $1.2\text{ k}\Omega$  and the load line plotted through point A. Easy end points for the load line are determined when  $I_D = 0$  then  $V_{DS} = V_{DD}$  or  $+12\text{V}$ , and when  $V_{DS} = 0$ ,  $I_D = V_{DD}/R_D$  or  $10\text{ mA}$ .

### Biasing the Circuit

*Figure 4-11* shows various ways of biasing the JFET at operating point A. A combination of fixed and self-bias shown in *Figure 4-11d* is chosen for the design. The self-bias requires that the value of  $R_S$  be calculated. It should be noted that with self-bias, the  $V_{DS}$  will be reduced by the amount of the voltage developed across  $R_S$ . Looking at the characteristic curves of *Figure 4-10*,  $I_D$  will not vary significantly if  $V_{DS}$  is reduced by several volts. The voltage across  $R_S$  is chosen to be  $+2\text{V}$ . With  $I_D = 4.6\text{ mA}$ , the value of  $R_S$  can be calculated as:

$$R_S = 2\text{V}/4.6\text{ mA} = 0.435 \times 10^3 = 435\ \Omega$$

A standard value of  $430\ \Omega$  will be used.

Because the  $V_{GS}$  voltage must be  $-1.5\text{V}$  and the source is at the voltage across  $R_S$ , which is  $+2\text{V}$ , the gate voltage must be  $+0.5\text{V}$ . This voltage is provided by the resistor divider of  $R_1$  and  $R_2$ . The input impedance of the JFET is very high so it will not load the resistor divider; therefore, the values of  $R_1$  and  $R_2$  can be quite high to reduce the power dissipation. The voltage across  $R_2$  is  $+0.5\text{V}$  and can be calculated as:

$$0.5\text{V} = R_2/(R_1 + R_2) \times V_{DD} = R_2/(R_1 + R_2) \times 12\text{V}$$

$$12R_2 = 0.5R_1 + 0.5R_2$$

$$11.5R_2 = 0.5R_1$$

Transposing,

$$R_1 = 11.5R_2/0.5$$

$$R_1 = 23\ R_2$$

The value of  $R_1$  is 23 times the value of  $R_2$ .  $R_2$  is chosen as a standard value of  $47\text{ k}\Omega$ , and as a result,  $R_1$  equals  $1.1\text{ M}\Omega$ . The completed design is shown in *Figure 4-12*. As noted in *Figure 4-10c*, for a  $0.5\text{V}$  change in  $V_{GS}$ , there is a  $2.0\text{V}$  change in  $V_{DS}$  and a  $1.75\text{ mA}$  change in  $I_{DS}$  current. The amplifier has a voltage gain of 4.

### Example 3. Calculating Ratio of $R_2 : R_1$

In *Figure 4-11b*, if  $V_{DD} = +10\text{V}$  and  $-V = -10\text{V}$ , what ratio of  $R_2 : R_1$  should be used to obtain a  $V_{GS} = -1.5\text{V}$ ?

#### Solution:

Since  $V_{DD} = +10\text{V}$  and  $-V = -10\text{V}$  and  $V_{GS} = -1.5\text{V}$ , then the voltage across  $R_2$  is:

$$8.5 = R_2/(R_1 + R_2) \times 20\text{V}$$

$$8.5R_1 + 8.5R_2 = 20R_2$$

$$8.5R_2 = 11.5R_1$$

$$R_2/R_1 = 8.5/11.5 = 0.74$$

### G<sub>m</sub>—Transconductance

There is a parameter,  $g_m$ , for field-effect transistors called transconductance. It is defined as the change in drain-to-source *current* in amperes per *volt* of change in the gate-to-source voltage. It is a change in current,  $\Delta I$ , over a change in voltage,  $\Delta V$ ; or the inverse of resistance. Thus, transconductance has the units of mhos, rather than ohms. For the amplifier of *Figure 4-12*, as shown in *Figure 4-10c*, there is a  $1.75\text{ mA}$  change in drain current for a  $0.5\text{V}$  change in gate-to-source voltage. This is a  $3.5\text{ mA}$  per volt change or  $3500\text{ micromhos}$  for  $g_m$ .

 


Figure 4-12: Completed NPN JFET small-signal amplifier

The voltage gain of an amplifier can be expressed as:

$$A_v = -g_m R_L$$

Accordingly, the gain of the amplifier of *Figure 4-12* is:


$$A_v = 3500 \times 10^{-6} \times 1.2 \times 10^3 = 4200 \times 10^{-3} = 4.2$$

This matches the value computed from *Figure 4-10*. Examining the equation  $A_v = -g_m R_L$ , one can see that the gain can be increased by increasing  $R_L$ . To do this one would need to increase  $V_{DD}$ . Of course, if  $g_m$  is higher the gain is higher. Thus, devices are judged for amplifiers by their  $g_m$ . *Figure 4-2b* shows an easy way to evaluate  $g_m$ , it is the slope of a line tangent to  $I_{DS}$  vs  $V_{GS}$  curve.
 
## An NPN MOSFET Amplifier

The same characteristic curves shown in *Figure 4-10* apply to an enhancement mode N-channel MOSFET with a couple of exceptions. The gate-to-source voltages are positive and equal to and greater than the threshold voltage,  $V_t$ .  $V_t$  is required to start the channel current from drain to source in the enhancement mode. The characteristic curve that plots on the  $V_{DS}$  axis has  $V_{GS} = V_t$  and any additional curves have  $V_{GS} = V_t + V$ . The characteristic curves represent the full  $V_{GS}$  voltage, but only the  $V$  value above  $V_t$  is contributing to enhancing the channel current.

The characteristic curves for the N-channel MOSFET are shown in *Figure 4-13*. The transistor will be used in the enhancement mode to design a small-signal amplifier similar to the JFET amplifier. Again, the amplifier will be used in an automotive application so the power supply voltage is +12V. The operating point is set as point A, again in the linear region. At point A,  $V_{DS} = 8V$ ,  $I_{DS} = 3.3 \text{ mA}$ ,  $V_{GS} = 6V$  and  $V_t = 2V$ . The dotted parabolic curve is the locus of points where  $V_{DS} = V$ , the component of  $V_{GS}$  above  $V_t$ . The points on the  $V_{GS}$  curves where the  $V_{DS}$  curve intersects are the points where the channel goes into pinch off. Operation to the right of the dotted-line curve is in pinch off; operation to the left is in the triode region. Small-signal linear amplifiers must operate in the pinch-off region. The load line is plotted for  $R_L = 1.2 \text{ k}\Omega$  just like the JFET design.



a. Characteristic curve

| Point A         | $V_t = 2V$ | $R_L = 1.2K$ |                                                            | Point B        | $V_t = 2V$ | $R_L = 2K$ |                                                              |
|-----------------|------------|--------------|------------------------------------------------------------|----------------|------------|------------|--------------------------------------------------------------|
| $V_{GS}$        | $I_{DS}$   | $V_{DS}$     | $g_m = \frac{3 \text{ mA}}{2V}$<br>$= 1500 \mu\text{mhos}$ | $V_{GS}$       | $I_{DS}$   | $V_{DS}$   | $g_m = \frac{4.5 \text{ mA}}{2V}$<br>$= 2250 \mu\text{mhos}$ |
| $V_t + 5V = 7V$ | 5.5 mA     | 5.5V         |                                                            | $V_t + 4 = 6V$ | 3.5 mA     | 17.0V      |                                                              |
| $V_t + 4V = 6V$ | 3.3 mA     | 8.0V         |                                                            | $V_t + 5 = 7V$ | 5.5 mA     | 13V        |                                                              |
| $V_t + 3V = 5V$ | 2.5 mA     | 9.0V         |                                                            | $V_t + 6 = 8V$ | 8 mA       | 8V         |                                                              |
| $\Delta = 2V$   | 3 mA       | 3.5V         |                                                            | $\Delta = 2V$  | 4.5 mA     | 9.5V       |                                                              |

b. Gain and  $g_m$

Figure 4-13: An N-channel enhancement-mode MOSFET  
TEAM LRN

## Fixed and Self-Bias

The MOSFET N-channel can be biased, as shown in *Figure 4-14a*, just like the JFET. The  $V_{DS}$  voltage is somewhat larger because the steady-state  $V_s$  can be much smaller due to the fact that all  $V_{GS}$  voltages are positive. In *Figure 4-14a*,  $R_L = 1.2 \text{ k}\Omega$  and  $I_{DS} = 3.3 \text{ mA}$ ; therefore, since  $I_s = I_D$ ,

$$R_s = 0.5\text{V}/3.3 \text{ mA} = 0.152 \times 10^3 = 152 \Omega$$

A standard value is  $150 \Omega$  so  $R_s = 150 \Omega$ .

To have  $V_{GS} = 6\text{V}$ , the gate must be at  $+6.5\text{V}$  since the source is at  $+0.5\text{V}$ ; therefore,

$$\begin{aligned} R_2/(R_1 + R_2) \times 12\text{V} &= 6.5\text{V} \\ 6.5R_1 &= (12 - 6.5)/6.5 \times R_2 \\ R_1 &= 0.846 R_2 \end{aligned}$$

$R_2$  is chosen as a standard value of  $470 \text{ k}\Omega$ , which results in a standard value of  $390 \text{ k}\Omega$  for  $R_1$ . The designed stage is shown in *Figure 4-14a*.

## Drain-to-Gate Bias

Another biasing arrangement that also provides negative feedback is shown in *Figure 4-14b*. In this arrangement, since gate current is zero,  $V_{DS} = V_{GS}$ , and a small increase in drain current causes a small reduction in  $V_{DS}$ . The small reduction in  $V_{DS}$  is fed back to cause a small reduction in  $V_{GS}$ , which compensates for the original increase in drain current. Now, since

$$V_{DS} = V_{GS} - V_t$$

It follows that adding a  $V_t$  voltage to  $V_{DS}$ ,

$$V_{DS} = V_{GS} - V_t + V_t = V_{GS}$$

As a result, a new parabolic locus of points is drawn on the characteristic curves that represents  $V_{DS} = V_{GS}$ , as shown in *Figure 4-13a*. In other words, the curve is displaced to the right by the value of  $V_t = 2\text{V}$ . Because of this, the operating point shifts to point C on the load line, and  $I_{DS} = 4.33 \text{ mA}$  and  $V_{GS} = V_{DS} = 6.8\text{V}$ .

## Gain and $g_m$

*Figure 4-13b* provides some large-signal voltage gain and  $g_m$  values for the circuit of *Figure 4-14a*. The voltage gain is  $1.75\text{V}$  per  $\text{V}$  and  $g_m$  is  $1500$  micromhos. Calculating the gain by using  $-g_m R_L$ , the voltage gain is

$$A_v = -1500 \times 10^{-6} \times 1.2 \times 10^3 = -1.8$$

The minus sign, of course, meaning a change in phase of the signal. It was pointed out for the amplifier of *Figure 4-12* that using a larger load resistor would increase the stage voltage gain. A new load line using a  $2 \text{ k}\Omega$  resistor is drawn on the characteristic curves of *Figure 4-13*. The operating point is now point B and  $A_v = 4.25\text{V}$  per  $\text{V}$ ,  $g_m = 2250$  micromhos and  $-g_m R_L = 2250 \times 10^{-6} \times 2 \times 10^3 = 4.25$ . The concern with this design is the increased power supply voltage to  $+24\text{V}$  and increased power dissipation when the operating point is point B where  $I_{DS} = 5.5 \text{ mA}$  and  $V_{DS} = +13\text{V}$ .

 


Figure 4-14: N-channel MOSFET small-signal amplifiers  
TEAM LRN

## Operational Amplifiers

Integrated circuit manufacturers have provided an excellent product—the operational amplifier (op amp)—to designers of electronic circuits for signal conditioning sensor signals. Many types and varieties are available for a wide spectrum of applications. System designers that need amplification in their design need not design an individual amplifier circuit but can use an op amp instead.

The term “op amp” refers to a direct-coupled amplifier that was used initially in analog computers to perform mathematical computations, while solving real-time control system problems. Op amps are DC amplifiers that have high gain, high input impedance, low output impedance, and wide bandwidth. Another significant advantage is that the amplifier’s characteristics can be varied using external components.

Figure 4-15 describes a general-purpose op amp. The amplifier has two inputs and one output. The amplifier output is normally a linear output voltage,  $V_O$ , that is proportional to the difference of the voltage between the two inputs. Thus, it is classified as a differential amplifier. The two inputs

 


Figure 4-15: General-purpose operational amplifier

are identified with a minus and a plus sign. The input with the *minus sign* is called the *inverting input*; the input with the *plus sign* is the *noninverting input*. If the noninverting input is more positive than the inverting input, the output voltage,  $V_O$ , is positive with respect to ground. Conversely, if the inverting input is more positive than the noninverting input,  $V_O$  will be negative with respect to ground. When both inputs are referenced to ground, and the inverting input is more positive,  $V_O$  swings negative; when the non-inverting input is more positive,  $V_O$  swings positive.

### Characteristics

Return to Figure 4-15. The output,  $V_O$ , can be represented by a generator,  $E_O = A_{VD} \times V_D$ , fed to the output through the output impedance,  $Z_O$ .  $E_O$  is the input differential signal,  $V_D$ , amplified by the open-loop differential gain,  $A_{VD}$ .  $Z_{IN}$  is the input impedance, and  $V_{IO}$  is the input offset voltage that causes the output voltage to be displaced from zero volts when there is no differential input signal.  $A_{VD}$  is usually a very large number ( $>20,000$ ) in most modern day op amps; therefore, even a very small input signal drives the output into saturation. This is a distorted output as shown previously in Figure 4-8. As a result, normal operation is with feedback from output to input to set the gain of the op amp at a particular value.

### Setting Gain

Look at Figure 4-16. A resistor,  $R_f$ , is connected from the output back to the inverting input to control the gain of the op amp with negative feedback.

 


Figure 4-16: Op amp with negative feedback and signal to inverting input

If the output goes positive, as it would for an input signal on A going negative, a portion of the positive output signal is fed back to the input to cancel part of the input signal. In *Figure 4-16*, the ideal op amp characteristics are listed. One of these is  $Z_{IN} = \text{infinity}$ . As a result,  $I_{IN} = 0$ ; therefore, from *Figure 4-16*,

$$I_i + I_f = 0$$

Since

$$I_i = (V_{IN} - V_D)/R_i \text{ and since } V_D = 0 \text{ because } I_{IN} = 0, \text{ then}$$

$$I_i = V_{IN}/R_i$$

and  $I_f = V_O/R_f$  because  $V_D = 0$ , then

$$V_{IN}/R_i + V_O/R_f = 0$$

$$V_O/R_f = -V_{IN}/R_i$$

and  $V_O/V_{IN} = -R_f/R_i$

or  $A_{Vf} = -R_f/R_i$

The gain of the inverting operational amplifier with feedback,  $A_{Vf}$ , is determined by the ratio  $R_f/R_i$ , both external components to the amplifier itself.

In *Figure 4-17*,  $V_{IN}$  is applied to the noninverting input; therefore,

$$V_{R1} = V_{IN} - V_O, \text{ but because } V_O = 0 \text{ since } I_{IN} = 0,$$

$$V_{R1} = V_{IN}$$

Therefore,

$$I_i = V_{IN}/R_i$$

Since,

$$I_i + I_f = 0, \quad I_f = I_i$$

Now,

$$V_O = V_{R1} + V_{Rf} = V_{R1} + I_f R_f$$

Now, with substitution for  $V_{R1}$  and  $I_f$ ,

$$V_O = V_{IN} + I_i R_f$$

Therefore, since  $I_i = V_{IN}/R_i$

$$V_O = V_{IN} + (V_{IN}/R_i) \times R_f$$

$$V_O = V_{IN} (1 + R_f/R_i)$$

Or  $V_O/V_{IN} = 1 + R_f/R_i$

And thus,  $A_{Vf} = 1 + R_f/R_i$

The feedback gain,  $A_{Vf}$ , for an op amp with the signal on the noninverting input is one plus the feedback gain of an op amp with the signal on the inverting input. The output is out of phase for the inverting input and in phase for the noninverting input.

In summary,

For inverting input:  $A_{Vf} = -R_f/R_i$

For noninverting input:  $A_{Vf} = 1 + R_f/R_i$

Even though the manufactured op amps are not ideal, the parameters are such that making the ideal amplifier assumptions cause very small errors (<0.5%). The above equations, when used for amplifier designs, will provide circuit performance that is well within the accuracy of other components used.



**Example 4. Calculating Op Amp Gain**


Calculate the op amp gain indicated using the values of  $R_f$  and  $R_i$  as shown.

**Solution:**

| $R_f$          | $R_i$          | Inverting                                  | Noninverting |
|----------------|----------------|--------------------------------------------|--------------|
| 1 M $\Omega$   | 10 k $\Omega$  | $1 \times 10^6 / 10 \times 10^3 = 100$     | 101          |
| 870 k $\Omega$ | 56 k $\Omega$  | $870 \times 10^3 / 56 \times 10^3 = 15.5$  | 16.5         |
| 330 k $\Omega$ | 4.7 k $\Omega$ | $330 \times 10^3 / 4.7 \times 10^3 = 70.2$ | 71.2         |
| 100 k $\Omega$ | 3.3 k $\Omega$ | $100 \times 10^3 / 3.3 \times 10^3 = 30.3$ | 31.3         |

**Op-Amp Power Supplies**

Notice that in *Figure 4-16* and *Figure 4-17* there are no power supply connections. They were omitted for clarity. Most op amps operate from plus and minus power supplies, but many manufacturers now have units that operate from a single supply. Units that operate from dual power supplies, use plus and minus voltages of equal value. The manufacturers recommend operating voltages, but most operate over a range of supply voltages. Parameters are tested for guaranteed values shown on data sheets at a particular power supply voltage.

 


**Figure 4-17: Op amp with negative feedback and signal to noninverting input**


$$\frac{V_O}{V_{IN}} = A_{VF} = 1 + \frac{R_f}{R_i}$$

**Op-Amp Offset Correction**

Many op amps in the past provided external package pins to aid in adjusting the amplifier output voltage for any offset voltage that might cause the output voltage to be other than zero when the input voltage is zero. The package pins are shown in *Figure 4-18*. Pin #1 and pin #5 are used to inject a current into the input stage and adjust  $V_O$  to zero when  $V_{IN}$  is zero. A high-value variable resistance is placed across the pins and the variable contact is fed by a current source. The resistance is adjusted until the output voltage is zero.

 

**Figure 4-18: Op amp with offset adjustment and frequency compensation**

 

**Figure 4-19: Frequency response of general purpose op amp**

**Frequency Response**

*Figure 4-19* shows the typical frequency response of a general-purpose op amp like the 741. The maximum open-loop gain of 200,000 is from DC to about 20 Hz and then the gain declines on a straight line until the gain equals 1. For this case,  $R_f$  is infinity so the feedback loop is open. When feedback is added, the gain is reduced and the gain vs. frequency curve fits under the open-loop gain response curve. For example, if feedback is added so the amplifier has a gain of 40—shown by the dotted line in *Figure 4-19*—then the frequency response is flat out to 100 kHz before it starts to roll off. If the gain is reduced to 4, the frequency response stays flat until 1 MHz before it starts to roll off.

The phase shift of the output signal is also shown in *Figure 4-19*. If the amplifier gain were greater than 1 at any frequency and the phase shift were greater than  $180^\circ$ , the amplifier circuit would oscillate at that frequency. One of the parameters where commercial op amps definitely deviate from the ideal specifications is in the bandwidth. Available op amps are definitely limited to a finite bandwidth.

### Frequency Compensation

Frequency compensation is the act of adding external components to stabilize the op amp and keep it from oscillating. Some op amps provide pin connections to which external capacitance can be connected to stabilize the op amp. This feature is shown for the package of *Figure 4-18*. Capacitance is added across the pins marked “compensation.” When the application demands more and more frequency response and higher frequency operation, more attention must be paid to circuit layout and lead lengths to keep the op amp from oscillating. For this reason, op amps with external connection pins for compensation may be a necessity.

### Conditioning the Output of a Pressure Sensor

It is necessary to amplify the output signal from a pressure sensor in order to have a voltage great enough to input it to an analog-to-digital converter. In *Chapter 3*, the construction of a pressure sensor was shown in *Figure 3-12*. Such a sensor is connected to an op amp in *Figure 4-20* that is acting as a difference amplifier. It is amplifying the difference voltage  $V_2 - V_1$  identified as  $V_{IN}$  in *Figure 4-20*. There are specific requirements for the op amp to be a difference amplifier. The ratio  $R_3/R_2$  must be equal to the ratio  $R_f/R_1$ .  $R_f/R_1$  determines the differential gain. With  $R_f/R_1$  equal to 20 for the circuit,  $R_3/R_2$  must be 20.  $R_2$  is  $2\text{ k}\Omega$ ; therefore,  $R_3$  is  $40\text{ k}\Omega$ . The reason that  $R_2$  is  $2\text{ k}\Omega$  is to have the input impedance to the sensing circuit, which is  $R_1 + R_2$ , as high as possible to keep from loading the pressure gauge bridge and causing inaccuracies.  $R_1$  tends to be small to allow the gain to be high, but this keeps the input impedance low, which would load the circuit. There is a compromise here.

The signal from the sensor is normally in millivolts (mV), and the input to the analog-to-digital converter needs to be 1V or more. If the input voltage is  $2\text{ mV}$  and the difference amplifier has a gain of 20, the output voltage will be  $V_O = 20 \times 2 \times 10^{-3} = 40\text{ mV}$ . More amplification is needed. Another op amp with the signal fed to the noninverting input is added with a gain of 41. Its output voltage will be  $V_O = 41 \times 40 \times 10^{-3} = 1.64\text{V}$ . Op amps are manufactured with dual circuits in a package; therefore, only one IC is used. The power supply voltages (plus and minus) are chosen for the convenience of the application. There are many op amps that operate from 3–4 volts to 20 volts.

### Common-Mode Rejection

One problem with instrumentation amplifier circuits such as *Figure 4-20* is that the signal output from the sensor is very small, but the noise voltage picked up on the leads connecting the sensor to the amplifier may be 100 to 1000 times greater.

 


Figure 4-20: Amplifying a pressure-sensor output  
TEAM LRN

An op amp with a high common-mode rejection must be chosen for such applications. Common-mode rejection means that any signal appearing on both inputs at the same time will not appear at the output. Only the differential signals will be amplified. Common-mode rejection ratio is:

$$\text{CMRR} = A_{VD}/A_{CM}$$

where  $A_{VD}$  is the differential gain and  $A_{CM}$  the common-mode gain. In decibels,

$$\text{CMRR}_{\text{dB}} = 20\log_{10} A_{VD}/A_{CM}$$

### Example 5. Common-Mode Rejection

If an op amp has an  $A_{VD} = 100$  dB and a  $\text{CMRR} = 80$  dB, what is the common-mode gain?

**Solution:**

$$\text{CMRR}_{\text{dB}} = 20\log_{10} A_{VD}/A_{CM}$$

$$80 = 20\log_{10} A_{VD}/A_{CM}$$

$$4 = \log_{10} A_{VD}/A_{CM}$$

$$10^4 = A_{VD}/A_{CM}$$

$$A_{CM} = A_{VD}/10^4$$

therefore,

$$A_{VD\text{dB}} = 20\log_{10} V_O/V_{IN}$$

$$100 = 20\log_{10} V_O/V_{IN}$$

$$5 = \log_{10} V_O/V_{IN}$$

$$10^5 = V_O/V_{IN} = A_{VD}$$

$$A_{CM} = 10^5/10^4 = 10$$

### A More Sophisticated Pressure Sensor Amplifier

Burr-Brown, manufacturers of op amps, in one of their application notes<sup>3</sup>, present a much more sophisticated pressure sensor circuit. It is shown in Figure 4-21. It is presented here to demonstrate several other uses of op amps that are very important to signal conditioning circuitry, and, in addition, the circuit is designed using only one power supply. The circuit uses four op amps, two in each package. In the circuit,  $A_3$  and  $A_4$  constitute a two-op-amp instrumentation amplifier whose output voltage is:

$$V_{\text{OUT}} = V_{\text{IN}}(2(1 + R/R_T)) + V_{\text{OUT1}}$$

$V_{\text{OUT1}}$  is the offset voltage at the output when  $V_{\text{IN}} = 0$ , or when there is zero pressure on the sensor. For the circuit shown, because the design required an output from the instrumentation amplifier when the input voltage was zero,  $V_{\text{OUT1}}$  was set at +0.5V.

 


Figure 4-21: A more sophisticated pressure-sensor amplifier

<sup>3</sup> Burr-Brown, AB-033A Application Note, © 1991, Burr-Brown Corporation.

## Voltage Follower

The +0.5V is set using what is called a voltage follower. The op amp  $A_2$  is a non-inverting amplifier with  $R_f = 0$  and  $R_1$  equal to infinity; therefore, its gain,  $A_{VD}$  is:

$$A_{VD} = 1 + R_f/R_1 = 1$$

and  $V_O = V_{IN}$

It is a unity gain amplifier, and its configuration is as shown in Figure 4-22. Its output voltage equals its input voltage, thus, the name voltage follower. It has a very high input impedance and a low output impedance so it isolates output from input. It has +0.5V applied to its noninverting input so it produces +0.5V at its output.

 


Figure 4-22: Unity gain amplifier or voltage follower

The  $A_1$  op amp is a similar stage but has a finite gain set by  $R_f = 5.8 \text{ k}\Omega$  and  $R_1 = 1 \text{ k}\Omega$ , so that its gain is:

$$A_{VD} = 1 + 5.8 = 6.8$$

It also has +0.5V on its noninverting input, so that it produces an output voltage of  $6.8 \times 0.5 = 3.4\text{V}$ . This output voltage is used as a reference voltage for the bridge sensor and will remain very stable. Op amps make excellent voltage followers and produce outputs that are isolated from the inputs because of the high input impedance and low output impedance. They do not have to be unity gain amplifiers.


The component called REF200 in the circuit is one half of a dual constant-current source. It supplies a constant current of  $100 \mu\text{A}$ . A constant-current source can be a high resistance connected to a power supply; however, REF200 is made up of active devices that produces a very accurate, stable source of  $100 \mu\text{A}$ . The  $100 \mu\text{A}$  through a precision  $5 \text{ k}\Omega$  resistor produces a very accurate +0.5V required for the circuit.

The gain of the  $A_3$  and  $A_4$  op amps, as stated previously, is two times the gain of a noninverting amplifier; therefore, with  $R_T = 85 \Omega$  and  $R = 10 \text{ k}\Omega$

$$A_{VD} = 2 (1 + 10 \times 10^3)/85 = 2(1 + 118) = 238$$
 
## Current Mirror

One other circuit that is useful for signal conditioning is a current mirror shown in Figure 4-23. It can be made using MOS or bipolar transistors, and there are more elaborate circuits than those shown in Figure 4-23. In each of these circuits, the output current is equal to a constant factor times the input current. When transistors are made in integrated circuit form and used for current mirrors, they are next to each other, and, therefore, have identical characteristics.



a. MOS circuit

b. Bipolar circuit

Figure 4-23: Current mirrors

As a result, the current mirrors produce very accurate outputs vs. inputs. They are used to supply accurate currents in themselves or to establish accurate voltage references by developing a voltage across precision resistors. The output current for the MOS transistors turns out to be the input current times the ratio of the channel width,  $W$ , to the channel length,  $L$ , of the MOS transistors used in the design.

### Example 6. $W/L$ Ratio of Current Mirrors

In Figure 4-23a, if  $I_1 = 50 \mu\text{A}$  and  $(W/L)_2 = 4$  and  $(W/L)_1 = 2$ , what is the value of  $I_O$  for the current mirror?

**Solution:**

$$I_O = I_1 (W/L)_2 / (W/L)_1 \quad \text{where } W \text{ is channel width and } L \text{ channel length}$$

$$I_O = 50 \mu\text{A} \times 4/2 = 100 \mu\text{A} \quad \text{for the MOS transistors used in the design.}$$


## Applications of Op Amps

### Thermocouple Amplifiers

Figure 4-24a shows an amplifier for use with a thermocouple. The thermocouple is connected to the non-inverting input. A  $1 \text{ M}\Omega$  variable resistor is used for  $R_f$  so that the gain and sensitivity can be adjusted to the requirements of the application. Short lead lengths and bypass capacitors on the power supply leads may be required at the highest gain settings.

### Solar Cell or Photodiode Amplifier

Figure 4-24b is an amplifier for use with a photodiode or a solar cell. Again the gain is adjustable to fit the application. Short lead lengths and component placement are important in both of these applications to make sure the circuit does not oscillate.

 

### Thermistor Amplifier

Figure 4-24c is an amplifier to use with a thermistor temperature sensor. Beside a gain adjustment, there is a level adjustment to set the output at a particular temperature.  $25^\circ\text{C}$  might be the temperature for many applications.

 


Figure 4-24: Sensor amplifiers using op amps

Recall that with an op amp, as shown in Figure 4-25b,

when a signal,  $v_i$ , is applied to the noninverting input that the output,  $v_o$ , is in phase with the input signal. If now the output is fed back to the noninverting input through a feedback circuit, as shown by the dotted box,

the output signal reinforces the input and the circuit is turned into an oscillator. An oscillator is a circuit that outputs a continuous signal, usually at a constant frequency, with  $v_i = 0$ . In other words, the oscillator puts out a continuous signal without having an input. In Figure 4-25,  $\beta$  is the gain of the feedback network shown in dotted lines. It either increases or decreases  $v_o$  as it feeds back the signal from output to input; therefore,

$$v_i = \beta v_o$$

Since  $v_i = 0$ ,  $v_i$  when amplified by  $A_v$  produces  $v_o$ , and

$$v_o = A_v \beta v_o$$

or, cancelling out  $v_o$ ,

$$A_v \beta = 1$$

The oscillator will maintain an output signal without an input signal when the loop gain is equal to or greater than 1 and will oscillate at a frequency where the phase from input back to input is  $360^\circ$ .

It so happens, when many amplifiers are built, not enough precaution is taken with component layout so that part of the output signal is fed back to the input. The circuit oscillates at a sine-wave frequency where the loop gain is greater than 1 and the phase shift through the feedback loop is  $180^\circ$  or greater. This assumes that the phase shift through the amplifier stage is  $180^\circ$ . There are many types of oscillators that output waveforms other than sine-waves—square-wave, triangular waves, pulses of constant width, or pulses that vary in width, but the principle is the same—the phase shift from input to output to input is  $360^\circ$ , and the gain is greater than 1 through the feedback loop.

## Power Amplifiers

### Class A Amplifiers

The small-signal amplifiers that have been discussed are Class A amplifiers—there is current in the transistors, as discussed in Figure 4-9, for  $360^\circ$  of the signal cycle. When Class A amplifiers are used for power amplifiers, where high current and high voltage swings are required at the same time, there is a large amount of power dissipated in the amplifier stage itself rather than being delivered to the load. The efficiency of power transfer to the load is low. The maximum efficiency is 25%, but in practical applications it usually is only 10% to 20%. As a result, Class AB, Class B and Class C amplifiers are used for power amplifiers. Because current in Class C amplifiers flows only for a small portion of an input signal cycle, current pulses are applied to a tuned circuit load resonant at a particular frequency, or over a narrow band of frequencies. Thus, Class C amplifiers are used for frequency-selective power amplifiers, and most applications of power amplifier circuits in this book will use Class AB or Class B amplifiers.

### Class B

Figure 4-26a is the circuit for a simple complementary bipolar transistor power amplifier.  $Q_1$  is a NPN power transistor whose collector is connected to  $+V_{CC}$ .  $Q_2$  is a PNP power transistor whose collector is connected to  $-V_{CC}$ . The bases of the two transistors are connected together to  $V_i$ , the input voltage. When  $V_i = 0$ , both transistors are off and there is no current through  $R_L$ , the load, so  $V_o = 0$ . As  $V_i$  increases positively, when  $V_{BEQ1}$  is exceeded,  $Q_1$  conducts and becomes an emitter-follower with a voltage gain of 1.

 


Figure 4-25: An oscillator

$V_O = V_i - V_{BEQ1}$  results as shown in the transfer characteristics of Figure 4-26b. As  $V_i$  returns to zero and increases negatively, when  $V_{BEQ2}$  is exceeded,  $Q_2$  conducts and it becomes an emitter-follower.  $V_O = -(V_i - V_{BEQ2})$  as shown in the transfer characteristics of Figure 4-26b.

 


Figure 4-26: Simple complementary bipolar transistor Class B power amplifier

$Q_2$  is cutoff while  $Q_1$  conducts;  $Q_1$  is cutoff while  $Q_2$  conducts. There is no voltage gain but significant current gain to provide the power amplification. Each transistor is biased Class B with conduction only over  $180^\circ$  of the input signal cycle. Note, however, as shown in Figure 4-26b, that there is quite a bit of distortion, called crossover distortion, especially when the signal amplitude is small.

Figure 4-27 shows a Class B complementary transistor power amplifier that has the crossover distortion eliminated. It is eliminated because the transistors are operating in Class AB where each has a small quiescent current through it.  $I_1$  is the current through  $Q_1$  and  $I_2$  is the current through  $Q_2$  when  $V_i = 0$ . A biasing resistor,  $R_1$ , supplies a bias current to the diodes  $D_1$  and  $D_2$  to provide a two-diode constant voltage between the bases of  $Q_1$  and  $Q_2$ .  $Q_1$  and  $Q_2$  are matched to have the same  $V_{BE}$ . As a result,  $I_1 = I_2$ .

When the diode voltage drop is matched to the  $V_{BE}$  of  $Q_1$  and  $Q_2$ , point A in the circuit of Figure 4-27a will be at  $V_{BE}$ , point B will be at  $2V_{BE}$  and point C will be at the same voltage as point A,  $V_{BE}$ . Figure 4-27b shows the transfer characteristics. When  $V_i = 0$ ,  $V_O = V_{BE}$ . The transfer characteristics are displaced by  $V_{BE}$  and there is no crossover distortion.

The circuit operates as follows:  $V_i$  increases positively to cause point B to increase to  $2V_{BE} + V_i$  and for  $V_O$  to increase by  $V_i$ . Since the base of  $Q_2$  is at  $V_i$  and its emitter is at  $V_O = V_{BE} + V_i$ ,  $Q_2$  does not change in emitter-base voltage so  $I_2$  remains constant, but the current from  $Q_1$  flows through  $R_L$  to produce  $V_O$  across  $R_L$  as long as the input voltage is positive. When  $V_i$  increases negatively it causes  $Q_2$  to conduct  $I_2$  through  $R_L$ . At the same time, point B is pulled to  $2V_{BE} - V_i$  and since the output is at  $V_{BE} - V_i$ , the  $V_{BE}$  of  $Q_1$  remains constant and  $I_1$  remains constant. The output follows  $V_i$  due to  $I_2$ .

The output voltage cannot go any higher than about  $+V_{CC} - 2V$  for the positive swing, or  $-V_{CC} + 2V$  for the negative swing otherwise the transistors will go into saturation and the output signal will be distorted. Thus, the maximum load current,  $I_L$ , drawn by

 


Figure 4-27: Class AB power amplifier  
TEAM LRN  
55



either transistor will be  $(V_{CC} - 2V)/R_L$ , and it determines the power output of the amplifier.  $I_L$  divided by  $h_{FE}$  determines the maximum base current that will need to be supplied to the bases when the respective transistor is driving the output.  $I_{BIAS}$  of Figure 4-27a must always be larger than the maximum base current required to drive the load in order to have a proper design; therefore, using the maximum base current,  $R$  can be determined. Where the efficiency of the Class A amplifier is 10%–20%, Class B amplifiers can have efficiencies as high as 78.5%. Usually they average about 60%.

### Class B Audio Power Amplifier

A very successful Class B power amplifier used for signals with frequencies in the audio range is shown in Figure 4-28.  $Q_1$  and  $Q_2$  are biased just into conduction with a constant current supplied by  $R_1$  from  $+V_{CC}$ . This design condition eliminates crossover distortion. The circuit operates as follows:  $V_i$  is applied to the primary of the input transformer,  $T_1$ . It has a center-tapped secondary each side of which feeds a base of  $Q_1$  or  $Q_2$ . The positive-going alternation of the input signal produces a positive-going signal on the base of  $Q_1$ . The resulting base current produces amplified collector current from  $Q_1$  in the upper half of the primary of the output transformer,  $T_2$ . A positive-going output signal appears across the load resistor,  $R_L$ , connected across the secondary of the output transformer.

 


Figure 4-28: Class B transformer coupled audio power amplifier

The negative-going alternation of  $V_i$ , through the secondary connection of  $T_1$ , produces a positive-going signal on the base of  $Q_2$ . Amplified  $Q_2$  collector current is produced in the lower half of the primary of  $T_2$ . A negative-going output signal appears across  $R_L$ .  $Q_1$  conducts the power transferring collector current on the positive alternation of  $V_i$ , and  $Q_2$  conducts similar power transferring collector current on the negative alternation of  $V_i$ . Through transformer action, a positive-going signal appears across  $R_L$  when  $Q_1$  conducts, and a negative-going signal when  $Q_2$  conducts. Both transistors operate in Class B because they only conduct for 180° of the input signal. This power amplifier does not amplify DC. It must have time-varying signals because of the transformer action.

$Q_1$  and  $Q_2$  should be matched transistors so that there is the same quiescent current,  $I_Q$ , through each transistor, and so that they have the same  $h_{FE}$ .  $I_Q$  should be less than 1mA, but with  $I_Q = 1 \text{ mA}$ , and a minimum  $h_{FE} = 40$ ,

$$I_{BIAS} = 2I_Q/h_{FE} = 2 \text{ mA}/40 = 0.5 \times 10^{-4} = 50 \mu\text{A}$$

With  $I_{BIAS}$ ,  $R_1$  can be calculated for a given  $V_{CC}$ . The collector-to-emitter breakdown voltage must be greater than  $2V_{CC}$ , and the turns ratio,  $N_s/N_p$ , must be chosen to match the impedance of the load,  $R_L$ , to the output load required on the transistors,  $Q_1$  and  $Q_2$ , at the power level desired.

### Special Signals

#### Square Waves from Sine Waves

There are three other special signal-conditioning circuits that are important. The first is a circuit that produces pulses from a time-varying input signal. As shown in Figure 4-29a, an easy way of producing square waves from sine waves is to use diodes, either standard diodes or zener diodes. The amplitude of the square waves is determined by the diode drop. The higher the amplitude of the input signal the squarer the output waveform.



The use of a comparator is shown in *Figure 4-29b*. A comparator is essentially an op amp without any feedback. Since op amps have very high open-loop gain, any small signal at either input will drive the output into saturation. A positive signal drives the output to  $+V_{CC} - V_{SAT}$ , and a negative signal drives the output to  $-V_{CC} + V_{SAT}$ . If a reference voltage,  $V_R$  is placed on one input, the switching point will move to  $V_R$ . Control of the pulse width can be provided by the variation of  $V_R$ . The repetition of the square waves will be at the frequency of the input.

 


Figure 4-29: Square waves from sine waves

### Trigger Pulses from Square Waves

In many applications there is a real need to provide accurate trigger pulses at particular times. One of the simplest circuits for producing sharp timing pulses is the differentiating circuit formed with

 


Figure 4-30: Producing timing pulses from square pulses

a capacitor and resistor as shown in *Figure 4-30*. A pulse with a fast rising leading edge passes through  $C$  and appears across  $R$  as a sharp rising pulse. The time constant of  $RC$  is short compared to the pulse width  $t$ .  $C$  rapidly charges and  $V_O$  goes to zero while the maximum amplitude of the input pulse continues. When the  $V_i$  pulse returns to zero, the capacitor again transmits the fast falling trailing edge of the pulse across  $R$ , producing a negative sharp falling pulse. Out of the rectangular pulse of  $V_i$  both a positive and a negative timing pulse is obtained. *Figure 4-30* shows how the positive pulse is recovered. If the diode,  $D$ , is reversed, the negative pulse is recovered.

In the circuit of *Figure 4-31*, the  $R$  and  $C$  are reversed. Now the circuit is called an integrating circuit. When  $V_i$  is a series of pulses, an integrating circuit can produce a DC voltage from the pulses. The resistor now is in series with the input signal and the capacitor across it. The  $RC$  time constant in this case is very large compared to  $t$ . As the fast rising leading edge of the  $V_i$  pulse is applied, since the  $RC$  time constant is large,  $C$  changes slowly and doesn't reach full charge until the trailing edge of the input pulse. When the trailing edge of the pulse appears,  $C$  tries to discharge, but because of the large  $RC$ ,  $C$  discharges very little.

The charge and discharge repeats itself and a waveform with a ripple appears as  $V_o$ . The  $V_i$  pulses have been converted to a DC output voltage.

Op amps can be connected as integrators and differentiators but are much more complicated than the simple RC circuits. They are used in very sophisticated circuits when needed.


 


Figure 4-31: Integrating pulses into DC signals
 
## RC Time Constants

The concept of a time constant used in the differentiating and integrating circuits is shown in Figure 4-32. When a time varying voltage, in this case a pulse with a sharp rising leading and trailing edge, is applied to a capacitor through a resistor, the charge on the capacitor can only change as rapidly as the current through will allow. For example, for the integration schematic, the voltage across the capacitor cannot change as fast as the input voltage pulse. It is restricted because the resistor limits the current. The charge on the capacitor builds up at a predictable rate as shown by the curve A in Figure 4-32b. Curve A is the voltage,  $V_c$ , across the capacitor plotted against  $\tau$ .  $\tau$  is called the time constant and is equal to the ohms resistance in the circuit times the farads of capacitance in the circuit. As shown by curve A, after one time constant, the voltage across the capacitor has obtained a value 63.2% of its final value. It takes at least five times the time constant for the capacitor to be charged to full value. The value of voltage on the capacitor in a given time can be estimated by knowing the relationship of the time constant to the pulse width  $t$ . For integration,  $\tau$  should be at least five times  $t$ . For differentiation, where the capacitor must charge rapidly with respect to  $t$ ,  $\tau$  should be only one-fifth  $t$ , or even smaller.



On the trailing edge of the pulse applied to the integration circuit, the capacitor is trying to discharge. Its voltage can change only as rapidly as the time constant will allow. Its discharge is described by curve B in Figure 4-32b. In one time constant, the voltage has reduced to 36.8% of its value when the trailing edge of the input pulse changed. It takes at least five time constants for the capacitor to completely discharge. Applying the curve A

The time constant for the capacitor circuit is:

$$\tau = RC$$

where:  $\tau$  = RC time constant in **seconds**

R = Resistance in **ohms**

C = Capacitance in **farads**

Figure 4-32: RC time constants

Courtesy of Master Publishing, Inc.

to the voltage across the capacitor when the time constant is such that the capacitor charges rapidly, the differentiator circuit of *Figure 4-30* results. Here the time constant should be such that the capacitor fully charges in one-fifth of the pulse width. Thus,  $5\tau$  should be equal to one-fifth the pulse width to allow the capacitor to charge fully.

By applying curve A and B to a variety of circuits, it is possible to visualize many different signal shapes dependent upon the relationship of the time constant to the time of pulses or time varying signal edges applied.

### Example 7. RC Time Constant

- Using *Figure 4-30*, for differentiation,  $5\tau$  must be no greater than one-fifth the pulse width  $t$  so that C charges rapidly. If  $t = 10 \mu\text{s}$ , what is the value of R if  $C = 0.001 \mu\text{F}$ ? Remember  $\tau = RC$ .
- Using *Figure 4-31*, for integration, it should take at least  $5\tau$  to charge the capacitor in the pulse width  $t$ . C charges very slowly. Using the same values of  $t$ , and C, what is the value of R? Remember  $\tau = RC$ .

#### Solutions:

$$\text{a. } 5\tau = t/5$$

$$25\tau = t$$

$$25RC = t$$

$$R = t/25C$$

$$R = 10 \times 10^{-6}/25 \times 1 \times 10^{-9}$$

$$R = 0.4 \times 10^3 = 400 \Omega$$

$$\text{b. } 5\tau = t$$

$$5RC = 10 \times 10^{-6}$$

$$R = 10 \times 10^{-6}/5C$$

$$R = 10 \times 10^{-6}/5 \times 1 \times 10^{-9}$$

$$R = 2 \times 10^3$$

$$R = 2,000 \Omega$$

## Frequency Selection

There is signal conditioning that really doesn't amplify or change the waveform of the AC signal, but rather it is a frequency selection process. Many analog signals contain a composite of signals with different frequencies. In fact as discussed in *Basic Communications Electronics*,<sup>4</sup> signals of different frequencies are mixed together to form a resultant signal that is the sum of the two frequencies or the difference of the two frequencies. Each of these signals can be processed separately to communicate the information in the original signals. As a result, there is a need to select out the desired signal by its frequency from companion signals of different frequencies. Frequency selection signal conditioning is required for this.

### Band-Pass Filters

Look at *Figure 4-33a*. It is the familiar frequency response curve that was discussed for amplifiers. The mid-band gain of the curve is A, and that gain is maintained out to a frequency of  $f_H$ , the high-frequency cutoff point, and down to a frequency of  $f_L$ , the low-frequency cutoff point. At  $f_H$  and  $f_L$  the gain is reduced to 0.707A. Since at the cutoff points the gain is down -3 dB from the mid-band gain, they are called the "minus 3 dB" points.

A signal with a frequency much higher than  $f_H$ , as the curve shows, will be attenuated, that is, it will have a much lower amplitude; the higher the frequency the larger the attenuation. Similarly, signal frequencies below  $f_L$  will be attenuated in amplitude; the lower the frequency the larger the attenuation. Frequencies from  $f_L$  to  $f_H$  will have constant gain and not be attenuated. A circuit that has such a frequency response curve can be considered a *band-pass* filter. It passes signals with frequencies in the band from  $f_L$  to  $f_H$  and attenuates the others.

It can be considered as a circuit that selects signals with frequencies within the band and rejects signals with frequencies outside the band.

<sup>4</sup> *Basic Communications Electronics*, J.W. Hudson, G. Luecke, ©1999, Master Publishing, Inc., Lincolnwood, IL.


## Low-Pass Filter

Look at *Figure 4-33b*. Here the frequency response curve extends down to zero frequency—DC. The frequency response of a DC amplifier was shown previously. Its frequency response curve looks just like this. As the signal frequency is increased from zero, a frequency  $f_c$ , the cutoff frequency, is reached where the signal begins to be attenuated; further increases in signal frequency increases the attenuation. Circuits that have such a signal frequency response are called *low-pass* filters. Signal with frequencies below  $f_c$  pass without attenuation; signals with frequencies above  $f_c$  are attenuated.

 
## High-Pass Filter

Circuits with a frequency response as shown in *Figure 4-33c* are called *high-pass* filters. Signals with frequencies below  $f_c$ , the cutoff frequency, are “not passed” (attenuated), while signals with frequencies above  $f_c$  are “passed” without attenuation.


The filters of *Figure 4-33a,b,c* can have amplification built in or they may be circuits built with passive components that have no amplification. When they are used in combination with other signal conditioning circuits, they can select signal frequencies that cover a band of frequencies above  $f_L$  and below  $f_H$ , or they can pass only signal frequencies below a frequency  $f_c$ , or they can pass only signal frequencies above a frequency  $f_c$ . The rate at which the circuits attenuate is determined by the design of the filter.



a. Band-pass filter

 


b. Low-pass filter

 


c. High-pass filter

Figure 4-33: Filters are used for frequency selection

 

a. Parallel circuit

 

b. Series circuit


$$X_L = 2\pi f_r L$$

$$X_C = \frac{1}{2\pi f_r C}$$

When  $X_L = X_C$ , circuit is in resonance at  $f_r$

$$\therefore 2\pi f_r L = \frac{1}{2\pi f_r C} \text{ or } f_r = \frac{1}{2\pi\sqrt{LC}}$$

c. Resonance

 

d. Q of resonant circuits

Figure 4-34: Tuned-circuit filters

Courtesy of Master Publishing, Inc.

## Tuned-Circuit Filters

A special kind of band-pass filter used extensively in communications circuits is called a tuned-circuit filter. It is used to select out a narrow band of signal frequencies. The tuned-circuit filter is formed by a combination of an inductance,  $L$ , a capacitance,  $C$ , and a resistance,  $R$ . It is designed at a particular frequency,  $f_r$ , called the resonant frequency. The resonant frequency is special because at  $f_r$  the inductive reactance ( $X_L = 2\pi fL$ ) is equal to the capacitive reactance ( $X_C = 1/2\pi fC$ ). When these reactances are equal, as shown in *Figure 4-34*, the resonant frequency is given by:

$$f_r = 1/2\pi\sqrt{LC} \text{ where } L \text{ is in henries and } C \text{ is in farads}$$

The band pass characteristics are shown in *Figure 4-34d*.

## Bandwidth and Q

The frequency response of the band-pass filter is plotted in *Figure 4-34d* similar to the frequency response of *Figure 4-33*, except the frequency separation between  $f_L$  and  $f_H$  is very small, within a 20% variation on each side of  $f_r$ . The 0.707 attenuation points for  $f_L$  and  $f_H$  are shown. The frequency band between  $f_L$  and  $f_H$  is called the *bandwidth*, BW. Bandwidth is defined as the half-power bandwidth—the frequency band between the  $-3$  dB attenuation points on the response curve.

A means of describing the narrowness of the band-pass filter response is to use a quality factor called  $Q$ .  $Q = f_r/BW$  and is shown in *Figure 4-34d*. Note that in the equation, if the bandwidth is very narrow around the resonant frequency  $f_r$ ,  $Q$  will be large. The wider the bandwidth, the smaller  $Q$  will be. *Figure 4-34d* shows how the response curve varies as  $Q$  varies. If the  $Q$  of the band-pass filter is known, and  $f_r$  is known then the bandwidth can be calculated using  $BW = f_r/Q$ .

## Either Parallel or Series Resonant Circuits

A resonant circuit can be either a parallel resonant circuit or a series resonant circuit. Both are shown in *Figure 4-34*. *Figure 4-34a* is the parallel circuit; *Figure 4-34b* is the series circuit. The equation for  $f_r$  is the same but calculating BW is different. Here are the equations for  $Q$ :

Series Circuit

$$Q = X_L/R_S \text{ or } Q = X_C/R_S$$

Parallel Circuit

$$Q = R_P/X_L \text{ or } Q = R_P/X_C$$

$R_S$  and  $R_P$  are as shown in *Figures 4-34a,b* respectively. If the circuit values for  $L$ ,  $C$ , and  $R$  are known,  $f_r$ ,  $Q$ , and BW can be calculated. Or if the bandwidth that is desired is known around a frequency  $f_r$ , then  $Q$ , and the  $\sqrt{LC}$  can be calculated. Then  $L$  or  $C$  can be calculated after either one is chosen. Following  $L$  and  $C$ ,  $R_P$  and/or  $R_S$  can be calculated.

## Typical Application of Filters

The typical application of filters is shown in *Figure 4-35*. A broad bandwidth signal is amplified to increase its amplitude. Then a selection of particular signal frequencies is accomplished by passing the signal through a frequency selection filter. Some circuits will require a low-pass filter, others a band-pass filter, others a high-pass filter, and yet others a tuned-circuit filter.


 



Figure 4-35: Use of filters  
TEAM LRN

Figure 4-36 is a tuned-circuit band-pass filter amplifier. It uses an N-channel depletion mode JFET as the active device. The tuned circuit in the drain results in the amplification of only a narrow band of frequencies. The  $f_r$  and  $Q$  of the circuit can be adjusted to a wide range of frequencies and bandwidth limited, of course, by the frequency response of the JFET itself. The circuit is a combination of a tuned circuit to get the band pass desired and an amplifier to increase the amplitude of the signal.

N-CHANNEL JFET  
(Depletion Mode)

 

a. Symbol

 

b. Schematic

**Figure 4-36: RF-tuned amplifier**  
Courtesy of Master Publishing, Inc.

### Example 8. Bandwidth and $Q$

If the tuned circuit of Figure 4-36 has  $X_L = 100 \Omega$ ,  $R_p = 10,000 \Omega$  and  $f_r = 10 \text{ MHz}$ , what is the  $Q$  of the circuit and the bandwidth?

**Solution:**

$$Q = R_p / X_L = 10000 / 100 = 100$$

$$BW = f_r / Q = 10 \times 10^6 / 1 \times 10^2 = 100 \text{ kHz}$$

The resonant frequency of the circuit is 10 MHz. At resonance the load is  $R_3 = 10 \text{ k}\Omega$  in parallel with  $QX_L$ . The  $Q$  of the circuit is 100, the bandwidth is 100 kHz and the voltage gain is 30 dB.

### Summary

Signals from sensors need signal conditioning. The prime signal conditioning is amplification. In this chapter, individual bipolar and MOS transistor amplifiers have been explained, followed by op amps and power amplifiers. Several special signal-conditioning circuits conclude the chapter. In the next chapter, analog-to-digital and digital-to-analog converters will be discussed.

### Chapter 4 Quiz

1. Signal conditioning:
  - a. leaves the signal unchanged.
  - b. means to modify the signal to adjust it to the application.
  - c. does not include amplification.
  - d. doesn't occur in the A-to-D or D-to-A chain of functions.
2. Amplification:
  - a. is a signal conditioning function.
  - b. is performed by bipolar transistor circuits.
  - c. is performed by field-effect transistor circuits.
  - d. a, b, c above.
  - e. none of above.
  - f. a only above.

3. The amplifier circuit of *Figure 4-4*:
  - a. has no linear operating range.
  - b. has a linear operating range of  $I_B$  from 0.02 mA to 0.1 mA.
  - c. has a linear operating range of  $V_{CE}$  from 2 to 10 volts.
  - d. b and c above.
  - e. none of the above.
4. In a common-emitter bipolar transistor amplifier:
  - a. the base-emitter junction is forward biased and the collector-base junction is forward biased.
  - b. the base-emitter junction is reverse-biased and the collector-base junction is forward-biased.
  - c. the base-emitter junction is reverse-biased and the collector-base junction is reverse-biased.
  - d. the base-emitter junction is forward-biased and the collector-base junction is reverse-biased.
5. In a common-emitter bipolar transistor amplifier:
  - a. the forward-biased base-to-emitter voltage is approximately 0.7V.
  - b. the forward-biased base-to-emitter voltage is greater than 10V.
  - c. the reverse-biased collector-to-base junction is approximately 0.7V.
  - d. the collector is tied to ground.
6. Common ways of biasing a bipolar transistor amplifier circuit are:
  - a. fixed-current  $I_B$  bias.
  - b. voltage-divider bias.
  - c. collector-feedback bias.
  - d. a, b, c above.
  - e. none of the above.
  - f. b only above.
7. The voltage gain,  $A_v$ , of a common-emitter bipolar transistor amplifier is, where  $R_L$  = total load resistance and  $I_E$  is DC emitter current in mA, and  $I_C$  is DC collector current in mA:
  - a.  $R_L \times I_E$ .
  - b.  $R_L \times I_E \times I_C$ .
  - c.  $R_L I_E$  divided by 0.026.
  - d.  $V_{BE} + V_{CE}$ .
8. The voltage gain,  $A_v$ , expressed in dB is:
  - a.  $A_v = 20 \text{ dB} \times A_v$ .
  - b.  $A_v = 20 \log_{10} A_v$ .
  - c.  $A_v = 20 \log_{10} I_C$ .
  - d.  $A_v = 10 \log_{10} A_v$ .
9. The capability of an amplifier to handle signals over a frequency range is:
  - a. called its frequency response.
  - b. called its amplitude or gain.
  - c. called its single-frequency gain.
  - d. called its linearity.
10. Cascaded amplifiers:
  - a. are amplifiers coupled together to increase the overall gain.
  - b. can use different means of coupling between stages.
  - c. the dB gain can be added to arrive at overall gain.
  - d. b only above.
  - e. a, b, c above.
  - f. none of above.

11. With AC coupling between stages of a cascaded amplifier:
  - a. the frequency response does not go down to zero frequency.
  - b. the frequency response goes down to zero frequency.
  - c. the capacitance coupling doubles the high-frequency response.
  - d. the inductance coupling limits the low-frequency response.
12. The dynamic range of an amplifier is:
  - a. the signal range that is twice where distortion begins.
  - b. the signal range that extends beyond distortion.
  - c. the signal range from small-signal to where distortion begins.
  - d. the signal range that is 10 dB below the distortion point.
13. A class B amplifier:
  - a. operates only for 30° of the input signal cycle.
  - b. operates only for 180° of the input signal cycle.
  - c. operates only for 10° of the input signal cycle.
  - d. operates for 360° of the input signal cycle.
14. For field-effect transistor amplifiers:
  - a. a change in voltage from gate to source causes a change in voltage from source to source.
  - b. a change in current from gate to source causes a change in voltage from drain to source.
  - c. a change in voltage from gate to source causes a change in current from drain to source.
  - d. a change in current from gate to source causes a change in current from drain to source.
15. Transconductance for FETs is defined as:
  - a. a change in a current as a result of a change in a voltage.
  - b. a change in a voltage as a result of a change in a current.
  - c. a change in a voltage as a result of a change in a voltage.
  - d. none of the above.
16. Field-effect transistors operate:
  - a. in the enhancement mode and depletion mode at the same time.
  - b. in the enhancement mode.
  - c. in the depletion mode.
  - d. b and c above.
  - e. a only above.
  - f. none of above.
17. Ideal operational amplifiers are amplifiers with:
  - a. zero  $Z_{IN}$ , infinite gain, zero  $Z_O$ , infinite bandwidth and zero offset.
  - b. infinite  $Z_{IN}$ , infinite gain, zero  $Z_O$ , infinite bandwidth and zero offset.
  - c. infinite  $Z_{IN}$ , zero gain, zero  $Z_O$ , infinite bandwidth and zero offset.
  - d. infinite  $Z_{IN}$ , infinite gain, infinite  $Z_O$ , zero bandwidth, and zero offset.
18. The frequency response of a general-purpose op amp:
  - a. increases as the overall gain is reduced to one.
  - b. stays the same if overall gain is reduced.
  - c. reduces as the overall gain reduces.
  - d. none of the above.
19. When  $R_f = 0$  and  $R_i = \text{infinity}$ , an op amp becomes:
  - a. an amplifier with gain equal to infinity.
  - b. an amplifier whose output voltage equals its input voltage.
  - c. a unity-gain amplifier.



- d. a only above.
  - e. b and c above.
  - f. none of above.
20. An oscillator maintains an output signal without an external input signal:
- a. when its internal gain is at least 1 and the phase of the output feedback to its input equals  $360^\circ$ .
  - b. when its internal gain is 0 and the phase of the output feedback to its input equals  $360^\circ$ .
  - c. when its internal gain is at least 1 and the phase of the output feedback to its input equals  $180^\circ$ .
  - d. when its internal gain is at least 1 and the phase of the output feedback to its input equals  $90^\circ$ .
21. A Class B complementary bipolar transistor amplifier:
- a. has no crossover distortion.
  - b. has crossover distortion.
  - c. cannot have a circuit that eliminates crossover distortion.
  - d. none of the above.
22. Diodes are very important:
- a. in forming special signal shapes or timing signals.
  - b. in circuits conducting current in both directions.
  - c. because they have the same characteristics in the forward and reverse direction.
  - d. c only above.
  - e. none of the above.
23. RC time constants are:
- a. combinations of inductance and capacitance in circuits.
  - b. very important in integrating and differentiating circuits.
  - c. combinations of inductance and resistance in circuits.
  - d. not used extensively in electronic circuits.
24. A band-pass filter has:
- a. a low-frequency and high-frequency cutoff point.
  - b. only a low-frequency cutoff point.
  - c. only a high-frequency cutoff point.
  - d. frequency response down to zero frequency.
25. The Q of a band-pass filter is:
- a. equal to  $X_L/R_S$  or  $X_C/R_S$  for a series resonant circuit.
  - b. equal to  $R_p/X_L$  or  $R_p/X_C$  for a parallel resonant circuit.
  - c. equal to  $f_r/BW$ .
  - d. all of the above.
  - e. none of the above.
  - f. c only above.

Answers: 1.b, 2.d, 3.d, 4.d, 5.a, 6.d, 7.c, 8.b, 9.a, 10.e, 11.a, 12.c, 13.b, 14.c, 15.a, 16.d, 17.b, 18.a, 19.e, 20.a, 21.b, 22.a, 23.b, 24.a, 25.d.


# Analog-to-Digital and Digital-to-Analog Conversions

## Introduction

As this chapter begins to develop an understanding of converting an input analog signal to digital codes or converting digital codes to analog signals, let's look again at the binary numbering system as illustrated in *Figure 5-1a*. This same illustration was shown in *Figure 1-5*. It is repeated here to emphasize again the digit position weighted value in a binary numbering system. Recall that the binary number is made up of binary digits (bits) in each digit position of the binary number. Each bit can only have two values, 0 or 1. Each digit position has a weighted value that is the binary digit value of 1 or 0 multiplied by the weighted value of the digit position. If the bit is a 1 the digit position has the weighted position value; if the bit is a 0, the weighted position value is 0. The total value of the binary number is the sum of all the weighted position values.

As shown in *Figure 5-1a*, the binary digit weighted digit position value increases by 2 times over the digit value to the right. This is very important to the design of digital-to-analog converters (DACs) and analog-to-digital converters (ADCs).

For example, the most significant bit (MSB) of the 8-bit binary number shown in *Figure 5-1a* has a weighted digit position value of 128. This is one-half the total value of 256 of the 8-bit binary number. Note also that the weighted digit position value for the next digit to the right (the 7<sup>th</sup> bit) is 64, or one-half the MSB value. This reduction by one-half in weighted digit position value as the bit position is moved to the right continues down to the least significant bit (LSB). The design of DACs and ADCs is based on testing the value of the input quantity to see if it is greater than the MSB value; if it is, is it greater than the MSB value *plus* the weighted digit position value of the next bit to the right? If it is, is it greater than a total of the previous bit values plus the weighted digit position value of the next bit to the right? The process continues until the input is less than the sum of the weighted values. Then the last digit weighted position value is not added but made equal to zero and a weighted position value of a next bit to the right is added and the total

 

| Digit Position | Digit Position Value $2^{n-1}$ | Binary Number | Decimal Equivalent |
|----------------|--------------------------------|---------------|--------------------|
| 1              | $2^0 = 1$                      | × 1           | 1                  |
| 2              | $2^1 = 2$                      | × 1           | 2                  |
| 3              | $2^2 = 4$                      | × 0           | 0                  |
| 4              | $2^3 = 8$                      | × 0           | 0                  |
| 5              | $2^4 = 16$                     | × 1           | 16                 |
| 6              | $2^5 = 32$                     | × 1           | 32                 |
| 7              | $2^6 = 64$                     | × 0           | 0                  |
| 8              | $2^7 = 128$                    | × 1           | 128                |

## b. Equivalent decimal

Figure 5-1: Binary number and equivalent decimal

tested again. This process continues until the value is determined or the LSB's value is included which indicates that the evaluation is complete. In other words, as the input value is tested, the digit values are added or they are set at zero as the digit positions from MSB to LSB are evaluated, and when the LSB is reached it is the end of the evaluation.

### Decimal Equivalent of a Binary Number

It is important to the A-to-D and D-to-A process to know the decimal equivalent of a binary number. *Figure 5-1b* summarizes the evaluation process. It shows how the binary digit weighted position value is multiplied by the bit value at each bit position and the total of all bit values summed to arrive at the decimal value.

#### Example 1. Converting a Decimal Number to Binary

Convert the number 4311 to a binary number.

**Solution:**

$4311/2 = 2155$  with a remainder of **1**  
 $2155/2 = 1077$  with a remainder of **1**  
 $1077/2 = 538$  with a remainder of **1**  
 $538/2 = 269$  with a remainder of **0**  
 $269/2 = 134$  with a remainder of **1**  
 $134/2 = 67$  with a remainder of **0**  
 $67/2 = 33$  with a remainder of **1**  
 $33/2 = 16$  with a remainder of **1**  
 $16/2 = 8$  with a remainder of **0**  
 $8/2 = 4$  with a remainder of **0**  
 $4/2 = 2$  with a remainder of **0**  
 $2/2 = 1$  with a remainder of **0**  
 $1/2 = 0$  with a remainder of **1**

Binary Number: **1000011010111**

**Check:**

$1 \times 4096 = 4096$   
 $0 \times 2048 = 0$   
 $0 \times 1024 = 0$   
 $0 \times 512 = 0$   
 $0 \times 256 = 0$   
 $1 \times 128 = 128$   
 $1 \times 64 = 64$   
 $0 \times 32 = 0$   
 $1 \times 16 = 16$   
 $0 \times 8 = 0$   
 $1 \times 4 = 4$   
 $1 \times 2 = 2$   
 $1 \times 1 = 1$   
**4311**

### Digital Codes of ADC

The discussion of ADCs and DACs starts by examining the codes generated by an ADC as a result of an analog input signal. *Figure 5-2b* shows the digital codes generated by a 4-bit analog-to-digital converter which has 16 codes of four bits each that are generated as an analog signal increases from 0 to 15/16 of full scale. As the signal increases 1/16 of full scale, the code changes by a digital bit. As the analog signal, shown in *Figure 5-2a*, varies in amplitude with time, the digital code generated by the ADC changes to represent the amplitude of the analog signal at the time the signal was sampled. This is demonstrated by superimposing the analog signal of *Figure 5-2a*, onto the ADC transfer curve shown in *Figure 5-2b*. The points of sampling are shown and numbered from 1 through 16, and correspond to the sampling points versus time shown in *Figure 5-2a*.

The digital codes generated at each sampling point in *Figure 5-2b* are listed in *Figure 5-2c*. The digital code generated at a particular sample is the code *nearest the amplitude just exceeded by the signal* but not large enough to generate the next code step. These codes from the sampling points appear in sequence at the output of the ADC to describe the analog signal. Depending on the ADC, the digital codes may be presented a bit at a time in series, or all bits together in parallel at specific times determined by a timing network.

As shown in *Figure 5-3*, the digital data from the ADC, represented in codes, is manipulated by computing networks to alter, modify and redefine the data, but it emerges from the computing networks again as a series of digital codes, again timed by the timing network. The codes are presented to the DAC to be converted back to an analog signal. The circuit discussion begins with a DAC.

### A Resistor Network DAC

Recall that in a digital code, the MSB's weighted binary digit position value is equal to one-half the value of the full code value, and that the next least significant bit is one-half the MSB's digit position value. This principle is used to design the DAC shown in *Figure 5-4*. It is called a R/2R ladder DAC. The circuit, shown in *Figure 5-4a*, is a resistor network with a particular combination of resistor values. From a reference voltage of  $V_{REF}$  to ground, there are resistors with  $2R$  values for each bit separated by resistors with  $R$  values, and terminated in a resistor to ground with a  $2R$  value. The circuit is for a 4-bit DAC. A switch at the end of each bit resistor of  $2R$  value either

 
 


Figure 5-2: Converting AC signals to digital codes—A-to-D conversion

 


Figure 5-3: Computing network manipulates digital data

connects to ground or to the input of an operational amplifier used as a summing amplifier. If each bit in the code to be converted is a 0, then each  $2R$  resistor is connected to ground and there is zero current into the summing amplifier.

### The Equivalent Resistance of the Network

Looking at the right end of the network at the LSB leg, the equivalent resistance of the  $2R$  resistors in parallel is  $R$ . This equivalent resistance  $R$  in series with the  $R$  between the second LSB leg equals  $2R$ . This  $2R$  parallels the  $2R$  of the second LSB leg to make an equivalent resistance of  $R$ . This process continues so that the equivalent resistance of the network between  $V_{REF}$  and ground is  $R$ .

### The Digit-Position Currents

When all bits are zero, all bit resistors are connected to ground; with  $R = 10\text{ k}\Omega$  and  $V_{REF} = 5\text{ V}$ , the current into the network is  $500\text{ }\mu\text{A}$ . The current into the MSB leg is  $250\text{ }\mu\text{A}$  and the current into the remaining network is  $250\text{ }\mu\text{A}$ . At the next lower significant bit, the  $250\text{ }\mu\text{A}$  divides into


$125\text{ }\mu\text{A}$  down the next lower significant bit leg and  $125\text{ }\mu\text{A}$  to the remaining network. The  $125\text{ }\mu\text{A}$  divides into  $62.5\text{ }\mu\text{A}$  down the second LSB leg and  $62.5\text{ }\mu\text{A}$  to the remaining network. The  $62.5\text{ }\mu\text{A}$  divides to  $31.25\text{ }\mu\text{A}$  down the LSB leg and  $31.25\text{ }\mu\text{A}$  to the remaining network. Therefore, each current in the bit legs is one half of the current in the bit position to the left, just like the digit position values in a binary number. Thus, the summing of the currents in the digit position legs results in the value of the binary number.

### The Summing Amplifier


Refer again to Figure 5-4a, when the code bit is equal to 1, the bit leg current is connected to a summing amplifier. For the summing amplifier:

$$V_{OUT} = -I_F R_F$$

 Where  $I_F$  is the current into the inverting input of the operational amplifier, and  $R_F$  is the feedback resistor from output to input. The minus sign means the output is  $180^\circ$  out of phase from the input.



a. 4-bit circuit

 

b.  $V_{OUT}$  vs. digital input (4-bit conversion)

Figure 5-4: 4-bit  $R/2R$  ladder DAC

Since,

$$I_F = I_{D3} + I_{D2} + I_{D1} + I_{D0}$$

then

$$V_{OUT} = -(I_{D3} + I_{D2} + I_{D1} + I_{D0}) R_F$$

When the code is 0101, then

$$V_{OUT} = -(I_{D2} + I_{D0}) R_F$$

If  $I_{D2} = 125 \mu\text{A}$  and  $I_{D0} = 31.25 \mu\text{A}$ , then, with  $R_F = 20 \text{ k}\Omega$

$$\begin{aligned} V_{OUT} &= -20(156.25) \times 10^{-3} \\ &= -3.125\text{V} \end{aligned}$$

Here are two more examples:

A. the code 0001 results in:

$$\begin{aligned} V_{OUT} &= -(I_{D0}) R_F = -(31.25 \mu\text{A}) \times 20 \text{ k}\Omega \\ &= -625 \times 10^{-3} \\ &= -0.625\text{V} \end{aligned}$$

B. the code 1111 results in:

$$\begin{aligned} V_{OUT} &= -(I_{D3} + I_{D2} + I_{D1} + I_{D0}) R_F \\ &= -(250 \mu\text{A} + 125 \mu\text{A} + 62.5 \mu\text{A} + 31.25 \mu\text{A}) 20 \text{ k}\Omega \\ &= -9375 \times 10^{-3} \\ &= -9.375\text{V} \end{aligned}$$

The codes and the output voltage at each step are shown in *Figure 5-4b*.

### No Change in Current for Bits of 1 or 0

The current in the digit position legs remains the same whether the bit is a 1 or a 0. Even when the current leg is connected to the summing amplifier inverting input, because of the high input impedance of the summing amplifier, there is no current from the inverting input to the noninverting input. As a result, The inverting input is at the same potential as the noninverting input, which is ground. There is no change in the currents because in both cases, whether a 1 or a 0, the terminating point is at ground.

#### Example 2. Output Voltage of R/2R Ladder DAC

The output voltage from a R/2R ladder DAC for n bits can be expressed as:

$$V_{OUT} = -(\text{decimal equivalent of binary number}) \frac{V_{REF}}{2^n}$$

What is the output voltage of a 4-bit R/2R DAC with an input code of 1010 and a reference voltage of 10 volts?

#### Solution:

The decimal equivalent of 1010 is  $8 + 2 = 10$  and  $2^4 = 16$ , therefore,

$$V_{OUT} = -(10)10/16 = 6.25\text{V}$$

Check your answer with code and voltage given in *Figure 5-4b*.

## A Simple Resistor-String DAC

One of the simplest DACs, from a circuit standpoint, is the resistor-string DAC.  $2n - 1$  resistors of equal value are interconnected from a reference voltage,  $V_{REF}$ , to ground. The outputs from the resistor string are fed to a decoder. The decoder closes the appropriate switch dictated by the input digital code. A resistor-string for a 4-bit DAC is shown in Figure 5-5a and given in more detail in Figure 5-6a.

The first position of the string is for zero volts. The next position has a voltage

$$V = (R/15R) \times V_{REF}$$

or

$$V = V_{REF}/15$$

or for any string, since it is the number 1 position

$$V_1 = 1 \times V_{REF}/2^n - 1$$

where  $n$  = bits in digital code.

The next position, position 2, has a voltage

$$V_2 = (2R/15R) \times V_{REF}$$

or

$$V_2 = 2V_{REF}/15$$

or for position 2 for any string

$$V_2 = 2 \times V_{REF}/2^n - 1.$$

The position one removed from  $V_{REF}$  has a voltage

$$V_{14} = 14 \times V_{REF}/2^n - 1.$$

## The Decoder

Figure 5-5b,c and d shows the details of the decoder as different input codes are received to identify the analog voltage and produce an analog voltage equivalent.

Figure 5-5b is for an input code of 0111; Figure 5-6c is for a code of 0011, and Figure 5-6d is for a code of 1101.

## Accuracy and Increments

The number of increments or steps in a digital code with  $n$  bits is shown in Figure 5-6b. If  $n = 4$ , there are 16 increments; if  $n = 10$ , there are 1024 increments. The  $n$  corresponds to the resolution for the ADC and DAC systems. If a system needs to have an accuracy of 0.5%, the measurement must be made to 1 part in

 


Figure 5-5: Decoder for resistor string

200; therefore, an 8-bit system which has 256 increments must be used. A 10-bit system must be used for an accuracy of 0.1% (1 part in 1000). With a full-scale range (FSR) set at a particular voltage, then the voltage value of each increment is  $FSR/2^n$ . The voltage increment for an  $FSR = 10V$  is  $10/1024$  or about 10 millivolts (9.77 to be exact).

General System Increments

Here are the increments for a general system. The first increment above zero in the resistor string is equal to:

$$V_{REF}/(2^n - 1)$$

which is equal to  $FSR/2^n$ ; therefore,

$$V_{REF}/(2^n - 1) = FSR/2^n$$

or 
$$V_{REF} = (2^n - 1)/2^n \times FSR$$

The increment is then,

$$\text{Incremental Voltage} = \frac{(2^n - 1)/2^n \times FSR}{2^n - 1} = FSR/2^n$$

For the eighth code (the 7<sup>th</sup> increment) of a 4-bit resistor string, the voltage is:

$$7^{\text{th}} \text{ Incremental voltage} = 7 \times FSR/16$$

A Simple Current-Steering DAC

A DAC similar to the resistor-string DAC can be designed by decoding a binary code and switching binary-weighted currents into a current summing amplifier. Its design is based on the same principles used for the R/2R ladder DAC of Figure 5-4. Figure 5-7 shows a very simplified version of such a DAC. A binary input code is decoded and the appropriate binary-weighted constant current is routed to a current summing amplifier to produce a proportional output voltage. If it is a 10-bit DAC, the MSB constant-current source is 512 times the LSB constant-current source. Summing the constant currents from the bit positions that have a value of 1 produces the proportional analog output voltage.


 


Figure 5-7: Simple switched constant-current 10-bit DAC

 

a. 4-bit resistor-string DAC

|      |    |    |     |      |      |
|------|----|----|-----|------|------|
| n =  | 4  | 6  | 8   | 10   | 12   |
| INCR | 16 | 64 | 256 | 1024 | 4096 |

b. Increments in N-bit code

Figure 5-6: Resistor-string DAC



An excellent application in integrated circuits is to produce the binary-weighted currents using current mirrors of the type shown in *Figure 4-23*. The currents produced are precise and uniform because of the side-by-side processing on the IC chip and wafer or slice.

### Example 3. Summing Constant-Current DAC Output

Using the constant-current DAC circuit of *Figure 5-7* and a 10-bit code, what is the final summed current for the binary input of 0110011101 when the LSB current is  $20\text{ }\mu\text{A}$ ?

**Solution:**

| MSB |      |      |   |   |     |     |    |   |    | LSB                                           |  |
|-----|------|------|---|---|-----|-----|----|---|----|-----------------------------------------------|--|
| 0   | 1    | 1    | 0 | 0 | 1   | 1   | 1  | 0 | 1  |                                               |  |
|     | 5120 | 2560 |   |   | 320 | 160 | 80 |   | 20 | $= 8,260\text{ }\mu\text{A} = 8.26\text{ mA}$ |  |

## Analog-to-Digital Converters (ADC)

The input portion of *Figure 5-3* is an ADC, an analog-to-digital converter. One of the earliest ADCs was the counting ADC shown in *Figure 5-8*. It is made up of a binary counter that counts pulses from a central clock. The counter's binary output is fed to two units—a DAC and a latch. Each unit has the number of input or output bit lines to cover the number of bits required from the ADC. Notice the DAC in the loop. This is the reason that the discussion of the DAC came first. The binary code input to the DAC produces an analog voltage that feeds one input of a comparator. The analog input voltage to be converted to a digital output is the other comparator input. When the input from the DAC is lower than the analog input, the comparator will be a high voltage (a digital 1); when the input from the DAC is equal to or greater than the analog input, the comparator output is a low voltage (a digital 0). When the comparator output changes from a high voltage to a low voltage, it triggers the latch to latch in the binary values from the bit lines of the counter. Thus, the output of the latch is the binary code matching the value of the input analog voltage.

The A to D process works like this. The counter is reset to a count of zero. The DAC output is zero as a result. If the analog input voltage,  $V_{in}$ , is some positive value, the comparator output will be a 1. As the clock increments the counter, the output of the DAC will increase in steps, each a small positive voltage. If the DAC output is a lower positive voltage than  $V_{in}$ , the counter continues to count and increases the DAC output voltage until it is greater than  $V_{in}$ . This triggers the comparator, its output goes to 0 to latch in the binary code at the output to the ADC and reset the counter. Resetting the counter to zero causes the comparator output to go to a 1 and the ADC is ready for another conversion. One of the disadvantages of the counting ADC is the time for conversion. The conversion time can be as great as  $2^n - 1$  clock cycles, where  $n$  is the number of bits of the binary output of the ADC.

 


Figure 5-8: An 8-bit counting ADC

**Example 4. Maximum Conversion Time for Counting ADC**

What is the maximum conversion time for an 8-bit, 12-bit and 16-bit counting ADC when the clock frequency is 1 MHz?

**Solution:**

The maximum conversion time is  $2n - 1$  clock cycles; therefore, since the period of a 1 MHz clock is 1  $\mu\text{s}$ ,

| N  | $2n - 1$ | Max. Conversion time                              |
|----|----------|---------------------------------------------------|
| 8  | 255      | $255 \mu\text{s} = 0.255 \text{ milliseconds}$    |
| 12 | 4095     | $4095 \mu\text{s} = 4.095 \text{ milliseconds}$   |
| 16 | 32767    | $32767 \mu\text{s} = 32.767 \text{ milliseconds}$ |

**Successive Approximation Register (SAR) ADC**

An improvement in conversion time results when using a Successive Approximation Register (SAR) ADC. As shown in Figure 5-9, the counter of Figure 5-8 is replaced with logic, register and latch circuits to make up the SAR, one of the most popular ADCs. The SAR can have conversion times from 100  $\mu\text{s}$  to 1  $\mu\text{s}$  and up to 16 bits in resolution. Semiconductor technologies of bipolar, CMOS and combinations of both have been used to design the SAR. The SAR seems to be the design of choice for the conversion time required because the desired performance can be obtained at a reasonable cost. In addition, system throughput (speed) can be traded for accuracy—increasing speed decreases accuracy.

The SAR gets its name from successively comparing the input analog voltage to the output of a DAC that has a binary-weighted code at its input. The conversion process begins by setting the MSB of the input to the DAC from the SAR to a 1. All the other bits are set to 0. This produces an analog voltage at the DAC output equal to one-half the full-scale range of the DAC. At the comparator, as with the counting ADC, the DAC output is compared to the input analog voltage. If the input voltage is greater than the DAC voltage,

 


Figure 5-9: Successive approximation ADC  
TEAM LRN  
74

the comparator output is a 1 and the SAR MSB is left at a 1, and the next most significant bit input to the DAC is set to a 1. With the MSB and next significant bit set to a 1, the output from the DAC will now be one-half plus another one-quarter to equal three-quarters of the full-scale range of the DAC. The sequence is shown in *Figure 5-9b*.

The sequence continues to set the next most significant bit to a 1 (all other bits are zero) as long as the comparator output is a 1. Each time a binary-weighted voltage is added by the DAC to its output—one eighth, one sixteenth, one thirty-secondth, and so on—the comparator output will be a 1 as long as the input voltage is greater than the output of the DAC. When setting the next significant bit to a 1 causes the input voltage to be less than the DAC output, the comparator output goes to 0. This results in setting the last significant bit back to a 0 from a 1, reducing the DAC output below the input voltage. But at the same time the next most significant bit is set to a 1 and the DAC output increased again; however, this time only say one thirty-secondth of an increment of voltage is added instead of the one-sixteenth that was added at the bit before. This is shown in *Figure 5-9b*. The successive approximation continues until all bits are tested and the closest approximation is obtained. The result is that the SAR output bit either is set to a 1 or a 0 depending on the result of the comparison of the output of the DAC and the input voltage. The final digital code for *Figure 5-9b* is 11101010.

The time to convert the input analog voltage to a digital output is  $n$  clock cycles, much less than the counting ADC. *Figure 5-9b* shows that after  $n$  clock cycles all the bits have been tested and set and the SAR output will be the digital output code. The output can be taken in parallel or shifted out as each comparison is made. This is an additional advantage of the SAR ADC.

### Example 5. Maximum Conversion Time for SAR DAC


Repeat the calculation of the maximum conversion time of an 8-bit, 12-bit and 16-bit SAR ADC. The clock frequency is 1 MHz whose period is 1  $\mu$ S.

**Solution:**

| $n$ | Max. Conversion Time ( $n$ clock cycles) |
|-----|------------------------------------------|
| 8   | 8 $\mu$ S                                |
| 12  | 12 $\mu$ S                               |
| 16  | 16 $\mu$ S                               |

### Capacitor Charge-Redistribution ADC

A block diagram of a hybrid resistor-tree, capacitor charge-redistribution ADC is shown in *Figure 5-10*. It consists of a resistor-tree conversion circuit that handles  $M$  bits of the ADC output and a charge-redistribution capacitor bank conversion circuit that handles  $K$  bits of the ADC output. The control logic, under synchronization by the clock, provides the switching logic for setting the bits in the SAR, the switch settings for the resistor tree and the switch settings for the capacitor bank. After comparison of a bit by the comparator, similar to the process previously described for the SAR ADC, the bit evaluation by the comparator is fed to the SAR to set the bit for the ADC output. The hybrid DAC is a compromise between using an all capacitor charge-redistribution circuit and an all resistor-tree circuit. The capacitor-charge redistribution has slow conversion times;

 

**Figure 5-10: Hybrid R-tree capacitor charge-redistribution ADC**

the resistor-tree circuit has faster conversion times but uses large IC real estate, especially as the bits in the ADC output increase. In integrated circuits, resistors use more area than capacitors.

## The ADC Operation

In the hybrid ADC, the input analog voltage is captured as an amount of charge on a bank of capacitors. The capacitors are binary-weighted and handle a certain number of bits (equal to  $K$ ) of the digital code to be converted. The remaining bits (equal to  $M$ ) are converted through a resistor tree conversion. The charge on the capacitors, which remains constant during the conversion, plays an important part, not only in the  $K$  bit conversions, but also in the conversion of the  $M$  bits using the resistor tree. For example, in *Figure 5-11*,  $M = 5$  and  $K = 3$  so that five bits are converted using the resistor tree and three bits are converted using the binary-weighted capacitors. The  $M$  bits are the five most significant and the  $K$  bits are the three least significant.

 


Figure 5-11: Details of resistor tree and capacitor bank (data acquisition period)

## Converting the M Bits

The conversion process starts with the data acquisition period shown in *Figure 5-11*. Switch  $S_b$  is connected to the input analog voltage,  $V_{in}$ , switch  $S_x$  is connected to  $V_{DD}/2$  and  $S_a$  is connected to  $V_{issb}$ . The binary-weighted capacitor bank charges to  $V_{DD}/2 - V_{in}$  because the lower end of the capacitors are connected to Node Z. The total capacitance in the bank is  $2^K C$ . The offset capacitor  $C_{OS}$ , equal to  $C/2$ , is charged to  $V_{DD}/2 - V_{issb}$ . Both inputs to the comparator are connected to  $V_{DD}/2$  at this time, thus, no comparison.

At the completion of the data acquisition period  $S_x$  opens,  $S_b$  switches from  $V_{in}$  and is connected to the  $V_m$  line of the resistor tree, as shown in *Figure 5-12*, and  $S_a$  is connected to ground. The voltage at Node X is the important voltage in all of the conversions for it feeds the minus input to the comparator. The plus input of the comparator is connected to  $V_{DD}/2$ . If the value of Node X is less than  $V_{DD}/2$ , the comparator output will be a 1; if it is greater than  $V_{DD}/2$ , the output will be a 0.

With  $S_b$  connected to the resistor tree, the control logic sets the MSB of the output digital code to a 1 and selects the tap from the resistor tree that represents one-half of full-scale range for  $V_m$  just as in the SAR ADC. As a result, the voltage at Node X is evaluated against  $V_{DD}/2$ . If the voltage of Node X is less than  $V_{DD}/2$ , the MSB of the output digital code from the SAR is set to 1. If the voltage at Node X is greater than  $V_{DD}/2$  the output bit of the SAR is set to 0. This completes the evaluation of the MSB; it is either set to a 1 or a 0.

The control logic steps to evaluate the next significant bit. It sets the next significant bit to a 1. This along with the MSB value of a 1 or 0 will cause the SAR to select the corresponding

 


Figure 5-12: Evaluating R-tree bits

value of  $V_m$  from the resistor tree to feed the Node Z line connected to the capacitor bank. The new voltage value on the Z line causes the constant charges on the capacitor bank to redistribute and change the voltage at Node X. The new Node X voltage is compared to  $V_{DD}/2$ , and the bit evaluation is completed by setting the second most significant bit to a 1 or 0 depending on the result of the comparison. The bit evaluation process continues until all M bits are evaluated. This results in a set SAR code output for the M bits. At the end of the M bit evaluations, the voltage of Node X will be representative of the value of the five most significant bits in the SAR output digital code.

### Converting the K Bits

The Node X voltage value is maintained as the evaluation now changes to the capacitor bank circuit to evaluate the K bits, the last three significant bits of the digital output code. The K bit evaluation is accomplished by switching the ends of the capacitors in the respective bit position, one bit position at a time, to the Y line. The Y line connects to a resistor-tree connection that is one significant bit higher in voltage ( $V_m + \Delta v$ ) than the Z line voltage.

 


Figure 5-13: Evaluating capacitor bits

The most significant bit of the three K least significant bits is evaluated first as shown in Figure 5-13. The end of its capacitor, in this case of value C, is connected to the Y line. The charge on the capacitors redistributes and changes the voltage at Node X. If Node X is greater than  $V_{DD}/2$ , the bit is set to a 1 and the end of the capacitor is left connected to the Y line; if it is less than  $V_{DD}/2$ , the bit is set to a 0 and the end of the capacitor is switched back to the Z line. With the bit set to a 1, the voltage on capacitor C is added to the resistor tree value to set the Node X voltage value.

The control logic switches the end of the next binary-weighted capacitance of the next least significant bit by changing its  $S_d$  switch and connecting it to the Y line. The charge redistributes with the new capacitor, now with a value of  $2C$ , and the voltage at Node X changes correspondingly. The Node X voltage is compared to  $V_{DD}/2$  and the bit evaluated as above and the output set to a 1 or a 0. As before, if the bit is set to a 0, the end of the capacitor is returned to the Z line with switch  $S_d$ . The process continues until all K bits are evaluated and the final SAR digital code is sent out from the SAR.

## Highest Speed Conversions

The highest speed conversions are made with flash ADCs. The high speed is made possible by the use of simultaneous comparisons of the analog input voltage to references generated from a resistor string. A block diagram of a flash ADC is shown in *Figure 5-14*. For an  $n$ -bit flash converter, there are  $2^n - 1$  reference voltages and  $2^n - 1$  comparators required. Thus, for an 8-bit flash converter, 255 comparators are required, and for a 10-bit flash converter, 1023 comparators are required. A high price is paid for the speed advantage—high power, large silicon area for the ICs, and high cost contribute to the price that must be paid.

The conversion process is rather simple. The reference voltages are connected to the minus input of each comparator and are separated in value by one LSB. The analog input voltage is connected to the plus input of each comparator. A simultaneous comparison is made at each comparator. If the input analog voltage on the plus input is less than the reference voltage on the minus input, the output of the comparator is a 0. The comparator output will be a 1 if the input analog voltage is greater than the reference voltage. Each comparator output is presented to the decoder at the same time and the decoder's output is stored as an  $n$ -bit wide code in a latch. All the inputs of the input analog voltage that are greater than their respective resistor-string reference voltages will have comparator outputs of a 1; all the inputs that are less than their respective resistor-string reference voltage will have comparator outputs that are 0. The resultant digital code into the decoder results in the equivalent binary output code, for a given  $n$ -bit code, that represents the value of the input analog voltage.

 


Figure 5-14: Flash converter

## Sample and Hold and Filters

### Sample and Hold

There are two other functions that are associated with A to D conversions. One is sample and hold; the other is filtering. Sample and hold, as shown in *Figure 5-15*, is just what it says. The input analog signal is sampled by switch  $S_1$  closing momentarily and charging  $C_1$ .  $C_1$  then holds the value of the input voltage until the ADC can process the data. It probably is obvious that a capacitor that leaks its charge between samples would contribute errors to the sampling process. Likewise, switches that have variable contact resistance vary the times to charge the capacitors and contribute errors. Thus, high quality capacitors and fast switches are key to sample and hold

 


Figure 5-15: A simple sample and hold circuit

circuits. At one time, sample and hold circuits were available independently; however, most sample and hold circuits are incorporated right in the ADC. In fact, in the hybrid resistor-tree capacitor charge-distribution ADC there is no need for a sample and hold. It is built in as part of the circuit design, saving cost on providing such a circuit.

## Filtering

Filtering, as shown in *Figure 5-16a*, is used to limit the bandwidth of signals. As such, it can smooth out the input signal, eliminate noise spikes, limit the high frequency response, select particular signal frequencies, and the like. *Figure 5-16b* shows their specific

 


Figure 5-16. Filtering

use in DAC systems. The DAC output can be a step-like signal. Filtering is used to smooth out the step nature of the signal and output a smooth analog signal. Most filters are tailored to the particular application. They are selected to control a specific need of the system; therefore, general filters are usually not the solution. The filters must be chosen specifically for the application. The example for the DAC system in *Figure 5-16b* requires that the filter be chosen for the specific system. The output signal that emerges must be a smooth continuous signal with time rather than a jagged jerky out. The result is that the input signal shown in *Figure 5-2* is reproduced very accurately after the ADC conversion and the DAC conversion.

## Summary

In this chapter, DACs and ADCs have been discussed showing techniques used for each and circuits that implement the functions. In the next chapter, digital processors will be discussed. They receive the digital signals from the ADCs, modify and manipulate the digital signals, and then deliver the digital signals to the DACs.

## Chapter 5 Quiz

1. In a binary number:
  - a. the digit position value increases by 1 times over the digit value to the right.
  - b. the digit position value increases by 2 times over the digit value to the right.
  - c. the digit position value increases by 4 times over the digit value to the right.
  - d. the digit position value increases by 8 times over the digit value to the right.
2. A decimal equivalent of a binary number:
  - a. is the addition of all the bit position values for all the bits equal to 1.
  - b. is the multiplication of all the bit position values for all the bits equal to 1.
  - c. is the subtraction of all the bit position values for all the bits equal to 1.
  - d. is the division by 2 of the bit position value of the LSB.
3. The principle used to design a resistor-string DAC is:
  - a. the MSB is one-eighth the full value and the next bit position is one half of the MSB value.
  - b. the MSB is one-fourth the full value and the next bit position is one half of the MSB value.
  - c. the MSB is one-third the full value and the next bit position is one half of the MSB value.
  - d. the MSB is one-half the full value and the next bit position is one half of the MSB value.
4. The equivalent resistance between  $V_{REF}$  and ground of the R/2R ladder DAC is:
  - a.  $4R$ .
  - b.  $2R$ .
  - c.  $R$ .
  - d.  $R/2$ .
5. The digit position current in the R/2R ladder DAC is:
  - a. one half the current in the bit position to the left.
  - b. one eighth the current in the bit position to the left.
  - c. one fourth the current in the bit position to the left.
  - d. equal to the current in the bit position to the left.
6. The voltage increment from a 10-bit resistor-string DAC with 10V applied is:
  - a. about 10 volts.
  - b. about one volt.
  - c. about 10 millivolts.
  - d. about 100 millivolts.
7. A simple current-steering DAC:
  - a. combines both voltage and current to produce the analog output.
  - b. adds binary-weighted voltages to produce the analog output.
  - c. produces the analog voltage by sensing a resistor string.
  - d. adds binary-weighted constant currents to produce the analog output.
8. The counting ADC:
  - a. contains a DAC whose input is the output of a counter.
  - b. contains a comparator to compare the analog input to the output of a DAC.
  - c. latches the counter output code when the comparator inputs are equal.
  - d. all of the above.
  - e. a and b only above.
9. The SAR gets its name from a process that:
  - a. successively compares the input analog voltage to the output of a DAC that has a binary-weighted input code.



- b. sums a series of binary-weighted currents.
  - c. sums current from a ladder resistor network.
  - d. sums voltages from a resistor string.
10. The maximum conversion time for a SAR DAC is:
- a.  $4n$  clock cycles.
  - b.  $n$  clock cycles.
  - c.  $8n$  clock cycles.
  - d.  $n/2$  clock cycles.
11. In the hybrid resistor-tree capacitor charge-redistribution ADC:
- a.  $(M - K)$  bits are converted using an R tree and  $(M + K)$  bits using a C network.
  - b.  $K$  bits are converted using an R tree and  $M$  bits using a C network.
  - c.  $M$  bits are converted using an R tree and  $K$  bits using a C network.
  - d.  $(M + K)$  bits are converted using an R tree and  $(M - K)$  using a C network.
12. In the hybrid resistor-tree capacitor charge-distribution ADC:
- a. the  $K$  bits are evaluated first and then the  $M$  bits.
  - b. the  $M$  bits are evaluated first and then the  $K$  bits.
  - c. the  $K$  and  $M$  bits are evaluated at the same time.
  - d. only the  $K$  bits are evaluated.
13. In Flash ADCs:
- a. the high speed is made possible by simultaneous comparisons.
  - b. there are as many comparators as there are bits.
  - c. there are as many reference voltages as there are bits.
  - d. the basic string for comparisons is a capacitor charge-redistribution network.
14. A sample-and-hold circuit:
- a. has a momentary switch that connects the input voltage to a capacitor long enough for the capacitor to charge.
  - b. has a resistor in series with a capacitor in series with a switch.
  - c. has a capacitor that is charged to hold the value of the input voltage.
  - d. a only above.
  - e. a and c above.
  - f. none of the above.
15. Filtering is important to DAC operation:
- a. because it adds noise to the output signal.
  - b. because it returns the DAC output to a smooth continuous signal.
  - c. because it selects one frequency to pass on from the output.
  - d. because it acts as a very high-frequency high-pass filter.

Answers: 1.b, 2.a, 3.d, 4.c, 5.a, 6.c, 7.d, 8.d, 9.a, 10.b, 11.c, 12.b, 13.a, 14.e, 15.b.

# Digital System Processing

## Introduction

Previous chapters have sensed the analog signal, conditioned the signal and converted it from analog to digital. In this chapter, the processing of the digital signal to modify, calculate, manipulate, change the form of the signal or to route the signal to particular channels is discussed. All or any of these processing operations may be needed to accomplish a task predetermined by the application that is being fulfilled. The total system is designed to perform a task, and the digital processor is a very important part of the system.

## Digital Processor or Digital Computer

As the name implies, the digital processor inputs, stores, performs operations and outputs digital signals. Performing logic or arithmetic computations, modifying the format of the signal, storing data temporarily or more permanently, decoding signals for display and outputting signals are some of the operations dictated by the instructions in the application program.

Figure 6-1 shows the basic structure of a digital processor, more generally called a digital computer. The main brain of the structure is the CPU (central processing unit) where the operations that are performed are decided upon and controlled. The digital signals

in the form of binary codes that tell the digital processor which operation to perform are called instructions. Each digital processor is manufactured to respond to a particular set of instructions. Each instruction in the set will cause the digital processor to do a unique operation. For example, an instruction might cause the digital processor to input a digital signal from a particular input. Or an instruction might tell the processor to take the input signal and store it temporarily, or to store it in memory more permanently. Another instruction might take a digital signal that has been operated on by the processor and output it to a particular output. Or an instruction might tell the processor to do a logical operation (for example, AND two binary numbers together), or to do an arithmetic operation like ADD two binary numbers, or maybe subtract them. The instructions, presented in sequence to the processor, are called a program.

## Digital Computer Program

The arrangement of the instructions, one after another, for the digital processor to perform set operations in a particular sequence to accomplish a task is called a *program*. The set of instructions in a program is stored in memory to be recalled each time that the desired task is required. If a different task is required, then a different program is needed.

 


Figure 6-1: A digital processor

As shown in *Figure 6-1*. The instructions of a program are stored in memory at specific addresses, usually in sequence, and are moved from memory to the CPU over the data bus. It is just like a home with a particular address. The post office uses the address to deliver the mail. In like fashion, the instructions in memory are at unique addresses. When a particular task is needed, the address of the first instruction in the program is sent by the CPU to memory over the address bus. The address locates the instruction in memory, the CPU instructs the memory to read the instruction and it is sent over the data bus to the CPU. The CPU decodes the instruction and performs the directed operation. Each subsequent instruction in the program is addressed, recovered from memory, sent to the CPU and executed.

### Address and Instruction/Data Bus

Addresses, over the address bus, are not only used to locate instructions in memory but are used to identify particular inputs or particular outputs. By addressing a particular input, the CPU has selected that input to supply input data; or addressing a particular output, the CPU will send data to that output to be transmitted to the next function. And there is another use of addresses. When an instruction calls for an arithmetic operation, (or other operations that require unique information), such as, ADD A and B, the data A and the data B must be supplied to the CPU before the operations can be performed. Data A and B and other data used for the program being executed are stored in another portion of memory, separate from the program. Data A and Data B are addressed over the address bus just like instructions and recovered and sent to the CPU. The instructions and the data are transmitted from memory to the CPU over the data bus; thus, this bus is usually called the instruction/data bus.

### Timing and Control

All the CPU operations, all address, instruction, and data transfers, as shown in *Figure 6-1*, occur in a timed sequence determined by the timing and control signals derived from the CPU's clock. The clock is a circuit that outputs a series of repetitive pulses occurring at a set frequency or set frequencies. The clock pulses have fast rise and fall times so that circuits can be triggered on either edge to accurately time the operation of the circuits. The rise time is called the leading edge and the fall time the trailing edge of the pulses.

Clock signals must be very accurate. As a result, they are generated by phase-locked loops (PLLs), or for the greatest accuracy, by quartz crystal oscillators. Quartz crystals, of a particular cut and size, when excited with electricity, will oscillate at a very precise frequency. The clock signals precisely control the transfers, manipulations, and storage of information throughout the CPU and the accompanying total system.

### Power Systems

Each digital processor has a complete unique power system. Sophisticated systems are required for the distribution of the supply voltages and the required currents, regulated to keep the variation of voltages to within tight limits, as the circuits switch rapidly from one state to another. Extensive use of bypass capacitors at critical junctions help to maintain voltages within limits as significant values of current are switched along the supply lines.

As the density of integrated circuits has increased, there is more need for heat sinks and cooling air distribution as the watts/in<sup>2</sup> dissipation increases. IC technology has led the way as circuit density increased within an IC to change the circuit type from bipolar to MOS (metal-oxide-semiconductor) to CMOS (complementary MOS) so that the power dissipation per circuit function has been reduced. As density further increased, the supply voltages for circuit operation have been reduced from 5V to 3V, and now 1.8V to again reduce the power dissipation per function. The tight regulation specifications still remain even with the reduction in the voltage values.

## The CPU— Program Counter

Figure 6-2 is a diagram of a generalized central processing unit (CPU). The main components are the program counter, the instruction register, the instruction decoder, the data address register, the arithmetic and logic unit (ALU), the timing and control circuits, and the permanent and temporary storage. As discussed previously, a digital code, called an instruction, organized in sequence into a program, is sent to the CPU to

 



Figure 6-2: A generalized CPU

instruct it to execute a particular operation. The instruction came from a memory address contained in an instruction address register called the program counter. The program is stored in memory one address after another in sequence so the program counter holding the address can be incremented by one to step through the program instructions one step after the other. Thus, the name for the address register is the *program counter*. Each instruction address from the program counter addresses the next step in the program as the task proceeds.

### Example 1. Program Counter

Using 4-bit addresses, show in a simple example how the program counter is incremented to sequence through a program to add 16 to 8.

**Solution:**

 

### CPU—Instruction Register and Instruction Decoder

As the digital code representing the CPU instruction is retrieved from its memory location it is stored in a temporary storage register called the *instruction register*. Here it is recognized and decoded by the *instruction decoder* and directed to the appropriate circuits to execute the operation dictated by the instruction.

### CPU—The Data Address Register

If the instruction requires that additional data be fetched from memory, then the next instructions will direct the CPU to place the address for the data in the *data address register*, send the address to memory to retrieve the data and store it in a temporary storage location in the CPU, either a register, or a RAM location. Through a multiplexing switch, the instruction and data address are sent to memory over the same bus, the data bus.

### CPU—The Arithmetic Logic Unit (ALU)

The ALU provides the logical, computational, and decision-making capabilities of the CPU. Basic arithmetic operations, such as, addition, subtraction, multiplication, and division; basic logical decisions, as well as, greater than, less than, equal to, positive or negative are all performed by the ALU.

Registers for temporary storage of data brought from inputs or from memory are available in the ALU. The information in these registers is used by the CPU for completing the operation directed by the instruction addressed by the program counter. When the operation is completed the information is erased or replaced with new information to be used for executing the next instruction.

### CPU—Internal Memory

There are internal memories contained within the CPU. They may be additional registers, read-only memory (ROM) or random-access memory (RAM). They store particular sets of instructions called subroutines, temporary data, and data routing information. The RAM is of the type that needs to be refreshed periodically. Some CPUs do not have any ROM or RAM, but usually have the additional registers. For these CPUs, the ROM or RAM is in the external memory shown in *Figure 6-1*.

### Timing and Control

Each of the operations of the CPU is timed and controlled by circuits that operate at specific times. Many operations occur at the same time; others are sequenced so they operate after data is entered, or transmitted, or before another operation. The timing and control signals, generated from the master clock signals, not only time the CPU, but also are distributed throughout to time and control the complete system.


### CPU—Input and Output (I/O)

Not all CPUs have the input and output selection circuits in the CPU; for some, these circuits are external as shown in *Figure 6-1*. *Figure 6-2* shows the I/O contained in the CPU. The input address registers determine the particular input that will receive data, and the output address registers determine the particular output used to couple out data to external destinations. If the CPU needs data, the CPU sends the address of the input to receive the data to the input address register and inputs the data from that input. The CPU inputs the data at a select time so that it is synchronized to the operation that is being executed. Likewise, after the CPU has executed an operation, the resultant data needs to be outputted to complete the task. The CPU sends the address of the output that is to couple out the resultant data to the output address register, and, synchronized by the clock, outputs the data.

**Example 2. I/O Selection**

Show with a simple example, using a 4-bit code, how a particular input is selected by the CPU.

**Solution:**

 **What is a Microprocessor?**

When all the circuitry for the functions shown in *Figure 6-2* for a CPU are contained in an IC, the IC is known as a microprocessor. Attach to it the I/O functions, memory, and power supply, and one has a digital processor shown in *Figure 6-1*, or more commonly, a digital computer.

**What is a Microcomputer?**

When all the circuitry for a digital computer is contained on one integrated circuit, the unit is called a microcomputer. Even though there are self-contained memory and I/O circuits contained in a microcomputer, external circuits of the same type may be added, especially memory. As a result, there are many variations between microprocessors and microcomputers. Memory, I/O, signal conditioning, timing and control many times are added to adapt the particular IC to an application, or to a market requirement.

A particular type of microcomputer, now called a microcontroller unit (MCU), has been adapted to the industrial control market. A microcontroller unit from the MSP430 family manufactured by Texas Instruments will be used in *Chapter 7* to explain assembly-language programming and in *Chapter 10* to demonstrate the application of MCUs by providing the reader an opportunity for a hands-on project that can be built from contained instructions.

**System Clarifications****System Buses**

In *Figure 6-1* and *Figure 6-2* there are wide signal paths connecting the functional units in the diagrams. Each of these contains multiple wires connecting between units. Each is called a “bus” because it represents more than one wire making the interconnections between units. For example, if the memory in *Figure 6-1* has 65,536 different memory storage locations, then a binary address of 16 bits must be used to address each location. The address bus, as a result, is really 16 wires bundled together, each wire carrying a binary signal of 1 or 0 to make up the 16-bit word for the address.

The expansion of memory locations as bits are added to the address is shown in *Figure 6-3*. If the address is expanded to 24 bits, 16,777,216 memory locations can be addressed; if the address is expanded to 32 bits, 4,294,967,296 locations can be addressed. If each memory location has an 8-bit piece of binary information (called a byte), then 24 bits will locate 16 million bytes of information; more precisely, 16,777,216 bytes of memory, but shortened by industry use to a 16-Megabyte memory (16 MB). In like fashion, a 32-bit address will locate 4.2 billion bytes or is a 4.2-Gigabyte memory (4.2 GB).

Memory and data buses are the buses that must be the widest (to be able to handle the largest number of bits at a time) in order to carry the memory addresses and the instructions required by the system. Control

| Address Bits | Locations | Address Bits | Locations | Address Bits | Locations  | Address Bits | Locations     |
|--------------|-----------|--------------|-----------|--------------|------------|--------------|---------------|
| 1            | 2         | 9            | 512       | 17           | 131,072    | 25           | 33,554,432    |
| 2            | 4         | 10           | 1024      | 18           | 262,144    | 26           | 67,108,864    |
| 3            | 8         | 11           | 2048      | 19           | 524,288    | 27           | 134,217,728   |
| 4            | 16        | 12           | 4096      | 20           | 1,048,576  | 28           | 268,435,456   |
| 5            | 32        | 13           | 8192      | 21           | 2,097,152  | 29           | 536,870,912   |
| 6            | 64        | 14           | 16,384    | 22           | 4,194,304  | 30           | 1,073,741,824 |
| 7            | 128       | 15           | 32,768    | 23           | 8,388,608  | 31           | 2,147,483,684 |
| 8            | 256       | 16           | 65,536    | 24           | 16,777,216 | 32           | 4,294,967,296 |

Figure 6-3: Memory locations vs. address bits


buses and timing signal lines may have only a single line, but in most cases have multiple lines, but their buses hardly need to be as wide as the address and data buses.

## Digital Information Nomenclature and Transfer


Binary strings of bits are identified in a number of ways. Long strings of bits are called *words*. Modern day digital computers use 16-, 32-, and 64-bit words. In *Figure 6-4a* a 16-bit word is shown. In any binary representations, the most significant bit (MSB) is on the left of the string, and the least significant bit (LSB) is on the right.

A group of 8 bits, as shown in *Figure 6-4a*, is called a “byte,” and is a very common grouping used to identify memory capacity. A 1 MB (1 megabyte) memory has a storage capacity of one million locations with a byte (8 bits) at each location. Even though a memory may be organized differently, say two million locations with 4 bits per location, the capacity is still referred to as 1 MB. Years ago this 4-bit group was used extensively and called a “nibble.”

 
A byte, or a number of bytes, is a common way of identifying other binary signals. A control signal may contain a certain number of bytes. A code may be made up of words that are each a byte, or a code may contain any number of bits. This will be further clarified in the section on *Digital Signal Representations*.



a. Words, bytes, nibbles

 

b. Parallel transfer

 

c. Serial transfer

Figure 6-4: Digital information nomenclature and transfer

Data Transfers

Within a digital computer, digital processor, digital system, or digital circuit, the binary bits that carry the information must be transferred from place to place to allow the system or circuit to perform its task. *Figures 6-4b and c* show the method of transfer. *Figure 6-4b* is a parallel transfer and *Figure 6-4c* is a serial transfer. This discussion centers on the signals within a digital processor, or within a self-contained digital system. Further discussion of the transfer of data between digital systems is contained in *Chapter 8*.

In *Figure 6-4b*, all the bits of binary information are transferred at the same time. If it is a 16-bit word as shown, all 16 bits are sent from one location to the other at the same time, in parallel. The highest speed digital processors use the parallel transfer so no time is lost in processing the binary information to act on it.

The serial transfer, shown in *Figure 6-4c*, takes longer in time to process the information. As shown, each bit of information is shifted in sequence to identify all the bits in the 16-bit word. Using the 16-bit word as an example, 16 clock-shifting pulses are required to identify all 16 bits. The shifting of the bits can either be in a right or left direction, as shown, and there are a number of different types of shifts—a logical, circulate, or arithmetic.

Logical Shifts

A right 11-step shift is shown in *Figure 6-4c*. As the bits are shifted right toward the LSB position, a detection circuit receives the LSB output and identifies the bit value as 1 or 0. The bits arrive serially, one bit after another, until all 16 bits of the word are identified. In a logical shift, bits of 0 values are inserted at the MSB position as the shifting occurs. For a left shift, the identifying circuit is at the MSB position rather than the LSB position, and the bits are inserted at the LSB position.

Arithmetic Shifts

Many times the instruction to the processor may only be for one shift because shifting a binary word to the right divides the binary value by 2. Likewise, shifting a binary word one bit position to the left, multiplies the binary value by 2. These types of shifts are particularly significant in arithmetic operations.

Example 3. Arithmetic Shift Left for Multiplication

Show an example, using an 8-bit word, to demonstrate how shifting a binary number one bit position to the left multiplies the binary value in the number by 2.

Solution:

|                                      |     |    |    |    |   |   |   |   |            |
|--------------------------------------|-----|----|----|----|---|---|---|---|------------|
| Bit Position Value                   | 128 | 64 | 32 | 16 | 8 | 4 | 2 | 1 |            |
| Original No. Value                   | 0   | 0  | 0  | 16 | 0 | 4 | 0 | 1 | = 21       |
| Original No.                         | 0   | 0  | 0  | 1  | 0 | 1 | 0 | 1 |            |
| New Value                            |     |    | 32 | 0  | 8 | 0 | 2 | 0 | = 42       |
| Original number shifted left one bit | 0   | 0  | 1  | 0  | 1 | 0 | 1 | 0 | ← Insert 0 |

In a right circulate shift, the bit value in the LSB position is *circulated back and inserted at the MSB position*. After 16 clock shifts, the bits of the 16-bit word are shifted out and identified, and, after the shifting is complete, the same data is in the 16-bit word as before the shifting process began. Such shifts are very useful in arithmetic and logical shifts without destroying the original data present before the shifts.

Binary information can identify both positive and negative numbers. To do this, the MSB of the binary word is reserved to be a sign bit. If the bit is a 0, the binary number is positive; if the bit is a 1, the binary number



is negative. During an arithmetic shift, the sign bit in the MSB position is maintained. Thus, when a shift occurs, the value in the MSB position is reinserted into the MSB position, so that it remains the same and the arithmetic value of the binary number is not lost. Examples for a 4-bit code are shown in *Figure 6-5*.


| Binary Signals                                         |   | Decimal Numbers |   |   | Characters |     |     |     | Commands  |
|--------------------------------------------------------|---|-----------------|---|---|------------|-----|-----|-----|-----------|
| MSB    LSB                                             |   | or<br>or        |   |   |            |     |     |     |           |
| When<br>MSB = 0<br>represents<br>8 positive<br>numbers | 0 | 0               | 0 | 0 | @          | \   | P   | p   | Power OFF |
|                                                        | 0 | 0               | 0 | 1 | A          | a   | Q   | q   | STOP      |
|                                                        | 0 | 0               | 1 | 0 | B          | b   | R   | r   | GO        |
|                                                        | 0 | 0               | 1 | 1 | C          | c   | S   | s   | A ON      |
|                                                        | 0 | 1               | 0 | 0 | D          | d   | T   | t   | A OFF     |
|                                                        | 0 | 1               | 0 | 1 | E          | e   | U   | u   | B ON      |
|                                                        | 0 | 1               | 1 | 0 | F          | f   | V   | v   | B OFF     |
|                                                        | 0 | 1               | 1 | 1 | G          | g   | W   | w   | RIGHT     |
| When<br>MSB = 1<br>represents<br>8 negative<br>numbers | 1 | 0               | 0 | 0 | H          | h   | X   | x   | LEFT      |
|                                                        | 1 | 0               | 0 | 1 | I          | i   | Y   | y   | FORWARD   |
|                                                        | 1 | 0               | 1 | 0 | J          | j   | Z   | z   | BACK      |
|                                                        | 1 | 0               | 1 | 1 | K          | k   | [   | {   | IDLE      |
|                                                        | 1 | 1               | 0 | 0 | L          | l   | \   |     | SPEED 1   |
|                                                        | 1 | 1               | 0 | 1 | M          | m   | ]   | }   | SPEED 2   |
|                                                        | 1 | 1               | 1 | 0 | N          | n   | ^   | ~   | BRAKE     |
|                                                        | 1 | 1               | 1 | 1 | O          | o   | -   | DEL | POWER ON  |
| Column                                                 |   | 1               | 2 | 3 | 4          | 5   | 6   | 7   | 8         |
| ASCII bits                                             |   | 4321            |   |   | 5, 6, 7    | 110 | 001 | 011 | 101 111   |

**Figure 6-5: Digital signals can represent numbers, letters, special characters, commands, and so forth.**

#### Example 4. Arithmetic Shift for Recirculation

Show an example, using an 8-bit word, of how a right recirculate shift of the same number as the bits in the word reinserts the same word in a register after use of the word.

**Solution:**

 

#### Parallel vs. Serial

One can see the parallel transfer of information is fastest because it takes significant time to shift out the bits for identification in a serial transfer. However, there is a significant tradeoff in hardware of increased circuitry, increased interconnections, increased power dissipation, and so forth. Serial operation calls for only one detection circuit at the LSB or MSB position to identify the bits. Parallel operation requires a circuit for each bit so the bits can be identified all at the same time. This multiplication of circuits, interconnections, more power occurs throughout the system.

The trade off then is one between speed of operation versus amount of hardware. But IC processing, device and circuit technology is having a tremendous impact on this tradeoff, as discussed in more detail in *Chapter 8*. The advances by ICs in density per chip, faster operating speeds and lower power operation and new circuit protocols are reducing the separation in this tradeoff and serial operation is gaining in use.

Digital Signal Representations

*Figure 6-5* details that binary bits in digital information can commonly represent numbers, letters, characters and commands. A 4-bit binary code is shown that can represent 16 different entities. The 16 different entities can be the numbers from 0 to 15 (1<sup>st</sup> column); or they can be eight positive numbers from +0 to +7, and eight negative numbers from -0 to -7 (2<sup>nd</sup> column). As explained, the MSB of the code is used to tell whether the number is positive or negative. Or the 16 different codes can be used to identify the numbers from 0 to 9 and six special punctuation characters (3<sup>rd</sup> column). Or the 16 different codes could be used to identify 16 different commands (8<sup>th</sup> column).

In order to identify more characters and symbols, more bits must be added to the code. As an example, *The American Standard Code for Information Interchange* (ASCII), mentioned briefly in *Chapter 1* and contained in its complete form in *Chapter 8*, uses a 7-bit code. It identifies 52 upper and lower case alphabetic characters, 10 numbers from 0 to 9, 34 special data transfer and Teletype commands, and 32 other special characters for a total of 128.

Columns 4, 5, 6 and 7 of *Figure 6-5* are the 52 upper and lower case alphabetic characters and other special symbols that are identified in the ASCII code. Column 3, mentioned previously, is also used in the ASCII code. To fill out the 7-bit code, column 3 has bits 5, 6 and 7 at 110, and columns 4, 5, 6, and 7 have them at 001, 011, 101, and 111, respectively. As the combination of the 5, 6, and 7 bits change, the identities of the 16 codes change to new characters, numbers or symbols.

Example 5. ASCII Code

Identify what the given 7-bit codes represent using *Figure 6-5*.

Solution:

| Code | Bit | 7 | 6 | 5 | 4 | 3 | 2 | 1 | Data Represented |
|------|-----|---|---|---|---|---|---|---|------------------|
| 1.   |     | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 5                |
| 2.   |     | 1 | 0 | 0 | 1 | 0 | 1 | 0 | J                |
| 3.   |     | 1 | 1 | 0 | 0 | 1 | 1 | 1 | g                |
| 4.   |     | 0 | 1 | 1 | 1 | 1 | 1 | 1 | ?                |

What has been demonstrated is that within different digital systems, the binary information can represent many different things—numbers, characters, symbols, commands, instructions, and so on. System designers will define how the codes are used in particular systems.

Clock, Timing and Control Signals

As stated previously, a computer program is a series of steps that a digital processor must execute in sequence in order to accomplish a task dictated by the program. These steps in sequence occur at particular set times dictated by the timing and control signals. Within each step, instructions are dictating how electronic circuits are operating to perform the functions called for by the program. The instructions occur at specific times and the circuit operation occurs at specific times controlled by the timing and control signals.

## Clock

The heart of the timing circuits is the clock. Its source is usually a crystal-controlled oscillator that generates signals at a very precise frequency. Its signal output is formed into rectangular pulses that have very fast rising and falling edges. Typical pulses are shown in *Figure 6-6a*. The rising and falling edges of the clock pulse provide precise times for controlling electronic circuit action. The clock may have just one series of pulses like phase 1 ( $\Phi_1$ ), or it may have additional phases as shown in *Figure 6-6a*. The additional phases provide additional timing signals for the control of circuits. As shown in *Figure 6-6a*, some of the circuits controlled by the clock trigger on the rising edge of the clock pulse, while other circuits trigger on the falling edge of the pulse. Such alternatives in the triggering of circuits provide a wide selection and flexible means for timing the operation of electronic circuits.

## Gated Latch

A specific example of how electronic circuits are timed is shown in *Figure 6-6b*. The electronic circuit shown is called a gated latch. It is used for temporary storage of digital data. The inputs to the gated latch are the binary signal D (either 1 or 0), and the clock. The outputs are Q and Q', which are complementary to each other—if Q = 1, Q' = 0 or vice versa. A signal that appears on D is only stored in the latch and appears on Q after it is “clocked in,” i.e., the clock has appeared and has timed in the D signal. As shown in *Figure 6-6b*, Q only changes after D changes and a clock signal times the change into the latch.

The latch receives its name from the fact that it is a temporary storage electronic circuit that latches on to data and holds it. The gated latch means that data is gated in at a particular time.

 


Figure 6-6: Clock signals for timing and control

TEAM LRN

A truth table, shown in *Figure 6-6b*, identifies the output Q and Q' values for each D input value. It identifies the state of the signals before and after the clock.

### AND Gate Control

Another example of signal timing is shown in *Figure 6-6c*. Here a 2-input AND gate is used to time a control signal. The control signal required tells a memory to read information from memory. The address of the information has been received by the memory and decoded prior to the receipt of the control signal. An AND gate is used to provide the memory read signal at a precise time. As the truth table shows, both inputs to the AND gate must be a 1 for the output to be a 1. If both or one input is a 0, the output is a 0. By placing the memory read signal on the A input to the AND gate, when it is a 1, the memory is to be read. However, the control signal to actually tell the memory to read will not occur on the output of the AND gate until the clock signal is a 1. As a result, the memory is read at a precise time determined by the clock. The read signal on the input to the AND gate overlaps the clock signal in time, and can vary significantly in time position in relationship to the clock and still be timed correctly. The AND gate output, the memory read pulse in this case, turns out to be the same width as the clock pulse.

The fact that a clock may have different phases adds to the flexibility of the timing and control signals. For example, the clock used in *Figure 6-6b* might use Phase 2, while the clock used in *Figure 6-6c* might be Phase 4. This demonstrates the flexibility, mentioned previously, that a designer has to time the system circuits.

### Interrupts

A signal that controls a digital processor at unexpected or random times is called an interrupt. It interrupts the digital processor from what it is doing and directs it to do something different, as indicated by the interrupt signal. A STOP signal terminates whatever the processor is doing. It usually occurs at random times depending on the need to shut down the processor. Or maybe the processor is following a program and input signals are required. When the inputs are available, the input circuits notify the digital processor that the inputs are present. This initiates an interrupt to the processor, which halts what it is doing and inputs the data. After the data is inputted, the processor continues from the place it was interrupted. The CPU keeps track of where the processor is when the interrupt occurred.

Similar action occurs at the outputs. The processor is required by the program to output data to an external unit. The processor addresses the I/O and selects an output. The output circuits send an interrupt to the CPU to signify that the output is ready. The interrupted processor switches to a routine to output the data. When the transfer to the output is complete, the processor returns to the program location directly after the location at which it was interrupted.

The application of a digital processor may be dictated by its response to an interrupt. Some processors respond very quickly to interrupts so that the overall performance to execute its program and complete a task is not affected. While other processors may be slow to respond to interrupts, and, therefore, if an application depends on many interrupts, the overall performance of the processor will be slowed a great deal. The ultimate speed at which the processor can accomplish the task is severely limited. Some digital processors only respond to an interrupt when they want to, not randomly or unexpectedly. Most modern digital processors respond quickly to interrupts that occur at random and unexpected times.

### Status Bits


Digital processors operate using control signals derived from the condition of check bits called status bits. Status bits are stored in a register. A register is a chain of latches strung together to temporarily store a set number of bits; as an example, a 16-bit register stores 16 bits. Most registers store the number of bits in the word being used throughout the digital system. The status register is somewhat different. It holds a variety

of different bits where the state of each bit is somewhat independent of the other bits in the register. Many of the bits are set independently and their value depends on the result of a particular processor operation. For example, what was the sign of a number as a result of an arithmetic operation—positive or negative? A status bit is set after the operation is executed to indicate the result. Was the result of an arithmetic operation greater or less than zero? A status bit is set to indicate the result. Was there a carry or a borrow when an arithmetic operation was performed? Is the number too large for the digital system to handle? The setting of status or condition bits after such operations, and the checking of the bits by the processor, contribute to the control of the operation of the digital processor as it executes its program.

### Example 6. Status Register

The N bit of a status register is set when the result of an arithmetic operation is negative. Show an example of how this occurs.

**Solution:**

 

### More About Software

Refer again to *Figure 6-4* for a short review. The digital information flowing through a digital processor flows as a given combination of bits—a 32-bit address code, a 16-bit instruction code, or an 8-bit character code. Circuits that identify and decode the digital information must identify the value of each bit (either a 1 or a 0) and act as a result of the value to decode the information. As stated previously, the program that the processor follows is a series of instructions in sequence. Each instruction has a given number of bits and a unique code for a particular instruction. The instructions come from memory to the processor over the data bus. Inside the processor the instructions are stored temporarily in the instruction register so that the instruction decoder circuits can decode them. The decoder evaluates the bits and identifies the action the processor must take to execute the instruction.

Humans write the computer programs. The instructions to the computer must be written in a language that humans understand; yet the instructions that the computer follows must be in digital codes that the computer understands. A conversion is required from the human language to the digital codes that the machine (processor) understands. The digital code that the machine understands is called *machine code*. A computer program written in machine code is called a *machine-language program*.

### Machine-Language Programs

Humans can write programs in machine language. To do so, the programmer writes the program directly in the digital codes that the machine understands. No conversion is necessary. The machine can decode the instructions directly and execute them to accomplish the task required. However, the task is extremely difficult, tedious and time consuming, and if errors are made, and they will be regularly, it becomes an even more difficult and tedious task to find the errors and correct them.

### Assembly-Language Programs

In order to make it easier to write the programs, the manufacturers of digital processors have designed their processor to respond to instructions that are closer to human language. These instructions are called *assembly-language instructions*. They are easier to understand than machine code but require the

manufacturer to provide a program to convert the assembly-language instructions into machine code. Such a program is called an *assembler*. A computer is much more accurate in doing the conversion, and by processing an assembly language program for a particular processor using its assembler, all the instructions are converted very accurately into machine code for that processor.

Mnemonics

The operation or action that the assembly-language instruction causes the processor to perform is identified by an abbreviation called a *mnemonic*. The abbreviation used for the mnemonic gives a strong suggestion to the programmer what the instruction does. *Figure 6-7a* shows an example of arithmetic instructions and their directed actions, and gives the mnemonic that represents each of the instructions. The mnemonic is a short two or three letter symbol that identifies to the programmer the processor action caused by the instruction. *Figure 6-7b* gives an idea of what other types of instructions may be available in digital processors.

| Arithmetic     | Mnemonic       | Action                                 |
|----------------|----------------|----------------------------------------|
| Add            | A or AD or ADD | Addition of two binary codes           |
| Subtract       | S or SU or SB  | Subtraction of two binary codes        |
| Multiply       | MPY            | Multiply two binary codes              |
| Divide         | DIV            | Divide two binary codes                |
| Absolute Value | ABS            | Take absolute value of a binary number |
| Negation       | NEG            | Change sign of a binary number         |
| Shift          | ROL or ROR     | Shift left or shift right              |
| Increment      | INC or INR     | Add 1 to binary code                   |
| Decrement      | DEC or DCR     | Subtract 1 from binary code            |

a. Example of mnemonics for arithmetic instructions

| Logical | Data Movement | Branch        | Comparison   |
|---------|---------------|---------------|--------------|
| AND     | Move          | Unconditional | Less than    |
| OR      | Load          | Conditional   | Greater than |
| NOT     | Store         | Subroutine    | Equal        |
| XOR     |               |               |              |

b. Examples of other processor instructions

Figure 6-7: Examples of digital processor instruction set

Operands

In an assembly-language instruction, the instruction itself describes the operation to be performed, but does not say what is to be operated on; therefore, *operands* (what is to be operated on) must be added to the instructions. For example, the instruction:

```
Mov A,B
```

The mnemonic MOV means that a move operation is to be performed and the operands are register A and register B. The contents of register A are to be moved to register B. Suppose that register B is the program counter; therefore, it contains the memory address of the next instruction of a program or subroutine. By loading register A with the address of the first instruction of a program, moving the contents of register A to register B a new program is started. Incrementing register B (subtracting one from its contents) with the instruction:

```
Inc B,
```

causes the processor to step to the next instruction. After the instruction is executed, the program loops back to the Inc B instruction and the processor steps to the next instruction. The processor steps through addresses of the instructions in sequence to execute the program.

## Sophisticated Programming Languages

The writing of a computer program to perform a task consists of organizing the digital processor instructions into the correct sequence. It is a paper process that doesn't require the building of any hardware, but just understanding the processor's instructions and using them to manipulate existing hardware to perform the task required. Thus, programs are called *software*, and people that write programs are called software engineers or just programmers. It is the objective of programmers to write their programs in a language as close to human language as possible. They would also like to learn a particular programming language and not be restricted to using it only for one processor. They would like to apply their knowledge of the language to other processors solving other application problems. To satisfy this need, sophisticated programming languages have been developed.

Sophisticated programming languages are a step up and beyond assembly-language programming. They are, once learned, used for writing many different programs, using different processors. Such languages are referred to as high-level languages because they are somewhat general purpose because they are used to program different processors.

Whatever high-level language is used one thing is certain, the program must be converted to machine-language code. In earlier times this was a two-step process. First a program called a *compiler* converted the high-level language to assembly language. Then, an assembler was used to convert the program to machine code. Today most compilers convert the high-level language directly to machine code. In addition, many digital processors are members of a family of processors; the compiler for a particular processor usually handles the whole family of processors.

### Software Summary

Figure 6-8 provides a summary of programming. A digital processor can be programmed directly in machine language, but it is very tedious and difficult to find errors. Or it can be programmed in assembly language, put through a specially designed program (an assembler) that converts the program to machine code. Or it can be programmed using a sophisticated high-level general-purpose language. The program must be put through a specially designed program (a compiler) that converts the high-level language instructions into machine code for the particular processor used. Fortran was an early high-level language. Today, "C", "C+", UNIX, JAVA are names of sophisticated languages for writing programs.

 


Figure 6-8: Programming computers

## How Parts of a Processor Perform Their Functions

### ALU—Arithmetic Logic Unit

The discussion now switches to how various parts of a processor perform their functions. The first of these is the arithmetic logic unit (ALU). An arithmetic function performed by the ALU is addition, shown in Figure 6-9. The central electronic circuit used for addition is an adder, shown in Figure 6-9a. The full-adder has three inputs—the two binary numbers to be added and a carry input. Figure 6-9a shows not only the



 


Figure 6-9: The addition function

full-adder block diagram, but also its truth table. A truth table, remember, catalogs the state of the outputs for all the states of the inputs. If A or B or C<sub>i</sub> is a 1, the sum bit will be a 1. When A and C<sub>i</sub> or B and C<sub>i</sub> or A and B are a 1, the sum bit is a 0 and C<sub>o</sub> will be a 1. When A and B and C<sub>i</sub> are all 1s, the sum bit is a 1 and C<sub>o</sub> is a 1.

Figure 6-9b shows an 8-bit adder and the addition of two 8-bit binary numbers A and B. Note how the C<sub>o</sub> output of one stage of the adder becomes the C<sub>i</sub> input to the next stage to the left. The example shows how the carry bit is generated and propagates to determine the sum bit at the next stage. The speed of operation of the adder is determined by how long it takes the carries to propagate through the adder. Using the adder multiple times, plus shifting, provides the multiplication function. Subtracting is performed by adding the one's (1's) complement of one of the binary numbers instead of the number itself, and multiple subtractions, plus shifting, results in a division function.

## ALU—Logic Functions

Figure 6-10 shows three logic functions that are normally available in an ALU. Using A and B 4-bit binary numbers as examples, the logic operations are performed bit by bit giving the result C from LSB to MSB. A 1 appears as the result for the AND function only when A and B are a 1. A 1

appears as the result C when A or B or both are a 1 in the OR function. The complement of the input—a 1 if input is a 0, or a 0 if input is a 1—will appear as the result C for the NOT function. The electronic circuit that performs the NOT function is called an inverter.

An example of using the OR function to set particular bits in a binary number to a particular value is shown in Figure 6-10b. In the 8-bit binary number for A, 01110110, bits b<sub>0</sub> and b<sub>3</sub> and b<sub>7</sub> are 0. The program

 


Figure 6-10: Logic functions



requires that bits  $b_0$  and  $b_3$  be set to a 1. By performing an OR function between A and B, where B is the binary number 00001001, the result C will have bits  $b_0$  and  $b_3$  set to a 1. The bits that were 1s in B will be set to a 1 in the result C.

## Memory and Input/Output

Figure 6-11a shows the typical interface between a microprocessor and memory. This corresponds to what was shown in Figure 6-1, but details it just for memory. The address bus carries the binary code put out by the microprocessor for the address of information in memory. The memory size determines the number of bits in the code. The data bus will either have data on it that is put there by the microprocessor to store in memory (write to memory), or it will have data or instructions that come from the address location (reading from memory) to the microprocessor. Whether the memory is being written to or read from is controlled by the read/write signal. In addition, whenever memory is to be used, whether writing or reading, an enable signal is sent to memory to activate it. The read/write and enable signals are timed control signals operating at precisely designed times.

 
 


Figure 6-11: Data to and from memory and input/output

Input/output or I/O circuits operate very similar to memory as shown in Figure 6-11b. The microprocessor sends out an I/O address on the address bus to specify which I/O is to be used. At the same time, a control signal tells the I/O that it wants to input data to the microprocessor over the data bus; or that it wants to output data that the microprocessor is placing on the data bus. As with memory, timed control signal enables the I/O circuits. They are not active until the enable signal arrives.


Input/output or I/O circuits operate very similar to memory as shown in Figure 6-11b. The microprocessor sends out an I/O address on the address bus to specify which I/O is to be used. At the same time, a control signal tells the I/O that it wants to input data to the microprocessor over the data bus; or that it wants to output data that the microprocessor is placing on the data bus. As with memory, timed control signal enables the I/O circuits. They are not active until the enable signal arrives.

## Addressing Modes

Program instructions tell a digital processor what to do, where to find the information it is to use with the instruction, and where to put the result after the instruction is executed. Addresses or addressing is needed to direct the processor to the correct location. *Addressing modes* are the means by which the instruction indicates the address. They are the designed ways that the instruction tells the processor how to locate the information it needs to use with the instruction. There are several common addressing modes for digital processors. Five different ones are shown in Figures 6-12, 13, 14, 15 and 16.
 
### Immediate Addressing

Immediate addressing is diagrammed in Figure 6-12. The program counter contains a memory address that points to the operation code (op code) of the instruction—the operation the instruction wants the processor to perform. Following immediately after the op code, in the next memory location, is the data on which the instruction will operate. So if the instruction is addressed with immediate addressing, the code that describes the operation to be performed is in the memory location addressed by the contents of the program counter, and the data is in the next memory location. There is relatively little decoding. The instruction knows immediately where the data (operand) is located.




The op code is contained in the memory location pointed to by the PC followed, in the next memory location, by the data that is to be used.

Figure 6-12: Immediate addressing

## Register Addressing

Figure 6-13 diagrams register addressing. Here the data is not contained in memory locations but in registers. The instruction contains the op code and specifies in which register the source data is located and, if need be, the register for the destination data.

 


The source and destination data are contained in registers. The instruction contains the op code and specifies a register as a data location. In the case shown, data is contained in a register for both the source and destination.

Figure 6-13: Register addressing

## Register Indirect Addressing

Figure 6-14 diagrams register indirect addressing. In register indirect addressing, instead of specific registers containing the data to be operated on as in Figure 6-13, now the specific registers contain the memory address of the data. Thus, loading different memory locations in registers causes the processor to operate on different data stored in memory.

 


Instead of the register containing the data as in register addressing, the register contains the memory address of the data. Thus, by loading the register with different memory locations, different data is operated on by the instruction.

Figure 6-14: Register indirect addressing

## Indexed Addressing

Figure 6-15 diagrams indexed addressing. The next memory location after the op code contains an index. The address of the data to be used is the sum of a value in a register and the value of the index. The instruction is used separately for the source and for the destination. Indexed addressing is used extensively for data that is grouped together in memory. The program can be modified quickly to select a different set of data by changing the index in the instruction.

 


For index addressing, the address of the data is the sum of a value contained in a register and the value of the index. The selection of data addresses that appear in groups can be modified quickly by changing the index.

Figure 6-15: Indexed addressing

**Example 7. Register Indirect Addressing**

Show an example of register indirect addressing.


**Solution:**

 

The program counter points to the memory address where the instruction MOV @R1,@R2 is located. R1 and R2 are register numbers and the @ sign indicates that the contents of the register is the address in memory where the information on which the instruction is to operate is located. The instruction, with MOV as the op code, says move the contents of the memory location whose address is the contents of R1 (the source) to the memory location whose address is the contents of R2 (the destination).

**Direct or Symbolic Addressing**

Figure 6-16 diagrams direct or symbolic addressing. In immediate addressing of Figure 6-12, the memory location following the op code contained the data to be operated on. In direct or symbolic addressing, the next location in memory after the op code is an address in memory that contains the data.

 

As with immediate addressing, the instruction op code is contained in the memory location, but now the next word does not contain the data for the instruction, but contains a memory address for the data.

**Figure 6-16: Direct or symbolic addressing**

Instruction sets for different processors use specific symbols and notations for their instructions and for their addressing modes. They usually are specific to the particular processor. In Chapter 7, there will be further discussion of the addressing modes used for the MSP430 family of microcontrollers.

**Summary**

This completes the discussion about the basic operation of a digital processor, some of its specific functions, and how the processor is made to do what is instructed by a program to perform a desired task. In the next chapter, the discussion centers on the details of programming the processor.

## Chapter 6 Quiz

1. A digital processor, more commonly called a digital computer, has a unit that is the brain of the system called the:
  - a. I/O—input/output.
  - b. permanent memory.
  - c. temporary memory.
  - d. CPU (central processing unit).
2. Each digital processor is manufactured to respond to:
  - a. a wide variety of different sets of instructions.
  - b. a particular set of instructions.
  - c. only one or two instructions.
  - d. only input/output instructions.
3. A digital processor responds to a program that is:
  - a. designed to randomly operate the processor in many different sequences.
  - b. always changes every time it runs the processor.
  - c. a set of operations in a particular sequence to accomplish a task.
  - d. not needed by the processor for most tasks.
4. The instruction/data bus is used:
  - a. to send addresses to locate instructions and data to be delivered to the CPU.
  - b. to identify inputs and outputs to receive or output data for the CPU.
  - c. to send timing information throughout the system.
  - d. a and b only above.
  - e. c only above.
5. Clock signals in the digital processor:
  - a. precisely control the transfer, manipulation and storage of information throughout the processor.
  - b. must be very accurate in time.
  - c. are a series of repetitive pulses that have fast rise and fall times.
  - d. all of above.
  - e. a and c only above.
6. Power systems in digital processors:
  - a. must have very accurate voltage regulators and good power dissipation control.
  - b. require no precise voltage or current control.
  - c. require little concern for power dissipation.
  - d. operate with high voltage and high current.
7. The devices that have contributed most to low power dissipation in digital processors are:
  - a. power transistors.
  - b. bipolar logic transistors.
  - c. CMOS—complementary-metal-oxide-semiconductor—integrated circuits.
  - d. a mix of bipolar and MOS devices.
8. The data bus carries to memory a digital code representing:
  - a. the instruction address and the data address.
  - b. only the instruction address.
  - c. only the data address.
  - d. none of the above.

9. The arithmetic logic unit (ALU) in the CPU:
  - a. provides the I/O capabilities.
  - b. provides the clock capabilities.
  - c. provides the storage capabilities.
  - d. provides the logical, computational, and decision making capabilities.
10. Read-only memory (ROM), random-access memory (RAM) and registers are:
  - a. logical circuits contained in the CPU.
  - b. types of memory that are or maybe contained in a CPU.
  - c. data transmission circuits contained in a CPU.
  - d. I/O circuits contained in a CPU.
11. A microcontroller unit (MCU):
  - a. is an industrial control computer made up from individual ICs.
  - b. is the smallest possible microcomputer.
  - c. is a microcomputer IC that is adapted to the industrial control market.
  - d. is a computer made up of individual ICs, but designed for low-power use.
12. The MSB (most significant bit) of a word is:
  - a. is the second bit in the code representing the word.
  - b. is the left-most bit in the code representing the word.
  - c. is the right-most bit in the code representing the word.
  - d. is the middle bit in the code representing the word.
13. In a parallel data transfer:
  - a. all bits arrive at a point at the same time.
  - b. all bits do not arrive at a point at the same time.
  - c. all bits are delayed one bit at a time.
  - d. all bits arrive at a point one after another.
14. In a serial data transfer:
  - a. all bits arrive at a point at the same time.
  - b. all bits are collected, delayed, and then arrive at the same time.
  - c. all bits are delayed, then arrive at a point at the same time.
  - d. all bits arrive at a point one after another in sequence.
15. The ASCII code can identify:
  - a. numbers only.
  - b. letters only, not special characters.
  - c. numbers, letters, special characters, commands.
  - d. commands only.
16. Clock signals inside a digital processor:
  - a. may trigger electronic circuits only on the falling edge.
  - b. may trigger electronic circuits into action on either the rising or falling edge of the clock pulse.
  - c. may trigger electronic circuits only on the rising edge.
  - d. don't trigger electronic circuits on the rising or falling edges.
17. An interrupt signal to a digital processor:
  - a. speeds up the operation of a digital processor.
  - b. controls a digital processor at unexpected or random times.
  - c. acts just like any other digital processor control signal.
  - d. none of the above.

18. A mnemonic is a:
  - a. short two or three letter symbol that represents a program instruction.
  - b. random set of letter symbols that varies continuously.
  - c. long set of letter symbols that is an instruction in itself.
  - d. symbol that has no relationship to assembly-language programming.
19. Programs written in high-level languages:
  - a. can be written for different processors using the same language.
  - b. must be converted to machine code to run the processor.
  - c. use a compiler to convert the high-level language to machine code.
  - d. all of above.
  - e. c only above.
20. Addressing modes for a digital processor:
  - a. are always immediate addressing.
  - b. are the designed ways the instruction tells the processor what to do.
  - c. are the means by which the instruction indicates the action to be taken by the processor.
  - d. c only above.
  - e. b and c only above.

Answers: 1.d, 2.b, 3.c, 4.d, 5.d, 6.a, 7.c, 8.a, 9.d, 10.b, 11.c, 12.b, 13.a, 14.d, 15.c, 16.b, 17.b, 18.a, 19.d, 20.e.

# Examples of Assembly-Language Programming

## Introduction

Many times the easiest way to understand how to do something is to work with examples. That is the subject of this chapter. By looking at small subprograms that have been written to accomplish specific tasks, the reader will be introduced to assembly-language programming. The objective is to provide a base of understanding of how an assembly-language program is formulated so that programs can be deciphered, at least to obtain a “feel” for what the program is trying to accomplish. In no way will this chapter be a thorough coverage of assembly language, its format, its detail, its uniqueness, but, hopefully, by taking small segments of programs and discussing them, line by line, enough information will be transmitted to accomplish the basic understanding desired.

## A Processor for the Examples


In order to be specific about the programs discussed and the tasks, a Texas Instruments MSP430 Family microcontroller has been chosen to use for the programming examples because it is readily available, well-supported with documentation and applications information, and has relatively inexpensive evaluation tools. The family of microcontrollers is designed specifically for industrial control, instrumentation, and measurement tasks with low-power, extended battery-life applications as prime design objectives. These specifications are not necessarily important to its choice for this chapter. Rather, the easy-to-understand architecture, instruction set, and family structure contributed significantly to the selection.

## About the MSP430 Family

In Texas Instruments’ words, “The MSP430 devices constitute a family of ultra low-power, 16-bit RISC microcontrollers with an advanced architecture and rich peripheral set. The architecture uses advanced timing and design features, as well as a highly orthogonal structure to deliver a processor that is both powerful and flexible.” The architecture is called “von Neumann” since all program, data memory and peripherals share a common bus structure. RISC means reduced instruction set computer, and defines a specific design approach for the microcontroller. There are only 27 core instructions, which, through the technique of combining core instructions—called emulation—is expanded into a set of 51 instructions. The core instructions are built into hardware, while the emulated instructions are formed by the assembler (the program that interprets the assembly-language mnemonics and produces machine code).

## Family Block Diagram

A MSP430 Family system block diagram is shown in *Figure 7-1*. Note the 16-bit memory address bus (MAB), the 16-bit memory data

 

**Figure 7-1: MSP430 family block diagram**

*Courtesy of Texas Instruments Incorporated.*

bus (MDB), and the bus conversion for the I/O, USART and comparator. In *Chapter 10*, the MSP430F1232, part of a family of MSP430F12XX devices, will be used in an application. How the MSP430F12XX devices vary in the family is shown in *Table 7-1*.

### MSP430F12XX Devices of the Family

Memory

| 430 Device | Main | Flash | RAM  | I/O(8) | BOR | WDT | TA | C | USART | ADC    |
|------------|------|-------|------|--------|-----|-----|----|---|-------|--------|
| F122       | 4kB  | 256B  | 256B | 3      |     | X   | X  | X | 1     | slope  |
| F123       | 8kB  | 256B  | 256B | 3      |     | X   | X  | X | 1     | slope  |
| F1222      | 4kB  | 256B  | 256B | 3      | X   | X   | X  |   | 1     | SAR 10 |
| F1232      | 8kB  | 256B  | 256B | 3      | X   | X   | X  |   | 1     | SAR 10 |

**Table 7-1: Devices of the MSP430F12XX family**

The MSP430F12XX devices have program memory that is Flash memory. The devices are identified with a F in the device number as shown in *Table 7-1*. The Flash memory, which is made up of a large main memory and a smaller information memory, provides in-system programmability that permits flexible code changes, and, for remote systems that are battery operated, field upgrades. Flash memory is electronically erasable programmable ROM (EEPROM), and is programmable and erased by applying a voltage. The MSP430F12XX devices vary in program memory size from 4 kB to 8 kB, and all have the same size RAM. They have three 8-bit I/Os, a watchdog timer (WDT), and 16-bit PWM timer (TA), a USART communication interface, and ADCs. Some have no comparators (C), some have brownout reset (BOR), and the ADC varies from slope to SARs. They are packaged in 28-pin packages. The brownout reset is a function that resets the microcontroller when the power supply voltage reaches a critical low value. When the power supply voltage is re-established, the microcontroller starts again from the RESET condition.

### MSP430 Family Characteristics

The MSP430F1XXX family, which extends through the F13x, F14x, F15x, and F16x devices, includes devices with more USARTs and timers, hardware multipliers, 12-bit ADCs, an I<sup>2</sup>C communications bus, and SVSs—supply voltage supervisors. These devices are in 64-pin packages.

Another family group, the MSP430F4XX devices, extends the family into 64-pin and 80-pin packages. The devices have up to 60 kB of program memory and 2 kB of RAM, and most have 12-bit ADCs. All have LCD drivers—from 96 to 160 segments.

A segment of the family is based on ROM programming, the MSP430C or P3XX devices. They have similar LCD drivers to the F4XX devices, but do not have Flash memory. There are devices with 32 kB of program memory and 1 kB of RAM, but the most exotic have 6-channel, 14-bit ADCs that are packaged in 64-pin packages. Other devices are in 100-pin packages and have 32 kB of program memory, 1 kB of RAM, an 8-bit interval timer, a 16-bit timer A, a USART, and a hardware multiply. Such a variety of devices allow the designer of control systems a wide choice of design options.

### The CPU

The CPU for the family is the same. As mentioned previously, it is a 16-bit RISC CPU. It consists of a 16-bit ALU, 16 registers and instruction control logic. The register arrangement is shown in *Figure 7-2a*. Note the common memory address bus (MAB) and memory data bus (MDB). Four of the registers are for special purposes: program counter, stack pointer, status register and constant generator. The rest are



general-purpose registers. The constant generator supplies instruction constants, and is not used for storage. The sixteen fully-addressable, single-cycle 16-bit registers and orthogonal architecture provides versatility and simplicity in system applications.

## Program Memory and Data Memory

A map of memory available for the MSP430 family is shown in Figure 7-2b. There are 64KB (65,536) of addressable memory spaces divided over the address spaces from 0 to hexadecimal 0FFFFh (1111 1111 1111 1111 in straight binary). The special-function registers and peripheral module addresses are from 0 to 01FFh. Recall that an h after the address notation means it is in hexadecimal format and that 01FFh is really a 16-bit word with bits of 0000000111111111. In hexadecimal notation, when the hexadecimal address starts with the MSB of A,B,C,D,E or F, a zero is placed in front of the hexadecimal value to make sure the address is identified correctly, for example, 0BE14h.

The memory addresses (memory space) from 0200h to 0FFFFh are shared by data and program code memory. The space from 0FFE0h to 0FFFFh is reserved for a table of interrupt vectors in Flash/ROM (Flash for F devices) and more Flash/ROM is devoted to program, branch control tables and data tables below the address 0FFDFh. The remaining addresses are used for Flash/ROM and RAM (random access memory) and are used for program and data storage.

Words of data, which occupy 16 bits or 2 bytes, are only located at even addresses, while bytes can be located at odd or even addresses. If a data word is located at an even address, the low byte is at the even address and the high byte is at the next odd address. The typical arrangement is shown in Figure 7-2c. Word A shows the actual bits of the high and low bytes, while word B is just identified by the position of the “high byte” and the “low byte.”

Note also that if a peripheral module is a 16-bit module, its address will be between 0100h and 01FFh. If it is an 8-bit module, its address will be between 010h and 0FFh. The addresses from 0 to 0Fh are reserved for special-function registers, SFRs. The functions served by the various portions of memory are shown

 


Figure 7-2: CPU, registers and memory map  
Courtesy of Texas Instruments Incorporated

in *Figure 7-2b*, and shows that some of the functions are only accessible with 8-bit (byte) or 16-bit (word) instructions, while others are accessible with either 8-bit or 16-bit instructions.

Instructions are fetched from program memory with 16-bit addresses, while data memory can be addressed either using 16-bit or 8-bit instructions. Program code can either be in Flash/ROM or RAM because the Flash/ROM and RAM are connected via the same two buses: the memory address bus (MAB) and the memory data bus (MDB). In addition to program code, data can be placed in the Flash/ROM section of the memory map, a significant advantage for data tables.

## Peripherals

The variation of peripherals is one of the major advantages of the MSP430 family. A general overview of the peripheral variations were pointed out in the family discussion, but more specific variations are shown in *Figure 7-1*. Shown are variations of the available I/O ports, as well as a comparator and a USART (Universal Synchronous/Asynchronous Receiver/Transmitter). Within the family, also available are different ADCs, different timers, and even a hardware multiplier. Most of the peripherals operate in byte format, and modules with 8-bit data buses are connected by bus-conversion circuitry to the 16-bit CPU. Most of the peripherals use a 5-bit memory address bus.

## Operation Control and Operating Modes

The contents of the special-function registers, mentioned previously, control the operation of the different MSP430 functions. The bits contained in the register(s) select system operation, enable interrupts, provide information about the status of interrupt flags (caution signals that tell a program whether it can continue or not) and define the operating modes of the peripherals.

Because the microcontroller that is used for the example digital processor has been designed to operate at low

power, and many of its applications are battery powered, there are a number of operating modes specially directed to saving power consumption. Six operating modes, AM through LPM4, are shown in *Figure 7-3*. AM is the active mode where the CPU is powered as well as all other modules that are designated to be active by the program. Modes LPM0 to LPM4 are so-called low-power modes with successively less power dissipated. If the operating mode is one of the LPM modes, anytime the CPU is required by the program, it must be called into the active mode by the program. To simplify the operation for the examples in this chapter, the only modes used will be the active mode and the LPM3 mode.

## Watchdog Timer

There is another component within the MSP430 microcontroller, the watchdog timer that is particularly associated with remote low-power operation. It is shown in *Figure 7-1*. It is called a watchdog timer because its primary function is to perform a controlled system restart after a software problem occurs. This is for system protection in case an application is in a remote battery-operated location and some glitch causes a software failure. After a set time interval, a system reset is generated and the program is restarted. What is important is

| Mode | Status Register Bits |      |        |        | CPU | Clock Functions |                 |                 |                 |
|------|----------------------|------|--------|--------|-----|-----------------|-----------------|-----------------|-----------------|
|      | SCG0                 | SCG1 | OSCOFF | CPUOFF |     | MCLK            | SMCLK           | ACLK            | DCO             |
| AM   | 0                    | 0    | 0      | 0      | ON  | ON <sup>1</sup> | ON <sup>1</sup> | ON <sup>1</sup> | ON <sup>1</sup> |
| LPM0 | 0                    | 0    | 0      | 1      | OFF | OFF             | ON              | ON              | ON <sup>2</sup> |
| LPM1 | 1                    | 0    | 0      | 1      | OFF | OFF             | ON              | ON              | OFF             |
| LPM2 | 0                    | 1    | 0      | 1      | OFF | OFF             | OFF             | ON              | OFF             |
| LPM3 | 1                    | 1    | 0      | 1      | OFF | OFF             | OFF             | ON              | OFF             |
| LPM4 | 1                    | 1    | 1      | 1      | OFF | OFF             | OFF             | OFF             | OFF             |

Notes:

1. Various modules are active as required.
2. If DCO is used as clock source.

**Figure 7-3: Operating modes of MSP430 family**

that if the system is operating properly and the watchdog timer is active, the program must reset the watchdog timer before its time interval expires, otherwise the system will be reset. If the watchdog timer function is not necessary, the timer can be used as an interval timer. Such use is in one of the program examples.

## System Reset

To make sure a system application always starts the same way, a reset of the system is initiated by the turn-on of power, called a power-on reset (POR). There is also another reset, called power-up clear (PUC), that is for resetting if the watchdog timer has expired, or there is some system violation. Reset is considered a system interrupt.

## Interrupts

In *Chapter 6*, an interrupt was described as a signal that interrupts the digital signal processor from what it is doing and directs it to do something different as indicated by the interrupt signal. It may control the digital processor at unexpected or random times.

One of the most common types of interrupts is from one of the peripheral modules, such as an I/O unit. The processor has had to wait on an input until it is available. Now it is available and signals the processor with an interrupt signal, and the processor accepts the input. If another interrupt were to occur simultaneously, the MSP430, as shown in *Figure 7-4*, has an interrupt priority scheme.

The peripheral modules that are nearer the CPU in the connection chain have the higher priority in case two signals were to appear at the processor at the same time. While the interrupt occurs, all other interrupts are blocked by default. For specific devices the modules included have specific hardware positions in the chain. Each device's interrupts are described in an interrupt vector table in the data sheet for the device.

## Oscillators and Clock Generators

Included in the microcontroller is a built-in oscillator that uses only an external crystal. The common oscillator uses a watch crystal and oscillates at 32,768 Hz, but using a higher-frequency crystal, it can oscillate at frequencies from 1MHz to 8MHz. In addition, there is a digitally-controlled oscillator that is digitally tuned. Such flexibility makes it easy to select a particular clock operating frequency.

The MSP430 basic clock system is shown in *Figure 7-5*. For the MSP430F12XX microcontroller used for this chapter, the LFXT1 oscillator is the low/high frequency crystal oscillator mentioned above. The DCO oscillator is a RC-type oscillator and is digitally controlled to adjust the frequency. Other family devices have a second crystal oscillator, XT2, that can oscillate at frequencies from 450kHz to 8MHz.

The main system clock, MCLK, can use either LFXT1 or DCO as its source controlled by the state of the selection bits SELM. By software commands setting the state of the DIVM bits, the source for MCLK can be divided by 1, 2, 4, and 8. The state of the DCOR bit, which chooses either an internal or external resistor, defines the fundamental frequency of the DCO. Then the state of the RSEL bits selects one of

 


Figure 7-4: MSP430 interrupt priority scheme  
Courtesy of Texas Instruments Incorporated


eight nominal frequency ranges defined in the specific device data sheet. The three DCO bits divide the DCO range selected by the RSEL bits into eight frequency steps approximately 10% apart. Because the DCO is a RC-type oscillator, its frequency varies with temperature, voltage and from device to device. The five MOD bits set the conditions to adjust and stabilize the DCO frequency.

The action of the three RSEL bits and the three DCO bits to set the DCO frequency after the fundamental frequency is set is shown in Figure 7-5b. The three RSEL bits, based on their binary value, select one of eight nominal frequency ranges for the DCO. The ranges are defined for a specific device in the device's data sheet. The three DCO bits, based on their binary value, divide the DCO range selected by the RSEL bits into eight frequency steps, approximately 10% apart. Thus, setting the binary value of the RSEL and DCO bits will result in a DCOCLK frequency for the system. The typical ranges and steps are shown in Figure 7-5b.

The auxiliary clock, ACLK, uses LFXT1 as its source, and divides LFXT1 down by 1, 2, 4, and 8 based on the state of the DIVA bits.

The subsystem clock, SMCLK, uses either XT2CLK or DCO as its source, again divided by 1, 2, 4, or 8 based on the state of the DIVS bits. However, when XT2CLK is not present, as is the case for the MSP430x11xx and x12xx devices, an internal connection is made in the MSP430 that connects LFXT1CLK in its place.

 
The choice of which clock system to use is based upon the application. Systems requiring very precise timing with little variation allowed will use the high-frequency crystal oscillators as sources. Systems with very nominal speed and accuracy for the timing and require very low power will use the DCO.



**Note: XT2 Oscillator**

The XT2 Oscillator is not present on MSP430x11xx or MSP430x12xx devices. The LFXT1CLK is used in place of XT2CLK.

a. Clock system block diagram

 

b. Typical DCOx range and RSELx steps

Figure 7-5: MSP430 basic clock system  
Courtesy of Texas Instruments Incorporated

## Timers

Timers are digital counters that use a clock at a set frequency as the source to establish time intervals by counting a certain number of input pulses. Thus, specific time periods can be established either by the number of pulses counted, or by changing the frequency of the pulses.

The timers in the MSP430 family are 16-bit counters that are extremely versatile. Their sources can be programmed to be any one of those shown in *Figure 7-5*. Some of the counters can be programmed to be 8-, 10-, or 12-bit counters. Each timer has capture/compare register blocks that sense when the counter has reached a particular count (capture) and compare the count to a set target. An output signal from the capture/compare block can be used as an interrupt or as an external signal. These timers are particularly useful to keep track of elapsed time, to set time intervals within which specific action occurs or is to occur, and to produce resets, alerts or warnings.

## Addressing Modes

Addressing modes were discussed in general in *Chapter 6*. Now the specific modes used in the MSP430 family will be discussed—the format, the symbols used, and a description of the modes. The seven addressing modes are shown in *Figure 7-6*; note the column **As/Ad**. **As** are bits in an instruction that define the addressing mode used for the source, and **Ad** are bits in an instruction that define the addressing mode used for the destination. In *Figure 7-6*, addressing modes 1, 2, 3 and 4 have bits in the **As** and **Ad** column; therefore, they can be used to address both the source and the destination. Modes 5, 6 and 7 can be used for the source only. Here is a short discussion of each addressing mode:

| As/Ad   | Addressing Mode        | Syntax | Description                                                                                                                       |
|---------|------------------------|--------|-----------------------------------------------------------------------------------------------------------------------------------|
| 1. 00/0 | Register mode          | Rn     | Register contents are operand                                                                                                     |
| 2. 01/1 | Indexed mode           | X(Rn)  | (Rn + X) points to the operand<br>X is stored in the next word                                                                    |
| 3. 01/1 | Symbolic mode          | ADDR   | (PC + X) points to the operand<br>X is stored in the next word.<br>Indexed mode X(PC) is used.                                    |
| 4. 01/1 | Absolute mode          | &ADDR  | The word following the instruction contains the absolute address.<br>X is stored in the next word.<br>Indexed mode X(SR) is used. |
| 5. 10/– | Indirect register mode | @Rn    | Rn is used as a pointer to the operand.                                                                                           |
| 6. 11/– | Indirect autoincrement | @Rn+   | Rn is used as a pointer to the operand. Rn is incremented afterwards by 1 for .B instructions and by 2 for .W instructions.       |
| 7. 11/– | Immediate mode         | #N     | The word following the instruction contains the immediate constant N. Indirect autoincrement mode @PC+ is used.                   |

**Figure 7-6: Addressing modes**

### 1. Register Mode—The symbol is Rn

If register mode addressing is used, the content of the register is the operand. For example, the instruction `Mov R1,R2` means that register addressing is used for both the source, register R1, and the destination, register R2. The contents of R1 are moved to R2. R2 is changed but R1 remains the same. Register mode can be used either for the source or the destination or both.

### 2. Indexed Mode—The symbol is X(Rn)

The X is an index that is added to the contents of Rn to form an address that is either the source of or the destination for the operand. For example, for the instruction `Mov 2(R1),4(R2)`. The operand at the source address (R1 + 2) is moved to the destination address (R2 + 4). The X index is stored in the next word after the instruction; the source in the first word and the destination in the second word. The contents of R1 and R2 are not affected.

### 3. Symbolic Mode—A symbol name such as ADDR

A symbolic name is given to the address of the operand, either the source or the destination or both. For example, the instruction `Mov ADDR,END` says to move the contents at the source address ADDR to the destination address END. The symbol ADDR and END are assigned digital words that are substituted by the assembler to make up the proper address.

### 4. Absolute Mode (&ADDR)

The & symbol is added in front of the operand, &ADDR. The & symbol indicates that the absolute operand address is contained in the word following the instruction. Absolute mode can be used for both the source and the destination. For example, the instruction `Mov &ADDR,&END` says move the contents of the source address ADDR to the destination address END. However, no calculations are involved as for symbolic mode. The absolute address for both the source and destination are in the words following the instruction, the source in the first word, the destination in the second word.

### 5. Indirect Register Mode (@Rn)

The @ symbol is added in front of a register number, @Rn. This is an addressing mode that is valid only for the source. It indicates that the *contents of the source* are to be used *as the address* of the operand. For example, the instruction `Mov @R1,0(R2)` says to move the contents at the source address, the contents of R1, to the destination address. Since indirect register mode cannot be used for the destination, the substitute for the destination operand is 0(R2), which means the destination address is the contents of R2. R1 and R2 are not modified.

### 6. Indirect Autoincrement (@Rn+)

Besides the @ symbol added in front of a register number a plus sign (+) is added after the register, @Rn+. This is the same addressing mode as for the indirect register mode except the source register content is incremented by one for a byte operation and by two for a word operation after the instruction is completed.

### 7. Immediate Mode (#N)

The # symbol is added in front of the operand, usually a constant number, #N. The # symbol, states that the number indicated, which is contained in the word following the instruction, is the source operand. The immediate mode can only be used for source addressing. For example, the instruction `Mov #9, ADDR` says that the constant 9 is to be moved to the destination ADDR (symbolic addressing). When executed, the program counter points to the word following the instruction and moves its contents (the number 9) to the destination ADDR.

## More on MSP430 Control

It will be important to the understanding of assembly-language programming to look further how the MSP430 microcontroller is controlled. One of the principal features of its design is the use of registers to implement the control. The state of a particular bit or particular bits in a register determines the operating condition or action of a particular function inside the MSP430.

### The Status Register

The status register, SR, shown in *Figure 7-7*, is a prime example. It is register R2 of the sixteen 16-bit registers in the CPU shown in *Figure 7-2a*. The status register, R2, has nine active bits; the remaining seven are available for future expansion. The LSB is the zero bit; the eight bit is the MSB. Each of the nine bits has a specific control over the CPU, or its state dictates that a particular action has occurred. For example, the four bit is labeled “CPUOFF.” If the four bit is set (to a 1), the CPU will be off. Program execution stops,



 


Figure 7-7: Status register R2

but the RAM, the port registers and any enabled peripherals stay active. The CPU is awakened when any enabled interrupt occurs.

The five bit, labeled “OSCOFF,” if set (to a 1), the crystal oscillator enters the off mode. The DCO remains ON so the CPU can be running. The RAM contents, the ports, and the registers are maintained. Wake up is possible only through enabled external interrupts.

The three bit is the general-interrupt-enable bit, GIE. If set, all enabled maskable interrupts are handled; if reset (to a 0), all maskable interrupts are disabled, GIE is cleared by interrupts and set by a return from interrupt, RETI instruction, as well as other appropriate instructions. The six and seven bit, labeled SCG0 and SCG1, respectively, determine, through their bit combination, which clock is active. If SCG0 is set (to a 1), the DCO dc generator is turned off; however, this only happens if the DCO is not being used as a source for MCLK or SMCLK. If SCG1 is set, SMCLK is turned off. It must be noted, as discussed in *Figure 7-3*, that the bits OSCOFF, CPUOFF, SCG0 and SCG1 work together to define an operating mode, not independently to provide various control. The eight bit, labeled V, is an overflow bit. It is set when the result of an arithmetic operation overflows the signed-variable range.

The zero, one and two bits are labeled C, Z, and N, respectively. The C or carry bit is set when a byte or word operation called for in an instruction produces a carry. It is cleared if no carry occurs. The Z or zero bit is set if the result of a byte or word operation is zero; if the result is not zero, it is cleared (set to a 0).

The negative bit, N, is set if the result of a byte or word operation is negative, and is cleared when the result is not negative. Instructions in the program will test the C, Z, or N bits and the CPU will respond as directed by the program instructions. Operations as a result of an instruction, or the instruction itself, can set the bits so that the CPU is controlled accordingly.

## Basic Clock System Control Registers

The basic clock system is set up (configured) by using three control registers, the DCOCTL (the digitally-controlled oscillator control register), and the two basic clock system control registers, BCSCTL1 and BCSCTL2. In addition, SCG1, SCG0, OSCOFF and CPUOFF bits in the status register control the operating mode as described. The DCOCTL register and a brief description of its bits and what they control is shown in *Figure 7-8*. The code represented by the state of the DCO bits defines one of eight frequency steps


within the DCO frequency range set by the RSEL bits in the BCSCTL1 control register. This was explained previously (*Figure 7-5*). The state of the five MOD bits set a modulation constant used to adjust the DCO frequency. At power up, the power-up control signal (PUC) loads the DCOCTL register with 060h to set the initial DCO frequency.

The two basic clock system control registers, BCSCTL1 and BCSCTL2, are shown in *Figure 7-9*, along with a brief description of the control affected by the bits of each register. BCSCTL1 controls basic clock system 1 and BCSCTL2 basic clock system 2. Referring to *Figure 7-5* and BCSCTL1 in *Figure 7-9*, the XTS bit determines if the LFXT1 oscillator will operate with a low-frequency or high-frequency crystal to produce the LFXT1 clock source. The states of the DIVA bits determine if clock source LFXT1 is going to be divided by 1, 2, 4 or 8 to produce the clock ACLK. The RSEL bits 0, 1, and 2 determine the nominal frequency range of the DCO as previously discussed for *Figure 7-5b*.


Referring to *Figure 7-5* and BCSCTL2 in *Figure 7-9*, the SELM bit states determine if DCO, XT2 or LFXT1 are going to be the source for the MCLK clock. The DIVM bit states determine if the clock source is going to be divided by 1, 2, 4 or 8 to produce MCLK. Likewise, the 3 bit, the SELS bit, state determines if DCOCLK, XT2CLK or LFXT1CLK will be the source for the SMCLK clock. The DIVS bit states determine if the source to SMCLK will be divided by 1, 2, 4 or 8. The DCOR bit controls whether current is going to be supplied to the DCO from an internal or external resistor to control oscillations. The complete clock system for the MSP430 can be set up initially using instructions to the CPU to set the bits of the DCOCTL, BCSCTL1 and BCSCTL2 registers.

### Watchdog Timer

The WDTCTL register controls the watchdog timer. It is shown in *Figure 7-10*, and a description of the control that each bit applies in a particular state is included. When the watchdog timer function is active, the WDTTMSSEL bit must be 0 to be in the watchdog mode and the WDTHOLD bit must be 0; if WDTHOLD is set, the counting stops.

 

**Figure 7-8: The digitally-controlled oscillator (DCO) control register**

 

**Figure 7-9: Basic clock system control registers**



If the watchdog timer is active, software should periodically reset the watchdog timer by writing a 1 to the WDTCNTCL clear bit to prevent the timer interval from expiring and restarting the system. Setting WDTCNTCL (to a 1) restarts the counter, WDTCNT, at 0000h. The WDTSSEL bit selects the clock source for WDTCNT, when = 0 the source is SMCLK; when = 1 the source is ACLK. The state of the WDTIS bits determines the time interval of the clock, either with SMCLK or ACLK as the source. The code for the time interval is shown in *Figure 7-10*.

 


Figure 7-10: Watch dog timer control register

The five bit, WDTNMI, controls whether a pin, RST/NMI, is a reset input or a nonmaskable interrupt input (NMI). When the state of WDTNMI is a 0, the RST/NMI input is a level-sensitive reset input, and when the state is a 1, it is an edge-sensitive nonmaskable input. When WDTNMI is set to 1, the six bit, WDTNMIES, controls whether the input triggers on the rising (WDTNMIES = 0) or falling edge (WDTNMIES = 1) of the input signal.

## Timer\_A Control Register

There is a 16-bit, general-purpose timer in the MSP430F1232 device used for this chapter, called Timer\_A. Its control register, TACTL, is shown in *Figure 7-11*, with a description of the control each bit applies in a particular state.

 


Figure 7-11: Timer\_A control register

The TASSEL bit states determines the clock source to be used for Timer\_A, either internal clocks ACLK or SMCLK or an external source TACLK. After clock selection, the state of the ID bits control whether the clock source is passed directly to Timer\_A, or whether it is divided by 2, 4 or 8. The state of the MC bits set the mode of the timer as shown. The modes of the timer are further clarified in *Table 7-2*.

| MC1 | MC0 | Mode                                                |
|-----|-----|-----------------------------------------------------|
| 0   | 0   | Stop                                                |
| 0   | 1   | Up (from 0 to value TACCRO)                         |
| 1   | 0   | Continuous (from 0 to 0FFFFh, then restart at 0)    |
| 1   | 1   | Up/Down (counts up to TACCRO value, then back to 0) |

**Table 7-2: Mode of Timer\_A**

To clear the counter, the two bit, TACLR, is set to a 1. The remaining one bit and zero bit control the response to an interrupt generated when Timer\_A reaches a specific value. The interrupt sets a flag, TAIFG, and the TAIE bit enables the interrupt if it is set to a 1 or disables the interrupt if it is reset to a 0.

## Input/Output Control

Previous discussion stated that the I/O ports in the MSP430 could be programmed to be inputs or outputs. For the family device used for this chapter there are three I/O ports, 1, 2 and 3. *Figure 7-12* shows the registers that can be programmed to configure the external pins of the MSP430. There are PxIN input registers; there are PxOUT output registers; there are PxDIR direction registers and there are PxSEL function-select registers.

All I/O ports are initially inputs when the machine powers up. If the zero bit of P1DIR is set to a 1, then the external Pin1.0 will be an output; if its state is a 0, the external Pin1.0 will be an input. Any input signal from pin P1.0, when programmed as an input, will be stored in the zero bit of the P1IN register. When pin P1.0 is programmed as an output by P1DIR, the P1OUT register zero bit is output to P1.0. Correspondingly, the other bits of P1IN and P1OUT will either receive data into their register or output data from their register based on the programming in the P1DIR register.

External pins can be used by other modules rather than I/O ports 1, 2 and 3. The PxSEL bits of the function-select register controls the selection. When the PxSEL bit for a particular pin is set to a 1, that pin will be used by a module other than port 1 or 2 or 3. The data sheet for the particular device, with its package pin layout, will indicate if pins have multiple function capability. When the multiple capability is available, the PxSEL must be configured to select the proper pin function.

To summarize, the PxDIR register bits are set (= 1) to dictate if the external pins of the I/O ports are to be outputs. The initial condition is that all I/O ports are inputs. Any input signal will be placed in the PxIN register(s). Any output pins will receive signals from the PxOUT register(s). If a particular external pin is not to be an I/O output or input from Port 1, 2 or 3, then the bits of the PxSEL register(s) are set to select the function that is to be on the pin. The functions available for the pin are called out on the data sheet for a particular device.

## Further Thoughts

Some further thoughts and concepts need to be examined before an actual assembly-language program is explained. The first of these is symbolic notation.

## Symbolic Notation

Recall that the actual 1s and 0s (machine language) that direct the circuits inside of a digital processor for a particular program must be formulated or coded for each instruction. This has been mentioned previously but it bears repeating. The language used for our programming is assembly language. To convert assembly-language programming to machine language an assembler, a computer program that converts the mnemonic instructions used in assembly-language programs into the 1s and 0s of machine code, is required. The assembler has been developed to recognize symbolic representations such as the mnemonics used for the assembly-language instructions; such as symbolic names used to identify register bits, system commands, system names, or system signals. When the assembler sees the respective symbolic name it has been programmed to insert a specific binary number that represents the symbol. Unique reference lists have been developed for the assembler of a specific device or family of devices that assign the binary numbers to symbolic names used for the devices. As the assembler reads the assembly-language program and encounters a symbolic name, it inserts the respective binary number and “assembles” the machine code for the program.

Table 7-3 is an example portion taken from a “Standard Register and Bit Definitions for the Texas Instruments MSP430 Microcontroller Family” reference list contained in the Appendix.

 


Figure 7-12: I/O Ports 1, 2 and 3

## \* STATUS REGISTER BITS \*

|                |          |
|----------------|----------|
| #define C      | (0x0001) |
| #define Z      | (0x0002) |
| #define N      | (0x0004) |
| #define V      | (0x0100) |
| #define GIE    | (0x0008) |
| #define CPUoff | (0x0010) |
| #define OSCoff | (0x0020) |
| #define SCG0   | (0x0040) |
| #define SCG1   | (0x0080) |

/\*Low Power Modes coded with bits 4 – 7 in SR\*/

\*if ndef\_IAR\_Systems\_ICC/Begin #defines for assembler\*/

|              |                                 |
|--------------|---------------------------------|
| #define LPM0 | (CPUoff)                        |
| #define LPM1 | (SCG0 + CPUoff)                 |
| #define LPM2 | (SCG1 + CPUoff)                 |
| #define LPM3 | (SCG1 + SCG0 + CPUoff)          |
| #define LPM4 | (SCG1 + SCG0 + OSCoff + CPUoff) |

Table 7-3: Reference list for assembler

Notice, first of all, that the symbolic names in *Table 7-3* are the same ones used to identify the bits in the status register, and the reference list is defining a binary number associated with the symbolic name. For example, the binary number for GIE is the 16-bit hexadecimal number 0008h, which is 0000 0000 0000 1000 in straight binary. If this number is loaded into the status register, it sets the GIE bit. Thus, if the program wants the GIE bit set, an instruction can use GIE as the source operand and SR as the destination, and the assembler knows, because of the reference list, to load the hexadecimal number 0008h into SR which sets GIE. Similarly, the binary number assigned in the reference list will set the bit with the symbolic name in one of the control registers if that symbolic name is used in the appropriate instruction.

Combining symbolic names and their associated binary numbers will set multiple bits in the control registers. This occurs in defining the bits to be set for the MSP430 low-power modes shown in *Table 7-3*. For example, to place the MSP430 system in the LPM3 mode, the SR bits SCG1, SCG0 and CPUoff must be set. One operand of (SCG1 + SCG0 + CPUoff) can be specified and the assembler will combine the binary numbers specified in the reference list and insert them in the SR as shown in *Figure 7-13*. The operand calls out the symbolic names and the respective bit corresponding to the name is set, even when multiple names are used in the operand.

## Format and Symbols

A final thought before discussing the actual programming. The format for the lines of code is as follows, shown with an example instruction:

| Label   | Instruction | Operands     | Comment     |
|---------|-------------|--------------|-------------|
| ADCLoop | bis.b       | #CLK, &P2OUT | ;Clock high |

| Before Instruction           |   |   |   |   |   |   |   | 8 | 7    | 6    | 5       | 4       | 3   | 2 | 1 | 0 | Bit |
|------------------------------|---|---|---|---|---|---|---|---|------|------|---------|---------|-----|---|---|---|-----|
| Status Register              |   |   |   |   |   |   |   | V | SCG1 | SCG0 | OSC OFF | CPU OFF | GIE | N | Z | C |     |
| Inserted from Reference List |   |   |   |   |   |   |   |   |      |      |         |         |     |   |   |   |     |
| SCG1 0080                    | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1    | 0    | 0       | 0       | 0   | 0 | 0 | 0 | 0   |
| SCG0 0040                    | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0    | 1    | 0       | 0       | 0   | 0 | 0 | 0 | 0   |
| CPU OFF 0010                 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0    | 0    | 0       | 1       | 0   | 0 | 0 | 0 | 0   |
| After Instruction            |   |   |   |   |   |   |   |   |      |      |         |         |     |   |   |   |     |
| Status Register              |   |   |   |   |   |   |   | V | SCG1 | SCG0 | OSC OFF | CPU OFF | GIE | N | Z | C |     |

With SCG1 set, SCG0 set and CPU OFF set the MSP430 is in the LPM3 low-power mode.

Figure 7-13: Substitution for symbolic names in status register

## Labels

Labels identify particular positions in the program. They are used extensively to identify the beginning of a program subroutine. When a program needs a particular subroutine, the program can do a subroutine jump to the particular label associated with the subroutine.

## Instructions

The actual instruction appears in the instruction column. In the instruction, bis.b, “set bits in destination”, the .b means it is a byte instruction dealing only with eight bits, the lower byte, of a 16-bit word. When the instruction is a word instruction where all 16 bits are involved, there need be nothing or .w can be used.

## Operands

An operand is the part of the instruction which will operated on by the instruction. Operands are the portion of an instruction designated by an op code to be the quantity to be operated on by the instruction. They appear in the operand column with the source always listed first separated from the destination by a comma. The source may have a symbol in front of it, and the same for the destination. The symbols will correspond to the syntax column in *Figure 7-6* identifying the addressing mode used. In the code line example shown above, the source CLK has a # sign in front of it, and the destination, register P2OUT, has an & in front of it. The # sign indicates immediate addressing for the source, and the & means absolute addressing is used for the destination.

## Hexadecimal Numbers

Hexadecimal numbers will have special identification in most cases. As discussed previously, any hexadecimal number that starts with A through F will have a zero in front of it to make sure the number is identified correctly. A small h is included in the number to identify it as hexadecimal, otherwise the assembler assumes the number is a decimal number. Or, as in the portion of the reference list shown in *Table 7-3*, the format 0x0000 may also be used for a hexadecimal number.

## Comments

The comments column contains hints to someone reading the program what the original programmer had in mind when the line of code was written—what the line of code should accomplish. Many times the comment column is also a refresher to the original programmer. A semicolon must precede all comments. In the explanations that follow of assembly-language programming, no time will be spent on the comments. The reader may use these for extra understanding of the program.

## Programming Examples

### Introduction

In order to explain how to develop a program using assembly language, several subprograms that perform different tasks will be explained in detail to help grasp the concept of programming, learn some of the programming details and get familiar with the format necessary for assembly-language programming. Obviously, sophisticated programmers use high-level languages, but assembly-language programming is used here because it offers an opportunity to grasp the fundamentals of programming so that higher-level language programming can be implemented with less difficulty. It offers fundamental concepts that aid in the understanding of programming in the higher-level languages.

### Subprogram No. 1

#### General Description

The program that will be described is a portion of a total program using a TLV0831 ADC that interfaces to a MSP430F12X microcontroller. The total program includes sampling an analog input voltage, converting it to a digital code, shifting the data into the MSP430, and transmitting the data to a personal computer (PC). The subprogram that is described here is the portion of the total program that deals with initiating the digital conversion and shifting the data into a temporary storage register in the MSP430. Essentially, this subprogram implements a shift register using software.

The block diagram of the system and the interconnections are shown in *Figure 7-14a*. A timing diagram of the events as they occur is shown in *Figure 7-14b*.

Here is a brief description of the application:

1. The TLV0831 is an 8-bit ADC. It samples its analog input, converts the signal to digital and stores the 8-bit digital output in an output register.
2. The TLV0831 data is then shifted out of the output register by the MSP430 into the ADCData register in the MSP430.
3. The TLV0831 data is coupled out on output DO. DO is connected to pin P2.3 of the MSP430, which is programmed to be an input.
4. Pins P2.0 and P2.1 are programmed to be outputs from the MSP430. P2.0 provides a chip select signal to activate the TLV0831, while P2.1 provides clock pulses to the TVL0831.

I/O Port 2, one of the three available, is used for this application. The content of register P2DIR is set to determine which I/O pins are to be inputs and which are to be outputs. The P2IN register inputs and captures the input data from any pins that are inputs, while the P2OUT register outputs the respective data onto the pins that are outputs. The P2.3 input is coupled to a register in the MSP430 called by the symbolic name of ADCData. The 8 bits from the output data register of the TLV0831 are shifted out serially onto DO and end up in this register. It takes 9 shifts to do this—one for a start bit and the remainder for the eight bits of data. The signal on P2.1 acts as the clock for the TLV0831 to shift out the bits onto DO. The start timing is


controlled by the signal on P2.0 of the MSP430, which is connected to CS of the TLV0831. A logic low on CS activates the TLV0831 and initiates the A-to-D conversion. The MSP430 is operated in the LPM3 low-power mode. The watchdog timer is used as an interval timer, set at 64 ms, and when it times out it generates an interrupt to wake up the system and initiate a conversion.

### The Initial Conditions


The subprogram No. 1 assembly-language program is shown in Figure 7-15. Normally, the A, B, C, and D notations are not present; they have been added to aid in the discussion of the program. The reference list that was discussed previously for the MSP430 applies to this program. It is contained in the Appendix. The A and B portions of this program are the same type of reference list, but they are specific only to this program. The assembler takes the “#define” and the “equ” and substitutes the numbers defined for the symbolic name. Software engineers call it “syntactic substitution”—substituting numbers for words (the symbolic notations) in the program.
 
### Section A and B

Section A defines the specific registers that are going to be used, R6(BitCnt) to count bits, R5(RxTxData) to receive and transmit data to the PC, and R11(ADCData) the register to store the data received from the ADC. Section B continues the same type definitions with the “equ” notation. Here the programmer has assigned specific hexadecimal numbers complementing the reference list but specific to this program. The subprogram will use ADCData, TXD, CS, CLK and DO. The remaining substitutions are used by the portion of the total program that transmits data to the PC and that calibrates the DCO. That portion is not included for the sake of brevity.




 a. Block diagram showing interconnections



b. Timing diagram

Destination Operand—Carry Left Shift

 

The destination operand is shifted left one position as shown. The carry bit (C) is shifted into the LSB and the MSB is shifted into the carry bit (C).

c. Rotate left through carry

Figure 7-14: Systems application implemented by Subprogram No. 1  
Courtesy of Texas Instruments Incorporated

```

A.      ; Dedicated CPU registers used
      (1) #define      BitCnt      R6
      (2) #define      RXTXData    R5
      (3) #define      ADCData     R11

B.      ;
      ; User definitions, 9600 Baud HW/SW UART, MCLK = 37.5x32768 = 1228800
      (1) Bitime       equ         0128          ; 104 us
      (2) Delta        equ         150          ; Delta = (target DCO)/(32768/4)
      (3) TXD          equ         002h         ; TXD on P1.1
      (4) CS           equ         001h         ; P2.0 Chip Select
      (5) CLK          equ         002h         ; P2.1 Clock
      (6) DO           equ         008h         ; P2.3 Data Out
      (7) LF           equ         0ah          ; ASCII Line Feed
      (8) CR           equ         0dh          ; ASCII Carriage Return
      ;

      Label  Instruction  Operands              Comment
      -----
C.      ;
      ORG    0F000h          ; Program Start
      -----
1.  Reset   mov          #0300h,SP              ; Initialize F12x stackpointer
2.          call         #Init_Sys              ; Initialize system
      -----
D.      ;
      Init_Sys; Subroutine sets up Modules and Control Registers
      -----
      Label  Instruction  Operands              Comment
      -----
16. StopWDT mov          #WDTPW+WDTHOLD,&WDTCTL ; Stop Watchdog Timer
17. SetupBC mov.b        #DIVA1+RSEL2+RSEL0,&BCSCTL1 ; ACLK/4 RSEL=5
18. SetupP1_2 bis.b      #TXD,&P1SEL            ; P1.1/TA0 for TXD function
19.          bis.b       #TXD,&P1DIR            ; TXD output on P1
20. SetupP2 bis.b        #CS,&P2OUT             ; CS, Set
21.          bis.b       #CS+CLK,&P2DIR         ; CS and Clk Output direction
22. SetupTA mov          #TASSEL1+TACLR,&TACTL  ; SMCLK, clear timer
23. SetupC0 mov          #OUT,&CCCTL0           ; TXD Idle as Mark
24.          call        #Delay                 ; Time for crystal to stabilize

25.          bis         #MC1,&TACTL            ; Start timer in Continous Mode
26.          call        #Set_DCO               ; Set DCO to target frequency
27. SetupWDT mov          #WDT_ADLY_16,&WDTCTL  ; WDT 16ms*4 Interval Timer
28.          bis.b       #WDTIE,&IE1            ; Enable WDT Interrupt
29.          eint                     ; General Interrupt Enable
30.          ret                          ; Return from subroutine
      ;

E.      Label  Instruction  Operands              Comment
      -----
3.  Mainloop bis          #LPM3,SR              ; Enter LPM3
      ;
4.  Meas_ADC; Shift      TVL0831 data into ADCData, R15 used as counter
5.          bic.b        #CS,&P2OUT             ; Chip Select low
6.          mov          #09,R15                ; 9 bits *1 start* + 8 data
7.  ADC_Loop bis.b        #CLK,&P2OUT           ; Clock high
8.          bic.b        #CLK,&P2OUT           ; Clock low
9.          bit.b        #DO,&P2IN              ; DO -> C (carry)
10.         rlc.b        ADCData                ; C -> ADCData

11.          dec         R15                    ; All shifted in?
12.          jnz         ADC_Loop               ; If not --> ADC_Loop
13.          bis.b       #CS,&P2OUT             ; Chip Select high
      ;
14.          call        #TX_ADC_2PC            ; ADC result --> PC
15.          jmp         Mainloop               ; Repeat
      ;

```

**Figure 7-15: Subprogram No. 1—an assembly-language program—a software shift register**  
*Program courtesy of M.E. Buccini and Texas Instruments Incorporated*



## Section C

Section C begins with the following line:

| Label | Instruction | Operands | Comment |
|-------|-------------|----------|---------|
|       | ORG         | 0F000h   |         |

The “ORG” instruction, called an assembler directive, tells the assembler where in memory to put the start of the program. For this program, it starts at the hexadecimal location F000 (1111 0000 0000 0000 in straight binary).

1. The first line of code is:

| Label | Instruction | Operands   |
|-------|-------------|------------|
| RESET | mov         | #0300h, SP |

RESET is a label to identify a location to which the program goes when the system power is turned on. The instruction “move source to destination” means to move the source, the hexadecimal number 0300h, to the destination SP, the symbolic name for the stack pointer. The assembler knows that SP means register R1 in the CPU, as shown in *Figure 7-2a*, and loads 0300 into R1. Recall that the stack pointer stores the return address from a subroutine call so that the program can proceed after it finishes a subroutine. The source is addressed with immediate addressing and the destination with symbolic addressing.

2. The second line of code is:

| Label | Instruction | Operands  |
|-------|-------------|-----------|
|       | call        | #Init_Sys |

The instruction “call” is a subroutine call. It directs the program, with immediate addressing, to a subroutine at a memory location identified as “Init\_Sys.”

## Section D

Section D is the subroutine “Init\_Sys.” It is the portion of the program that sets the initial conditions of the system by setting bits in the control registers that were discussed previously. The subroutine starts at line 16.

16. The sixteenth line of code is:

| Label   | Instruction | Operands                   |
|---------|-------------|----------------------------|
| StopWDT | mov         | #WDTPW + WDT HOLD, &WDTCTL |

The line of code is labeled “StopWDT” as a clue of what is happening. The instruction “mov” means to move the source WDTPW + WDT HOLD to the destination WDTCTL. Immediate addressing (# sign) is used for the source and absolute addressing (& sign) for the destination. WDTCTL is the watchdog timer control register shown in *Figure 7-10*. The symbolic names WDTPW and WDT HOLD load, from the reference list in the Appendix, hexadecimal numbers that correspond to the symbolic names. 05A00h is a password that allows the instruction to write to the WDTCTL, and WDT HOLD sets the HOLD bit to a 1. This holds/stops the watchdog timer.

17. The seventeenth line of code is:

| Label   | Instruction | Operands                         |
|---------|-------------|----------------------------------|
| SetupBC | mov.b       | #DIVA1 + RSEL2 + RSEL0, &BCSCTL1 |

The line of code is labeled “SetupBC” for setup basic clock. The instruction “move source to destination, byte mode” means to move the lower byte of the source into the destination, BCSCTL1, the basic clock system control register. Immediate addressing is used for the source and absolute addressing for the

destination. The symbolic names in the source, DIVA1, RSEL2 AND RSEL0, when moved to the BC-SCTL1, set the respective bits to a 1. Referring to *Figure 7-9*, setting DIVA1 divides the source for ACLK, LFTX1 by 4, and setting RSEL2 (value = 4) and RSEL0 (value = 1) means RSEL=5, or the fifth resistor combination to set the nominal frequency of the DCO.

18. The eighteenth line of code is:

| Label     | Instruction | Operands     |
|-----------|-------------|--------------|
| SetupP1_2 | bis.b       | #TXD, &P1SEL |

The line of code sets up Port 1, thus, labeled “SetupP1\_2.” The instruction “set bits in destination, byte mode”, means that the binary number associated with the symbolic name TXD, which is 002h according to Section B, is used to set the control register P1SEL. 002h, or 0000 0010 in binary, sets the one bit in P1SEL. Setting the one bit in P1SEL means that I/O pin P1.1 will be used by another function other than Port 1; in this case, for the TXD function to transmit data to the PC.

19. The nineteenth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bis.b       | #TXD, &P1DIR |

The instructions “set bits in destination, byte mode” again uses the hex number assigned to the symbol TXD (002h) to set the one bit in the direction control register, P1DIR, shown in *Figure 7-12*. Bit one when set means that pin P1.1 will be an output.

20. The twentieth line of code is:

| Label   | Instruction | Operands   |
|---------|-------------|------------|
| SetupP2 | bis.b       | #CS, P2OUT |

The line of code is labeled “SetupP2” to indicate it is setting up Port 2. The instruction “set bits in destination, byte mode” means the hex number assigned to symbol CS (001h per Section B) is used to set the output register P2OUT. The zero bit of P2OUT is set, and thus, in the high state.

21. The twenty-first line of code:

| Label | Instruction | Operands          |
|-------|-------------|-------------------|
|       | bis.b       | #CS + CLK, &P2DIR |

The instruction “set bits in destination, byte mode” means now the source is CS + CLK; therefore, both hex numbers assigned to the symbols CS and CLK will set bits in the destination, the P2DIR direction register. This sets I/O pin P2.0 and pin P2.1 as outputs. Since the zero bit of P2OUT is in the high state, pin P2.0 will be in the high state. P2.0 is the chip select line for the TLV0831. Since it is high, the TLV0831 is not active.

22. The twenty-second line of code is:

| Label   | Instruction | Operands                 |
|---------|-------------|--------------------------|
| SetupTA | mov         | #TASSEL1 + TACLR, &TACTL |

Timer\_A is being setup by the line of code labeled “SetupTA.” The instruction “move source to destination” means to move the hex numbers associated with the symbolic names TASSEL1 and TACLR to the Timer\_A control register, TACTL, shown in *Figure 7-11*. Setting TASSEL1 selects the SMCLK clock as the Timer\_A source and setting the CLR bit resets Timer\_A.

23. The twenty-third line of code is:

| Label   | Instruction | Operands     |
|---------|-------------|--------------|
| SetupCO | mov         | #OUT, &CCTL0 |

The label “SetupCO” explains that the OUT bit in a capture/compare control register is being set. The instruction “move source to destination” is setting the OUT bit of the capture/compare control register, CCTLO. Effectively, the TXD bit state is output onto pin P1.1 with this instruction. Since the P1OUT is a 1, TXD will be a 1 or a MARK in transmit language. A 0 is defined as a SPACE.

24. The twenty-fourth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | call        | #Delay   |

The instruction “call” means the program is calling a subroutine labeled “Delay.” This subroutine, not shown in our subprogram, provides a time delay with software. The crystal oscillator used as the source for the clocks needs time to stabilize. The instruction calls the subroutine, which when executed, provides the time delay needed for the oscillator to stabilize.

25. The twenty-fifth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bis         | #MC1, &TACTL |

The instruction “set bits in destination” sets the MC1 bit in the TACTL control register, shown in *Figure 7-11*, by inserting the assigned hex number. With MC1 = 1 (and MC0 = 0), Timer A is set into the continuous mode and starts counting from 0 to 0FFFFh. When it gets to 0FFFFh it restarts from 0.

26. The twenty-sixth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | call        | #Set_DCO |

The instruction “call” this time is calling the subroutine “Set\_DCO” which is not shown in our subprogram. It is a subroutine that calibrates the high-speed, digitally-controlled oscillator (DCO). For this program, the DCO is calibrated to 1,228,800 Hz (cycles per second), and configured to be the source for the main system clock, MCLK, and subsystem clock, SMCLK.

27. The twenty-seventh line of code is:

| Label    | Instruction | Operands              |
|----------|-------------|-----------------------|
| SetupWDT | mov         | #WDT_ADLY_16, &WDTCTL |

Labeled “SetupWDT” to explain that the watchdog timer is being set up, the instruction “move source to destination” moves the hex number assigned to the source WDT\_ADLY\_16 by the reference list to the destination, the watchdog timer control register, WDTCTL, shown in *Figure 7-10*. The assigned hex number 05A1E provides the 5A that is required when the WDTCTL is being written to, and sets bits WDTTMSSEL, WDTCNTCL, WDTSSEL and WDTIS1. Setting WDTTMSSEL makes the WDT an interval timer; setting CNCTL clears the WDCNT counter and restarts it at zero; setting WDTSSEL selects ACLK for the counter source; and setting WDTIS1 chooses a 512 division factor for the time interval which sets the time interval between pulses to be 62.5 ms (milliseconds).

28. The twenty-eighth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bis.b       | #WDTIE, &IE1 |

The instruction “set bits in destination, byte mode” takes the source hex number assigned to the symbolic name WDTIE (01h) and places it in the interrupt enable register, IE1. It sets the zero bit, which enables the watchdog timer interrupt. As a result, because this signal is active when the watchdog timer is in the interval timer mode, the watchdog timer interrupt is enabled.

29. The twenty-ninth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | eint        |          |

The instruction “enable (general) interrupts” sets the GIE bit in the status register shown in *Figure 7-7* and says “all interrupts are enabled.” This allows the interrupt generated when the WDT interval timer times out to interrupt the system, wake it up from the LPM3 mode and be active.

30. The thirtieth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | ret         |          |

The instruction “return from subroutine” tells the program to return to the code address following the subroutine call, in this program to line 3. The program has completed all initial conditions and now returns to do its main operations.

## Section E—Main Application

3. The third line of code is:

| Label    | Instruction | Operands |
|----------|-------------|----------|
| Mainloop | bis         | #LPM3,SR |

The label “Mainloop” identifies this line of code as the start of the main portion of the program. The instruction “set bits in destination” takes the hex number assigned to the source, symbolic name LPM3, by the reference list, and sets bits in the destination, SR. As shown in *Figure 7-3*, the hex number for LPM3 sets the bits SCG1, SCG0 and CPUOFF in the status register. This sets the system in the LPM3 low-power mode. Recall that in LPM3, the CPU is inactive but peripherals and the ACLK clock are active, and, in this application, that the WDT interval timer awakens the system.

4. The fourth line of code is:

| Label    | Comment                                               |
|----------|-------------------------------------------------------|
| Meas_ADC | ;Shift TLV0831 data into ADCData, R15 used as counter |

The comment for the label “Meas\_ADC” identifies that part of the program that initiates the ADC measurement, and, after the data is present, shifts the data into the register ADCData. The register R15 will be used to count off the number of shifts. Its contents determine the number of shifts.

5. The fifth line of code is:

| Label | Instruction | Operands   |
|-------|-------------|------------|
|       | bic.b       | #CS,&P2OUT |

The instruction “clear bits in destination, byte mode” means that the hex number assigned to CS (001h) in Section B will clear bits in the destination, P2OUT, the output register. Immediate addressing is used for the source, absolute addressing for the destination. The zero bit of P2OUT is cleared, and, as a result, pin P2.0, is a 0, or low. P2.0 is the CS signal to the TLV0831. Since it is low, it activates the TLV0831 and starts the ADC conversion.

6. The sixth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | mov         | #09,R15  |

The instruction “mov” means to move the source to the destination. There is immediate addressing for the source; register addressing for the destination. As a result, the number 9 is inserted as the contents of

(moved to) register 15 to determine how many bits are going to be shifted onto DO. As discussed earlier, a start bit is required for outputting serial data. Since the data is eight bits, the number 9 is loaded into R15 with the “mov” instruction. If the ADC were converting to a larger number of bits than eight, then R15 would have to be loaded with a correspondingly larger number.

7. The seventh line of code is:

| Label    | Instruction | Operands     |
|----------|-------------|--------------|
| ADC_Loop | bis.b       | #CLK, &P2OUT |

“ADC\_Loop” is a subroutine label. The program will continue to a decision point and then loop back to this label. The instruction “set bits in destination, byte mode” means that the source hex number assigned to “CLK” in Section B (002h) will be used to set bits in the lower byte of the destination, register P2OUT, the output register for Port 2. Thus, the one bit of P2OUT will be set, and pin P2.1 will have a 1 or high output. P2.1 is connected to CLK of the TLV0831; therefore, CLK is high.

8. The eighth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bic.b       | #CLK, &P2OUT |

The instruction “clear bits in destination, byte mode” means that the same source hex number assigned to “CLK” (002h) will be used to clear bits in the lower byte of the destination, the output register P2OUT. This line of code clears bits rather than set them as in line 7. As a result, the one bit of P2OUT is cleared to a 0, and pin P2.1 will have a 0, or a low, on it. Thus, CLK for the TLV0831 is now low. A low on CLK shifts the data onto the output DO, onto the pin P2.3 of the MSP430 and into register P2IN. The shifting of data occurs when the CLK line of the TLV0831 goes low as shown in the timing diagram of *Figure 7-14b*.

9. The ninth line of code:

| Label | Instruction | Operands   |
|-------|-------------|------------|
|       | bit.b       | #DO, &P2IN |

The instruction “test bits in destination, byte mode” means that the source hex number assigned to “DO” in Section B (008h) will be used to designate that the eight bit of the destination P2IN will be tested. And the result of the operation will affect the carry bit of the status register in the MSP430. Only the status register bits are affected. If the eight bit of P2IN is a 0, carry will be a 0; if the eight bit is a 1, carry will be a 1.

10. The tenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | rlc.b       | ADCData  |

The instruction “rotate left through carry” means that the contents of the ADCData register is rotated left one position and the carry bit of the status register is shifted into the LSB and the MSB is shifted into the carry bit. Symbolic addressing is used. *Figure 7-14c* illustrates the result of the rlc.b instruction. The carry bit from the previous instruction becomes the carrier of the data. When the carry bit is a 0, the ADCData register bit is a 0; when the carry bit is a 1, the ADCData register bit is a 1. The ADCData register becomes the temporary storage for the output data from the TLV0831 until all data is transferred. After all the data is collected, the ADCData register can be operated on by the MSP430 CPU.

11. The eleventh line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | dec         | R15      |

The instruction “decrement destination” means to subtract one from the contents of register R15. Register addressing is used. Register R15 has the number 9 in it. Nine minus one means the content of R15 is now 8.

At the same time, the register contents are tested and status bits are set in the status register. The Z bit is the one noted in the next instruction, so it is the bit of interest. Here is the rule for the test of the Z bit:

| Status Bit | Rule                                                    |
|------------|---------------------------------------------------------|
| Z          | Set if destination register contains 1, reset otherwise |

If destination register R15 is other than zero, then the Z bit is set to a 1.

12. The twelfth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jnz         | ADC_Loop |

The instruction “jump if not zero” tests the status register Z bit. If Z is not 0, the program jumps to the line in the program that has the label ADC\_Loop, which is line 7. Symbolic addressing is used. The program again runs through line 7, 8, 9, 10 and 11. This is called a subroutine jump, and the subroutine loop being lines 7, 8, 9, 10 and 11.

When the program returns to line 7, it again sets the TLV0831 CLK high. Line 8 then sets this same CLK low to shift the second bit to the output DO and pin P2.3 of the MSP430. The result is rotated into ADC-Data and R15 is decremented. The program again tests the Z bit and finds it is not zero and jumps back to line 7. The program continues in the loop rotating each bit in and subtracting 1 from R15 until the content of R15 is zero (9 counts).

When the status bit Z is zero as a result of R15 being zero, the program now does not jump but continues to line 13.

13. The thirteenth line of code is:

| Label | Instruction | Operands    |
|-------|-------------|-------------|
|       | bis.b       | #CS, &P2OUT |

The instruction “set bits in destination, byte mode” means that the hex number assigned to CS (001h) will be used to set bits in the lower byte of the output register P2OUT. Thus, the zero bit of P2OUT will be set and pin P2.0 will have a high output. P2.0 is the chip select for the TLV0831, and with it high, the TLV0831 is deactivated.

14. The fourteenth line of code is:

| Label | Instruction | Operands    |
|-------|-------------|-------------|
|       | Call        | #TX_ADC_2PC |

The instruction “call” tells the program to go to the label TX\_ADC\_2PC that is a subroutine in the program that transmits data from the register ADCData to a personal computer using a UART. The program will go through the subroutine TX\_ADC\_2PC, which is left out to keep the discussion brief. When it is finished, it returns to the program step after the subroutine call, step 15.

15. The fifteenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jmp         | Mainloop |

The instruction “jmp” is called an unconditional jump instruction. It is addressed with symbolic addressing. The program jumps to Mainloop, which is the label on line 3 that is the start of Section E, the measuring portion of subprogram No. 1. Thus, the program is ready to start another measuring cycle by initiating a conversion by the ADC.


## Subprogram No. 2

### General Description


All systems need a clock to synchronize timing of events occurring as the system operates. This subprogram sets up the MSP430 clock MCLK to use LFXT1 as its source. LFXT1 is operated in the high-frequency crystal oscillator mode using a crystal between 1 MHz and 8 MHz. As mentioned in Subprogram No. 1, the crystal oscillator requires a certain time to stabilize; therefore, the program is setup to test the crystal oscillator, and only after it is stable, will it use LFXT1 as the source for MCLK. MCLK drives a software loop that takes exactly 10 clock cycles; therefore, it produces a clock signal that divides MCLK by 10.

One other feature of the MSP430 is that there is a “fail safe” mechanism built into the clock system. Since the crystal oscillator needs time to stabilize, there is a default mode which uses the DCO as a clock source until the crystal oscillator is up and running properly. Even though the DCO is not as accurate as the crystal timing, the DCO keeps the system timed and operating properly from the start.

 The block diagram for the application is shown in Figure 7-16a and the timing diagram in Figure 7-16b. Pin P1.1 of I/O Port 1 is used as an output for the MCLK divided by 10 signal, and pin P2.0 of I/O Port 2 is used for an external clock, ACLK. Note that the Pin P1.1 output is an asymmetrical waveform.



a. Block diagram showing pin connections

 

b. Timing diagram

Figure 7-16: Subprogram No. 2 application—outputting clocks

### Section A—Initial Conditions

The subprogram is shown in Figure 17. It is understood that for this subprogram the same reference list that was used for Subprogram No. 1 is used again. Other very specific reference lists could be used here as in Subprogram No.1, but are not necessary. Any reference list is to be used by the assembler to insert specific hexadecimal numbers assigned to particular symbolic names.

Section A begins with the following line of code:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | ORG         | 0F000h   |

The assembler directive “ORG” tells the assembler to put the start of the program in memory location 0F000h. The same location used for Subprogram No. 1.

| ;*****       |             |                        |                                    |
|--------------|-------------|------------------------|------------------------------------|
| Label        | Instruction | Operands               | Comment                            |
| -----        |             |                        |                                    |
| A.           | ORG         | 0F000h                 | ; Program Start                    |
| -----        |             |                        |                                    |
| 1. RESET     | mov.w       | #300h,SP               | ; Initialize stackpointer          |
| 2. StopWDT   | mov.w       | #WDTPW+WDTHOLD,&WDTCTL | ; Stop WDT                         |
| 3. SetupBC   | bis.b       | #XTS,&BCSCTL1          | ; LFXT1 = HF XTAL                  |
| 4. SetupOsc  | bic.b       | #OFIFG,&IFG1           | ; Clear OSC fault flag             |
| 5.           | mov.w       | #0FFh,R15              | ; R15 = Delay                      |
| 6. SetupOsc1 | dec.w       | R15                    | ; Additional delay to ensure start |
| 7.           | jnz         | SetupOsc1              | ;                                  |
| 8.           | bit.b       | #OFIFG,&IFG1           | ; OSC fault flag set?              |
| 9.           | jnz         | SetupOsc               | ; OSC Fault, clear flag again      |
| 10.          | bis.b       | #SELM1+SELM0,&BCSCTL2  | ; MCLK = LFXT1                     |
| ;            |             |                        |                                    |
| 11.          | bis.b       | #001h,&P2DIR           | ; P2.0 = output direction          |
| 12.          | bis.b       | #001h,&P2SEL           | ; P2.0 = ACLK function             |
| 13.          | bis.b       | #002h,&P1DIR           | ; P1.1 = output direction          |
| ;            |             |                        |                                    |
| 14. Mainloop | bis.b       | #002h,&P1OUT           | ; P1.1 = 1                         |
| 15.          | bic.b       | #002h,&P1OUT           | ; P1.1 = 0                         |
| 16.          | jmp         | Mainloop               | ; Repeat                           |

**a. Asymmetrical waveform for output clock with MCLK/10 frequency**

|              |       |              |                 |
|--------------|-------|--------------|-----------------|
| 14. Mainloop | xor.b | #002h,&P1OUT | ; P1.1 = Toggle |
| 15.          | jmp   | Mainloop     | ; Repeat        |

**b. Symmetrical waveform for output clock with MCLK/12 frequency**

**Figure 7-17: Subprogram No. 2—assembly-language program—outputting clocks**

1. The first line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
| RESET | mov.w       | #300h,SP |

When power is turned on, the program goes to the line of code labeled RESET for its instruction “mov.w”. The instruction “move source to destination” loads the number 0300h into the stack pointer. This initializes the stack pointer. Note the .w notation has been used to identify the instruction as a word instruction. Immediate addressing is used for the source, and symbolic addressing for the destination. The reader should now be familiar with these notations so reference to them will be discontinued unless pertinent to the discussion.

2. The second line of code is:

| Label   | Instruction | Operands                 |
|---------|-------------|--------------------------|
| StopWDT | mov.w       | #WDTPW + WDTHOLD,&WDTCTL |

The label “StopWDT” explains the instruction is stopping the watchdog timer. The instruction “mov.w” moves the hexadecimal numbers assigned to the symbolic names of the source, WDTPW and WDTHOLD, to the watchdog timer control register WDTCTL to set the respective bits. The password WDTPW is 5A00h to write to the WDTCTL and set WDTHOLD. This holds or stops the watchdog timer, and thus, it will not interrupt the system.

3. The third line of code is:

| Label   | Instruction | Operands      |
|---------|-------------|---------------|
| SetupBC | bis.b       | #XTS,&BCSCTL1 |



Setup basic clock is what the label "SetupBC" means. The instruction "bis.b" means "set bits in destination, byte mode" and the binary number associated with the symbolic name of the source, XTS, will set that bit in the basic clock control register BCCTL1 shown in Figure 7-9a. With XTS set, the LFTXT1 clock will operate with a high-frequency crystal oscillator as the source.

4. The fourth line of code is:

| Label    | Instruction | Operands      |
|----------|-------------|---------------|
| SetupOsc | bic.b       | #OFIFG, &IFG1 |

As indicated by the label "SetupOsc", the instruction is used to setup the crystal oscillator used for the clock. The instruction "clear bits in destination, byte mode" means that the bit in the hex number associated with the source OFIFG will be used to clear a flag in the destination register IFG1. IFG1 is an interrupt flag register. The bit OFIFG is an interrupt flag for the crystal oscillator. If the crystal oscillator is not "up and running" the flag is set. Recall that the crystal oscillator needs a certain time delay before it is operating properly. When the OFIFG flag is not set, the oscillator is running properly. This instruction clears the flag so it is in the correct condition.

5. The fifth line of code is:

| Label | Instruction | Operands   |
|-------|-------------|------------|
|       | mov.w       | #0FFh, R15 |

The instruction "move source to destination, word mode" means that the hex number 0FFh will be loaded into register R15. R15 is going to be used as a counter whose content determines the time delay that is setup to allow the crystal oscillator to stabilize.

6. The sixth line of code is:

| Label     | Instruction | Operands |
|-----------|-------------|----------|
| SetupOsc1 | dec.w       | R15      |

"SetupOsc1" is a label identifying a subroutine loop that is associated with the crystal oscillator delay that is required. The instruction "decrement destination" subtracts one from the contents of R15.

7. The seventh line of code is:

| Label | Instruction | Operands  |
|-------|-------------|-----------|
|       | jnz         | SetupOsc1 |

The instruction "jump if not zero" tests the Z (zero) bit in the status register. If the result of the operation in line 6 is not zero, Z will be zero, and the program will jump to the subroutine label "SetupOsc1" which is line 6. The program will stay in this subroutine loop until Register 15 contents are decremented to zero. This produces a time delay of the time that is required to cycle through the loop until R15 = 0. The time delay is determined by the value loaded into R15 in line 5.

When R15 = 0, then the Z bit will be set and the program does not jump to line 6 but continues to line 8.

8. The eighth line of code is:

| Label | Instruction | Operands      |
|-------|-------------|---------------|
|       | bit.b       | #OFIFG, &IFG1 |

The instruction "test bits in destination, byte mode" means that the source bit, the oscillator fault interrupt flag, OFIFG, in the destination interrupt flag register IFG1, will be tested. If the crystal oscillator is not completely stable, the flag will be set.

9. The ninth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jnz         | SetupOsc |

The instruction “jump if not zero” again tests the Z bit. If the result of the operation in line 8 is not zero, i.e. the flag is set,  $Z = 0$  and the program will jump to the subroutine label “SetupOsc” which is line 4. Thus, the program returns to line 4 where it clears the oscillator fault interrupt flag bit, OFIFG, in register IFG1 and reloads R15 for an additional delay time. The loop of line 6 and 7 decrements R15 until the delay is complete. The fault flag OFIFG is tested again to see if it is set by line 8. If the oscillator is stable, OFIFG will not be set, the result will be zero and the program does not jump back on line 9, but continues to line 10. If the flag is set, then the oscillator is still not stable, and another pass through line 4, 5, 6, 7, 8 and 9 adds additional delay.

10. The tenth line of code is:

| Label | Instruction | Operands                 |
|-------|-------------|--------------------------|
|       | bis.b       | #SELM1 + SELM0, &BCSCTL2 |

The instruction “set bits in destination, byte mode” will set the bits SELM1 and SELM0 of the source, in the destination register BCSCTL2 as a result of assigned hex numbers from the reference list. Referring to *Figure 7-9b*, with SELM1 and SELM0 both equal to 1, the source LFXT1 is selected for the MCLK clock. What has happened is the program has assured that the high-frequency crystal oscillator is up and running and stable before it is used as a source for the main system clock, MCLK.

11. The eleventh line of code is:

| Label | Instruction | Operands      |
|-------|-------------|---------------|
|       | bis.b       | #001h, &P2DIR |

The instruction “set bits in destination, byte mode” loads the source 001h into the destination Port 2 direction register, P2DIR. This sets the zero bit in P2DIR and makes pin P2.0 an output.

12. The twelfth line of code is:

| Label | Instruction | Operands      |
|-------|-------------|---------------|
|       | bis.b       | #001h, &P2SEL |

The instruction “set bits in destination, byte mode” loads the source, again 001h into the special function register P2SEL and sets the zero bit. This means that the pin P2.0 is an output for an external clock ACLK, rather than the Port 2 output register P2OUT.

13. The thirteenth line of code is:

| Label | Instruction | Operands      |
|-------|-------------|---------------|
|       | bis.b       | #002h, &P1DIR |

The instruction “set bits in destination, byte mode” means that the source 002h is loaded into the destination, the direction register, P1DIR, to set the one bit. This sets pin P1.1 as an output.

## Section B—Mainloop

14. The fourteenth line of code is:

| Label    | Instruction | Operands      |
|----------|-------------|---------------|
| Mainloop | bis.b       | #002h, &P1OUT |

The label “Mainloop” indicates this is the start of a subroutine. The instruction “set bits in destination, byte mode” loads 002h into the destination, the output register P1OUT, and sets pin P1.1. This means that P1.1 is in the high state.

15. The fifteenth line of code is:

| Label | Instruction | Operands      |
|-------|-------------|---------------|
|       | bic.b       | #002h, &P1OUT |

The instruction “clear bits in destination, byte mode” clears the one bit, identified by the source 002, in the destination P1OUT output register. Thus, pin P1.1 is cleared to zero, a low state.

16. The sixteenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jmp         | Mainloop |

The instruction “jump unconditionally” directs the program to jump to the line of code labeled “Mainloop”, line 14. Thus, the program remains in the loop and cycles from line 14 to line 15 to line 16 and back to line 14 resulting in a square wave clock output on pin P1.1 as shown in *Figure 7-16b*. The clock driving the CPU is MCLK. It takes four clock cycles for the program to execute line 14, four clock cycles for executing line 15, and two cycles to execute line 16; thus producing an asymmetrical square wave clock output on P1.1 that is one-tenth the frequency of MCLK. This relationship is shown in the timing diagram of *Figure 7-16b*. Thus, two clocks result from the subprogram, one on P1.1 which is one-tenth the frequency of the high-frequency crystal oscillator, LFXT1, and the other an external clock, ACLK, on P2.0.

## Section B—Mainloop Modification

Because the program in *Figure 7-17a* produces an asymmetrical waveform it may not be as desirable as a symmetrical wave; therefore, the main loop instructions can be modified to produce a symmetrical wave. Steps 14 and 15 can be modified as shown in *Figure 7-17b*, and step 16 is omitted.

With steps 14 and 15 modified, the program proceeds from step 14 as follows:

14. The fourteenth line of code is:

| Label    | Instruction | Operands    |
|----------|-------------|-------------|
| Mainloop | xor.b       | #002,&P1OUT |

The label “Mainloop” is the same as previously and indicates this is the start of a subroutine. The instruction “Exclusive OR of source with destination, byte mode” does an exclusive OR logic operation with the source 002h and the output register P1OUT and places the result in the destination, the P1OUT register. Since pin P1.1 is the 1 bit of the P1OUT register, the result of the exclusive OR will appear on pin P1.1. In the first execution of line 14, if the 1 bit is 0, the XOR will toggle the state of the 1 bit—it will be a 1 and pin 1.1 will be a 1. In the next pass, the bit will be toggled to a 0.

15. The fifteenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jmp         | Mainloop |

The instruction “jump unconditionally” directs the program to jump to the line of code labeled “Mainloop”, line 14. Thus, the program remains in the loop and cycles from step 14 to step 15 and back again. The clock, as previously, driving the CPU is MCLK. As a result, for this modification, it takes four cycles to execute line 14 and two cycles to execute line 15. P1.1 will now have a symmetrical square wave output with a frequency equal to MCLK/12.

## Subprogram No. 3

### General Description

Here is a program that outputs a visual signal when an input voltage is at or greater than a particular value. The block diagram is shown in *Figure 7-18a*. This time a TLC549 ADC is used. It is an 8-bit analog-to-digital converter that converts the input analog voltage into an 8-bit code that is shifted into the MSP430 microcontroller register R11 labeled ADCData. There is an LED (light-emitting diode) on I/O output pin P1.0.

When the input voltage is equal or greater than  $+0.5V_{CC}$ , then the value of the contents of R11 will be equal to or greater than  $+0.5V_{CC}$ , and the LED will be lit. For any input voltage less than  $+0.5V_{CC}$ , the LED will not light; therefore, one can start at  $V_{IN} = 0$  and adjust the input voltage toward  $V_{CC}$ . When the input voltage is at  $+0.5V_{CC}$  the LED will glow to indicate  $+0.5V_{CC}$  had been reached.

The assembly-language program is shown in Figure 7-19. Again as with Subprograms No. 1 and No. 2, “Section A,” “Section B,” “Section C,” “Section D” and “Section E” have been added to aid in describing the program.

Sections A and B

Section A and B are specific to this subprogram. Section A again is clarifying that register R11 is identified with a label “ADCData” and that register R12 is identified with a label “Counter.” They are two of the 16-bit working registers as shown in Figure 7-2a.

Section B is again an addition to the standard reference list in the Appendix for the MSP430. In the section, the specific hexadecimal numbers shown are assigned to symbolic names that the assembler substitutes into the program when the symbolic names are used in the program.

Section C—Initial Conditions

The program starts in memory at address 0F000h established by the ORG instruction.


| Label | Instruction | Operands |
|-------|-------------|----------|
|       | ORG         | 0F000h   |

The assembler begins this program at the same location in memory (0F000h) used for Subprograms No. 1 and No.2. Then initial conditions are setup for the program with steps 1 through 5. Bits in the control registers discussed in Figures 7-7 to 7-11 will be set to control the initial conditions.


1. The first line of code is:

| Label | Instruction | Operands   |
|-------|-------------|------------|
| RESET | mov.w       | #0300h, SP |

 The type of addressing mode should now be fairly well understood so reference to the addressing modes will be omitted to simplify the discussion. The label “RESET” identifies where the program starts when



 a. Block diagram showing interconnections



b. R11 content versus % VCC

Figure 7-18: System application implemented by Subprogram No. 3 energizing an output when input is greater than  $+0.5V_{CC}$

```

;
A. #define          ADCData R11
   #define          Counter R12
B. CS              equ      001h          ; P2.0 - Chip Select
   CLK             equ      002h          ; P2.1 - Clock
   DO              equ      008h          ; P2.3 - Data Out
;-----
C.                      ORG      0F000h          ; Program Start
;-----
1. RESET          mov.w      #300h,SP          ; Initialize 'x112x stack
2. StopWDT        mov.w      #WDTPW+WDTHOLD,&WDTCTL ; Stop Watchdog Timer
3. SetupP2        mov.b      #CS,&P2OUT        ; /CS set, - P2.x reset
4.               bis.b      #CS+CLK,&P2DIR      ; /CS and CLK outputs
5. SetupP1        bis.b      #001h,&P1DIR      ; P1.0 output
;-----
D. 6. Mainloop    call       #Meas_549          ; Call subroutine
   18.           bic.b      #01h,&P1OUT        ; P1.0 = 0
   19.           cmp.w      #07Fh,ADCData      ; ADCData > 0.5Vcc?
   20.           jlo        Mainloop           ; Again
   21.           bis.b      #01h,&P1OUT        ; P1.0 = 1
   22.           jmp        Mainloop           ; Again
;-----
E. Meas_549;      Subroutine to read TLC549, data is shifted into ADCData
;                (R11), Counter (R12) is used as a bit counter.
;-----
7.               mov.w      #8,Counter         ; 8 data bits
8.               clr.w      ADCData            ; Clear data buffer
9.               bic.b      #CS,&P2OUT        ; /CS reset, enable ADC
10. ADC_Loop      bit.b      #DO,&P2IN         ; (4) DO -> C (carry)
11.               rlc.w      ADCData           ; (1) C -> ADCData
12.               bis.b      #CLK,&P2OUT       ; (4) Clock high
13.               bic.b      #CLK,&P2OUT       ; (4) Clock low
14.               dec.w      Counter           ; (1) All bits shifted in?
15.               jnz        ADC_Loop         ; (2) If not --> ADC_Loop
16.               bis.b      #CS,&P2OUT        ; /CS set, disable ADC
17.               ret                    ; Return from subroutine
;

```

**Figure 7-19: Subprogram No. 3—An assembly-language program energizing an output when input is greater than +0.5V<sub>cc</sub>**

power is turned on, or a reset is performed. The instruction “move source to destination” moves the source 0300h to the stack pointer, the special function register identified by the symbolic name SP. When a program completes a subroutine it will return to the address on the stack.

2. The second line of code is:

| Label   | Instruction | Operands                 |
|---------|-------------|--------------------------|
| StopWDT | mov.w       | #WDTPW + WDTHOLD,&WDTCTL |

The word instruction “move source to destination” sets bit in the destination, the watchdog timer control register WDTCTL, so that the watchdog timer is put on hold. The symbolic name WDTPW (5A00h) allows writing to WDTCTL and the symbolic name WDTHOLD sets that bit in WDTCTL to hold the watchdog timer and stop it from interrupting the system.

3. The third line of code is:

| Label   | Instruction | Operands   |
|---------|-------------|------------|
| SetupP2 | mov.b       | #CS,&P2OUT |

The label “SetupP2” identifies the instruction as one to setup the I/O P2. The “move source to destination, byte mode” takes 001h assigned to the source CS and moves it to the P2OUT register to set the zero bit of P2OUT or pin P2.0 to a 1. P2.0 is the chip select line to the TLC549.

4. The fourth line of code is:

| Label | Instruction | Operands          |
|-------|-------------|-------------------|
|       | bis.b       | #CS + CLK, &P2DIR |

The instruction “set bits in destination, byte mode” means that bits in the P2DIR control register will be set to control whether the pins of the P2 I/O will be outputs per *Figure 7-12*. If the pins are not set they will be inputs. 001h of CS sets the zero bit of P2DIR and 002h of CLK sets the one bit of P2DIR; therefore, pin P2.0 and pin P2.1 are outputs from the MSP430. Since P2.0 is a 1, or high, and is the chip select line for the TLC549, the TLC549 is inactive.

5. The fifth line of code is:

| Label   | Instruction | Operands      |
|---------|-------------|---------------|
| SetupP1 | bis.b       | #001h, &P1DIR |

This line of code is going to setup I/O P1 as indicated by the label “Setup P1”. The instruction “set bits in destination, byte mode” with the source, 001h, sets the zero bit of the direction control register P1DIR so that pin P1.0 is an output.

## Section D—Main Application

6. The sixth line of code is:

| Label    | Instruction | Operands  |
|----------|-------------|-----------|
| Mainloop | call        | #Meas_549 |

The label “Mainloop” identifies the location in the program as the start of the main part of the program—the part of the program that measures the input to the TLC549 ADC. The “call” instruction tells the program to jump to the subroutine labeled “Meas\_549.” The “Meas\_549 subroutine starts with the seventh line of code.

7. The seventh line of code is:

| Label | Instruction | Operands    |
|-------|-------------|-------------|
|       | mov.w       | #8, Counter |

The instruction “move source to destination, word mode” means that the source, the hex number 8 will be moved to register 12 which has been assigned the symbolic name “Counter.” It will be used to count the eight bits of the data output of the TLC549 ADC.

8. The eighth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | clr.w       | ADCData  |

The instruction “clear destination, word mode” means that register R11 identified with the symbolic name “ADCData” will be cleared to zero.

9. The ninth line of code is:

| Label | Instruction | Operands    |
|-------|-------------|-------------|
|       | bic.b       | #CS, &P2OUT |

The instruction “clear bits in destination, byte mode” means that the hex number assigned to CS (001h) will be used to clear the zero bit of the destination, the output register P2OUT; therefore, pin P2.0 will be reset to 0 or a low. Since P2.0 is the chip select line of the TLC549, this activates the TLC549 to measure its input analog voltage and convert it to an 8-bit digital code representing the value of the input voltage.

10. The tenth line of code is:

| Label    | Instruction | Operands   |
|----------|-------------|------------|
| ADC_loop | bit.b       | #DO, &P2IN |

The label “ADC\_loop” identifies the line of code as the start of a subroutine loop. The instruction “test bits in destination, byte mode” means that the source hex number assigned to “DO” in section B (008h) will be used to designate that the eight bit of the destination P2IN will be tested. The result of the operation will affect the carry bit of the status register in the MSP430. Only the status register bits are affected. If the eight bit of P2IN is a 0, carry will be a 0; if the eight bit is a 1, carry will be a 1.

11. The eleventh line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | rlc.w       | ADCData  |

The instruction “rotate left through carry” means that the ADCData register is rotated left one position and the carry bit of the status register is shifted into the LSB and the MSB is shifted into the carry bit. Refer to the diagram in *Figure 7-14c*. The carry bit from the previous instruction becomes the carrier of the data. When the carry bit is a 0, the ADCData register bit is a 0; when the carry bit is a 1, the ADCData register bit is a 1. The ADCData register becomes the temporary storage for the data as the eight bits of data are shifted into the register.

12. The twelfth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bis.b       | #CLK, &P2OUT |

The instruction “set bits in destination, byte mode” means the hex number assigned to the source CLK (002h) will be used to set the one bit of the P2OUT register so that pin P2.1 will be at a high level. P2.1 is tied to the CLK input of the TLC549.

13. The thirteenth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bic.b       | #CLK, &P2OUT |

The instruction “clear bits in destination” means that the same bit in the P2OUT register as in the previous instruction is now cleared back to 0, or a low level. The pin P2.1, being the clock for the TLC549, means that when the clock goes low the next bit from the ADC data is shifted out on the DO line of the TLC549.

14. The fourteenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | dec.w       | Counter  |

The instruction “decrement destination” means to subtract one from the contents of register R12, the register identified by the symbolic name “Counter.” Since this is the first pass through the loop, R12 will now have a contents equal to seven, since the register was originally loaded with the value eight.

15. The fifteenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jnz         | ADC_loop |

The instruction “jump if not zero” tests the status register Z bit which will be a 1 or 0 based on the result of the instruction in line 14. If the result of line 14 is not zero, Z will be 0, and the program jumps to the line in the program that has the label ADC\_loop, which is line 10. When the result of line 14 is zero, Z will be 1, and the program will not jump, but continue on to the next instruction. The program will continue in the

loop from line 10 to line 15 until the contents of R12, the counter register, reach zero. When the contents have the value of zero, it means that the eight data bits have been shifted out onto DO. When the contents of R12 is zero, the program does not jump, but continues to line 16.

16. The sixteenth line of code is:

| Label | Instruction | Operands    |
|-------|-------------|-------------|
|       | bis.b       | #CS, &P2OUT |

The instruction “set bits in destination, byte mode” means the hex number 001h assigned to CS is used to set the zero bit of the P2OUT register so that pin P2.0 is set to a high level. Since P2.0 is the chip select of the TLC549, the TLC549 is disabled and its conversion ceases.

17. The seventeenth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | ret         |          |

The instruction “return from subroutine” means the program picks up the return address from the stack pointer which is the address of the next line of code after the subroutine call. As a result, the program returns to line 18, the next instruction after line 6.

18. The eighteenth line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bic.b       | #01h, &P1OUT |

The instruction “clear bits in destination, byte mode” means that the zero bit of the P1OUT register designated by the source 01h will be cleared; therefore, pin P1.0 will be cleared to a zero, or low level.

19. The nineteenth line of code is:

| Label | Instruction | Operands       |
|-------|-------------|----------------|
|       | cmp.w       | #07Fh, ADCData |

The instruction “compare source and destination” means that ADCData is compared to the hex number 07Fh, and the bits in the status register are set accordingly.

20. The twentieth line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jlo         | Mainloop |

The instruction “jump if lower” means that the result of the operation in line 19 governs what happens in this instruction. If ADCData register contents are lower than 07Fh, then the program jumps to “Mainloop”, another subroutine Meas\_549 is called and another ADC conversion is accomplished as the program goes through the subroutine from line 7 through line 17. This continues again if ADCData contents are still lower than 07FH (which is 127 of a total of 256 of the full-scale content of ADCData. The value 127 is less than  $0.5V_{CC}$ , where  $V_{CC}$  is represented by the full-scale value of 256.

When the ADCData register contents are greater than 07Fh, then the program does not jump back to “Mainloop” but continues on to line 21.

21. The twenty-first line of code is:

| Label | Instruction | Operands     |
|-------|-------------|--------------|
|       | bis.b       | #01h, &P1OUT |

The instruction “set bits in destination, byte mode” means that the zero bit of the P1OUT register designated by the source 01h will be set to a one, or a high level. As a result, pin P1.0 will be set to a 1. This high level on P1.0 will light the LED that is connected to P1.0.



22. The twenty-second line of code is:

| Label | Instruction | Operands |
|-------|-------------|----------|
|       | jmp         | Mainloop |

The instruction “jump” tells the program to jump unconditionally to the line of code labeled “Mainloop” or line 6. Line 6 calls the subroutine “Meas\_549” and the whole measuring process begins again.

### ***Variation of Threshold***

The threshold voltage at which the system turns on the LED can be adjusted based on the binary number used for the comparison in the instruction of line 19. The relationship of the contents of R11, the register labeled as ADCData, to the percentage of  $V_{CC}$  is shown in *Figure 7-18b*. For  $+0.5V_{CC}$ , the binary number used in the comparison instruction was 07Fh, or one less than the binary number of 08F representing exactly  $+0.5V_{CC}$ . In like fashion, the binary number used for line 19 is 03Fh for  $+0.25V_{CC}$  and 0BFh  $+0.75V_{CC}$ . Other binary numbers per *Figure 7-18b* would adjust the trigger threshold to a selected percentage level of  $V_{CC}$ .

### ***Summary***

In this chapter the reader is exposed to the techniques used to program in assembly language. The Texas Instruments MSP430 microcontroller was chosen as the digital processor to use to explain assembly-language programming. Using its specific instruction set, the basics of writing an assembly-language program were discussed. Three assembly-language programs were discussed in detail to help the reader understand the concepts of assembly-language programming. With an assembly-language program, an assembler—a specific software program written to convert the assembly-language program into machine code—must be used before the program can be applied in a system. The next chapter will deal with the techniques of data transmission.

## Chapter 7 Quiz

1. A RISC microcontroller is:
  - a. a reduced, minimized component CPU.
  - b. a much more complicated CPU design.
  - c. based on a reduced-instruction-set CPU.
  - d. a CPU with reduced peripherals around it.
2. A von Neumann architecture:
  - a. is rectangular and triangular in nature.
  - b. has a separate bus for program memory and data memory.
  - c. has a separate bus just for peripherals.
  - d. has program, data memory and peripherals all sharing a common bus structure.
3. A peripheral module in the MSP430 family can be:
  - a. either a 16-bit or an 8-bit module.
  - b. can only be a 16-bit module.
  - c. can only be an 8-bit module.
  - d. a module with only 5-bits.
4. The peripherals in the MSP430 family:
  - a. use 16-bits exclusively for addressing.
  - b. use both 8-bit and 16-bit addresses.
  - c. use 8-bits exclusively for addressing.
  - d. use 12-bits exclusively for addressing.
5. The operating mode of the MSP430 microcontroller is:
  - a. determined by the I/O input number one.
  - b. determined by the state of the CPU.
  - c. determined by four control bits in the status register.
  - d. all of above.
6. Interrupts control the digital processor:
  - a. at specific well defined times.
  - b. at unexpected or random times.
  - c. at the same time every time.
  - d. at regular predetermined repeating times.
7. Timers are used in a MSP430 system:
  - a. to keep track of elapsed time.
  - b. to set time intervals within which specific actions occur or are to occur.
  - c. to produce resets, alerts or warnings.
  - d. none of above.
  - e. all of above.
8. When a source or destination in a MSP430 instruction have the form &ADDR, the addressing mode is:
  - a. symbolic mode.
  - b. register mode.
  - c. absolute mode.
  - d. indexed mode.
9. The MSP430 status register, R2:
  - a. has nine active bits.
  - b. has bits whose state dictates that a particular action has occurred.

- c. is one of sixteen 16-bit registers in the CPU.
  - d. all of above.
  - c. none of above.
10. The MSP430 status register bit:
- a. N is set when the result of a byte or word operation is negative.
  - b. Z is set when the result of a byte or word operation is zero.
  - c. C is set when the result of a byte or word operation produces a carry.
  - d. all of the above.
  - e. none of the above.
11. The MSP430 clock system control registers are:
- a. registers R4, R5 and R6.
  - b. BCSCTL1, BCSCTL2 and DCOCTL.
  - c. registers R7, R8 and R9.
  - d. registers R13, R14 and R15.
12. If the XTS bit in the BCSCTL1 control register is set to a 1:
- a. The LFXT1 oscillator in the clock system can operate with a high-frequency crystal.
  - b. the LFXT1 oscillator is OFF.
  - c. the LFXT1 oscillator in the clock system can operate with a low-frequency crystal.
  - d. it is a “don’t care” condition for the LFXT1 oscillator.
13. When the SELS bit in the BCSCTL2 control register is reset to 0:
- a. the DCOCLK is OFF.
  - b. the SMCLK is divided by 8.
  - c. the source for the SMCLK clock is LFXT1 oscillator.
  - d. the source for the SMCLK clock is DCOCLK.
14. In the MSP430, the watchdog timer control bit WDTTMSSEL:
- a. is set to 1 so that the watchdog timer is an interval timer.
  - b. is reset to 0 to have the watchdog timer inactive.
  - c. is not a factor in the operation of the watchdog timer.
  - d. is the bit that restarts the watchdog timer.
15. The WDTCTL control register must have:
- a. all its high-byte bits at 0.
  - b. a 069h password automatically inserted in the high byte when WDTCTL is read.
  - c. a password of 05Ah in the high byte if the instruction is to write to WDTCL.
  - d. all its high-byte bits at 1.
  - e. only b and c above.
  - f. only a above.
16. In the MSP430 system all I/O ports:
- a. are initially outputs when the system powers up.
  - b. remain constant as the applications program proceeds.
  - c. vary with each step of the program.
  - d. are initially inputs when the system powers up.
17. To set an external pin of an I/O port to be an output:
- a. the associated bit of PxDIR direction register must be set to 1.
  - b. the associated bit of PxSEL function-select register must be set to a 1.
  - c. the associated bit of the PxIN register must be set to a 1.

- d. the associated bit of the PxOUT register must be set to a 1.
- 18. When an external pin on the MSP430 I/O port is programmed to be an input:
  - a. the direction register bit associated with the pin is reset to a 0.
  - b. the PxIN register bit associated with the pin is set to whatever the input data dictates.
  - c. the PxOUT register bit associated with the pin is inactive.
  - d. all of above.
  - e. a and c only above.
  - f. none of above.
- 19. When an assembler program for the MSP430 sees a symbolic name:
  - a. it has been programmed to interrupt the processor.
  - b. it has been programmed to reset the system.
  - c. it has been programmed to insert a specific binary number that represents the symbol.
  - d. it has been programmed to disregard the symbolic name.
- 20. Symbolic name reference lists prepared for the MSP430 family:
  - a. are used exclusively for the I/O bits.
  - b. are used extensively for setting up initial conditions for the system.
  - c. are used sparingly in assembly-language programming.
  - d. are used to develop special symbols unrelated to actual register bits.
- 21. Labels:
  - a. identify particular positions in a program.
  - b. bear no relationship to the program.
  - c. are only used at the end of a program.
  - d. are not very useful in programming microcontrollers.
- 22. The .b in an instruction means:
  - a. it is dealing with a 16-bit word.
  - b. the instruction is part of a subroutine.
  - c. the instruction is to be used later in the program.
  - d. it is a byte instruction dealing only with the 8 bits in the lower byte of a word.
- 23. Operands are:
  - a. special types of AND logic circuits.
  - b. the portion of the instruction that identifies what quantities will be operated on using the instruction.
  - c. special amplifiers used in signal conditioning a signal.
  - d. the first component in an instruction line.
- 24. Hexadecimal numbers:
  - a. use bit positions that are entirely different than binary codes.
  - b. cannot be manipulated easily in binary systems.
  - c. use numbers from 0 to 9 and letters from A to F to identify the 16 possible codes when using a 4-bit code.
  - d. use no special notations to identify them in programs.
- 25. Assembly-language programming:
  - a. helps to grasp the concept of programming.
  - b. helps to learn programming details.
  - c. helps to get familiar with programming format.
  - d. all of above.

- e. b and c only above.
- 26. In assembly-language programming for the MSP430:
  - a. “syntactic substitution” is the technique of substituting numbers for words in a program.
  - b. the program instructions are converted to machine code by an assembler.
  - c. specific registers used for given tasks may be defined in a reference list.
  - d. the numbers used in the “syntactic substitution” are defined in a reference list.
  - e. all of above.
  - f. c and d only above.
- 27. In assembly-language programming for the MSP430, a label:
  - a. has many uses but one important one is to identify a subroutine.
  - b. only provides reference to a particular action in a program.
  - c. has little meaning in a program.
  - d. is the most prominent way to set initial conditions.
- 28. In an assembly-language program for the MSP430:
  - a. a .w after an instruction means a decimal instruction.
  - b. a .w after an instruction means a hexadecimal instruction.
  - c. a .w after an instruction means to branch to another location.
  - d. a .w after an instruction means it is an operation using a word (two bytes).
- 29. In assembly-language programming for the MSP430:
  - a. a # sign before an operand means it is register-mode addressing.
  - b. a # sign before an operand means it is immediate addressing.
  - c. a # sign before an operand means it is absolute-mode addressing.
  - d. a # sign before an operand means it is symbolic-mode addressing.
- 30. In MSP430 programming using assembly language:
  - a. a reference list is very important to syntactic substitution.
  - b. the programming depends totally on syntactic substitution.
  - c. a reference list is not important to syntactic substitution.
  - d. all syntactic substitution reference lists are constant for any application.

Answers: 1.c, 2.d, 3.a, 4.b, 5.c, 6.b, 7.e, 8.c, 9.d, 10.d, 11.b, 12.a, 13.d, 14.a, 15.e, 16.d, 17.a, 18.d, 19.c, 20.b, 21.a, 22.d, 23.b, 24.c, 25.d, 26.e, 27.a, 28.d, 29.b, 30.a.

# Data Communications

## Introduction

A typical requirement of systems described in this book is that digital information must be transported from one location to another, from one piece of digital equipment to another. The two locations may be very close to each other, or they may be separated by a great distance. In this chapter, data communication systems will be discussed and several techniques used to transmit and receive digital data will be examined.

## The Data Transmission System

Figure 8-1 shows a typical digital data communications system. Any digital communication must have a transmitter, receiver and a transmission medium. The transmitter prepares the digital information for transmission, the receiver detects and presents the digital information in original form, and the transmission medium transports the information, hopefully without modifying it or producing errors. The transmission medium may be twisted pair wire, wires in cables, fiber optic cable or wireless transmissions.

 


Figure 8-1: Data communication system

## DTE and DCE

In Figure 8-1, a data terminal equipment, DTE, is coupled to a piece of data communications equipment, a DCE. The most common DCE is a modem that converts the digital data into signals that match the requirements of the transmission medium. A very common arrangement is a modem that couples to a telephone line. The DTE in this common case is a computer. In fact, the DCE (modem) is contained right in the computer, and the DTE and DCE combination becomes the transmitter for this data communications system.

At the receiving end, another DCE (again, another modem) receives the data from the transmission medium, decodes it and presents it to a DTE for transformation, manipulation, modification and/or display. As shown in Figure 8-1, each combination of DTE and DCE can either be a transmitter or a receiver depending on the direction of transfer of data.


Also shown in Figure 8-1 is the fact that a DTE can be a computer, a printer, or a video monitor, and that beside the DTE to DCE and DCE to DTE data communication, there is and can be data transfers from a DTE to a DTE.

## Parallel and Serial Transmission


There are two main methods of communicating digital data from one place to another, either parallel transfer or serial transfer. Figure 8-2 shows the difference between the two. Parallel transfer is shown in Figure

8-2a. Here there are as many separate signal lines as there are bits of data in the digital signal. If the bits in the data change, all bits change at the same time. In other words, there is an information front that moves together on the lines, and when a change in the data is made all lines change at the same time.

Contrast this to serial transfer of data shown in *Figure 8-2b*. Here there is only one line, and if one would sit on the line, the digital bits representing the information would pass by one bit after the other—in series, thus, the name serial data. Additional data must be added to the digital data to make sure it is recognized. A start bit must be added to tell when the data starts, and a stop bit is added to tell when the data stops. A parity bit, which will be discussed later, is added to aid in correcting errors.

 

 a. Parallel transfer of information for ASCII “W” (odd parity)



b. Serial transfer of information for ASCII “W” (odd parity)

Figure 8-2: Parallel and serial data transmission

## Major Differences

The major differences between parallel and serial transfer are shown in *Figure 8-3*. As noted, serial transfers require only one line, while parallel transfers require a line for each bit of the multiple-bit character being transferred. If a moment of time is picked,  $t_x$  in *Figure 8-2a*, each line will have a bit value corresponding to the digital code for the character being transferred, 1110101 for *Figure 8-2a*. While in a serial transfer, as shown in *Figure 8-2b*, the bit values will come one after another at  $t = t_x$ . First, the start bit, then the character bits, a parity bit and then the stop bit. Thus, the speed of transferring of data for serial communications is slower than for parallel. In parallel communications, all the bits arrive at the same time, while in serial communications, one must wait until all bits arrive.

It is very difficult in parallel communications to keep the time relation between bits the same for each line as the distance of the transmission increases; therefore, the connecting cables are usually short—a computer to a printer, or one computer to another, or a computer to a video monitor. There are parallel communications that occur over long distances that use what is called a packet technique and over special transmission lines or on microwave links. These are discussed briefly, and then explained a bit further for the USB protocol,

|                          | PARALLEL                  | SERIAL                        |
|--------------------------|---------------------------|-------------------------------|
| Lines Required           | One line/bit              | Single line                   |
| Bit Sequence             | On all lines at same time | One bit following another     |
| Speed                    | Faster                    | Slower                        |
| Transmission line length | Usually a short distance  | Both long and short distances |
| Cost                     | More expensive            | Less expensive                |
| Critical Characteristic  | Time relationship of bits | Needs start, stop bit         |

Figure 8-3: Comparison of parallel and serial communications


but are really beyond the scope of this book. More detailed texts are required to explain it fully. Serial communications, on the other hand, using the latest technology, normally occurs over very long distances.

The equipment required for serial communications is less expensive since only one line is of concern rather than multiple lines in parallel communications. If 10-bit characters are being transmitted in parallel, the equipment multiplies by at least 10 times over what it is for serial communications. In parallel communications, one of the critical characteristics is the time relationship of signals on the line. In serial communications, additional information—a start and stop bit—must be added to be able to recognize and detect the information.

### Example 1. Shift Right from Register

Show the bit storage in the lower byte of Register R5 for an ASCII capital N and the waveform generated as the ASCII code is shifted right out of the register. Odd parity is to be used. The ASCII code is shown in *Figure 8-5*.

**Solution:**

 

### Protocols

“Protocol is the name given to hardware and software rules and procedures for making sure that any transmission errors are detected.”<sup>1</sup> Data communications must follow certain rules and procedures as noted by the above quote whether it be the hardware used, the electrical signal levels, the signal timing, or the software used. *Figure 8-4* shows one of the earliest protocols, the RS-232 interface. It was used, and is still used today, to connect together all types of data communications equipment.

 


Figure 8-4: RS-232 protocol

<sup>1</sup> *Understanding Data Communications*, G.E. Friend, et al. ©1984, Texas Instruments Incorporated.



In *Figure 8-4a*, the electrical characteristics of an RS-232 signal are shown. The two binary levels are identified as “Mark” and “Space.” In the RS-232 protocol, the receiver recognizes any positive signal from +3V to +25V as a space, and any negative signal from –3V to –25V as a mark. The transmitter, on the other hand, by specification, produces a space signal level between +5V and +25V, and a mark signal level between –5V and –25V. The mechanical connector and its associated pin connections are shown in *Figure 8-4b*.

Now look again at *Figure 8-2b*. Here the mark is identified as the 1 level and the space the 0 level. In modern day electronics, due to the influence of integrated circuits, and due to T<sup>2</sup>L and CMOS logic circuitry, the 1 or mark is a high level from +2.4V to +5V, and the 0 or space level is a low level of +0.4V to 0V. When the RS-232 protocol was set, the maximum transfer speed was 20,000 bits per second, and the modem speeds were no higher than 9600 baud per second. USB, which will be discussed later, is a much more recent protocol for serial data communications and can transfer data at 4 million bits per second.

## High-Speed Data Transmissions

As indicated, parallel data communications are limited by the length of the parallel wire cables; therefore, different techniques are used for such communications. Microwave, fiber optics, satellites are used for the transmission medium. The digital data is grouped into frames and packets to allow the data to be transmitted at millions of bits per second. Error detection and correction bits are added to the format so that the data can be communicated efficiently and without error at great speeds. This is possible because of the very wide bandwidth provided by microwave, fiber optic and satellite transmission links. Even though digital data communications require more bandwidth than analog signals, the very wide bandwidth is sufficient and available to allow high-speed digital data transmissions at ever increasing speeds.

## Serial Data Communications Advances

The most common data communications today are serial communications. Even though the bits of a character flow in series one after another, the advances in technology, especially in the speed at which digital ICs can process digital information, have advanced so that the transfer speeds have kept up with the industry. As a result, the emphasis for the rest of this chapter will be on serial data communications. The discussion starts with a return to *Figure 8-2b*.

## A Return to the Format

The two levels, Mark and Space, will be examined further. These terms come from the telegraph era. A pen attached to the armature of the sounder in a telegraph system would make a **mark** on paper moving under the pen as the armature was activated with the incoming signal. With no activation of the armature, the paper would just **space**. As the names for the two levels continued to be used, the mark was the state, of two available, in which there was a current. Space was identified as the state of no current. Still further use gave the idling state the name of “Mark” even though current was flowing. In this book, corresponding to accepted IC logic level, a “Mark” is the high level or a 1, and a “Space” is the low level or a 0. The RS-232 levels discussed before are really negative logic levels with a “Mark” being the most negative voltage level or a 1, and the least negative voltage level (the most positive level) a “Space” or a 0.

## Start, Data and Stop Bits

As shown in *Figure 8-2b*, a start bit identifies the start of the data transfer. It is generated by changing the level from a 1 to a 0. Following the start bit are the bits used to determine the data. Seven bits are used in this example because a common binary code used for text data transfer is the ASCII (American Standard Code for Information Interchange) code shown in *Figure 8-5*. The ASCII code for “W” was used in *Figure 8-2*.

|                |   |   |   |   |   |   |   |
|----------------|---|---|---|---|---|---|---|
| Bit Positions: |   |   |   |   |   |   |   |
| 7              | 6 | 5 | 4 | 3 | 2 | 1 |   |
| 0              | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0              | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0              | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0              | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0              | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0              | 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0              | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0              | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0              | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0              | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1              | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1              | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1              | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1              | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1              | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1              | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1              | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1              | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1              | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1              | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1              | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1              | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1              | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1              | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

Examples:

|            |   |   |   |   |   |   |   |                       |
|------------|---|---|---|---|---|---|---|-----------------------|
|            | 7 | 6 | 5 | 4 | 3 | 2 | 1 | bit                   |
| A          | 1 | 0 | 0 | 0 | 0 | 0 | 1 |                       |
| a          | 1 | 1 | 0 | 0 | 0 | 0 | 1 |                       |
| j          | 1 | 1 | 0 | 1 | 0 | 1 | 0 |                       |
| k          | 1 | 1 | 0 | 1 | 0 | 1 | 1 |                       |
| zero       | 0 | 1 | 1 | 0 | 0 | 0 | 0 |                       |
| space (SP) | 0 | 1 | 0 | 0 | 0 | 0 | 0 |                       |
| CR         | 0 | 0 | 0 | 1 | 1 | 0 | 1 | (carriage return)     |
| EOT        | 0 | 0 | 0 | 0 | 1 | 0 | 0 | (end of transmission) |

Figure 8-5: ASCII code

Following the seven bits of data, there is a parity bit and one or two stop bits. In case the data is eight bits, there would be a parity bit and only one stop bit. The stop bit is a continuous 1 level or idle condition.

## Parity Bit

The parity bit is a bit of information added to the original data to allow for error detection. The bit is added by the transmitter to make the sum of all 1 bits in the character transmission either odd or even. The error detection method is called odd parity if the sum of the 1 bits is made odd; it is called even parity if the sum of the 1 bits is made even. *Figure 8-6* shows examples of how the transmitter adds the bits to make odd and even parity.

At the receiver, circuits count the number of 1 bits in the character that is transferred. The system has been set up previously to operate either with odd or even parity. Suppose the system is operating using odd parity. If the counters always count odd numbers of 1s as the characters are transmitted, the receiver processes the data as correct. If, however, the 1 count turns up even, the receiver flags the information as incorrect and probably asks for it to be retransmitted. Even parity calls for the receiver to count an even number of 1s, and the data will be processed as correct as long as the count remains even. The receiver only flags the data as incorrect when the count is odd.

|     |                  |   |   |   |   |   |   |                  |                   |
|-----|------------------|---|---|---|---|---|---|------------------|-------------------|
|     | 7-bit ASCII Code |   |   |   |   |   |   | Parity Bit (odd) | Parity Bit (even) |
| Bit | 1                | 2 | 3 | 4 | 5 | 6 | 7 |                  |                   |
| B   | 0                | 1 | 0 | 0 | 0 | 0 | 1 | 1                | 0                 |
| Q   | 1                | 0 | 0 | 0 | 1 | 0 | 1 | 0                | 1                 |
| 3   | 1                | 1 | 0 | 0 | 1 | 1 | 0 | 1                | 0                 |
| z   | 0                | 1 | 0 | 1 | 1 | 1 | 1 | 0                | 1                 |

These bits added by transmitter

Figure 8-6: Odd and even parity

## Example 2. Odd and Even Parity

What will the odd and even parity bit be for the digital codes given?

**Solution:**

|  |   |   |   |   |   |   |   |   |     |            |                |
|--|---|---|---|---|---|---|---|---|-----|------------|----------------|
|  | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | bit |            | Parity Bit for |
|  |   |   |   |   |   |   |   |   |     | Odd Parity | Even Parity    |
|  | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |     | 1          | 0              |
|  | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |     | 0          | 1              |
|  | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |     | 0          | 1              |
|  | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 |     | 1          | 0              |
|  | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |     | 1          | 0              |
|  | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 |     | 0          | 1              |

## Baud Rate

In Figure 8-2b seven bits are used for the ASCII character and four bits are added—a start, parity and two stop bits. The total bits per character is eleven; therefore, the number of baud is 11. Suppose the rate of transmission is 10 characters per second. The baud rate will be characters per second  $\times$  total bits per character, or, in this example,  $10 \times 11 = 110$  baud per second. Modern telephone modems operate commonly at 56,000 baud per second.

### Example 3. Baud Rate

What is the baud rate of an 8-bit data word with a start, parity and one stop bit when the transmission rate is 500 characters per second?

#### Solution:

No. of bits in serial word =  $8 + 1 + 1 + 1 = 11$  characters

Transmission rate = 500/sec

Baud rate =  $500 \times 11 = 5500$  baud/sec

## Shift Registers

The shift register was discussed previously in Chapter 6. It is a main component of a serial communication system, and data can be manipulated in a number of ways, as shown in Figure 8-7, in order to arrive as serial data. In Chapter 7, the method shown in Figure 8-7f, rotate data left, was used to transfer data to the data register in the microcontroller, and is the same as the circulate example, in this case, left, discussed previously in Chapter 6.

 



Figure 8-7: Various types of shift registers

Courtesy of Master Publishing, Inc.

### Example 4. Parallel In—Serial Out Shifting


Show the contents of register R10 for each clock cycle as a 4-bit word is transferred in a parallel transfer and stored in R10. A logical shift right is then made to examine the bits, one by one. The 4-bit code loaded in R10 is 0110.

#### Solution:

 



with each other in the synchronous mode. The left unit is the master, which supplies the clock, and the right unit is the slave. The master transmits data at the clock rate. The slave uses the clock to shift information in and out. The STE signal, controlled by the master, enables the slave to transmit data as well as receive data. The master and slave send and receive data at the same time. Data is shifted out of the transmit shift register on one clock edge and shifted in to the receive shift register on the opposite edge. The timing is shown in *Figure 8-10*.

 


**Figure 8-10: Shifting out Tx data and shifting in Rx data**

The master output of the transmit shift register is coupled through the slave-in, master-out (SIMO) line to the slave receive shift register, while the slave out of the transmit shift register is coupled through the slave-out, master-in (SOMI) line to the master receive shift register. The data moves at a synchronized rate determined by the clock supplied by the master. The right unit could just as well be the master and the left the slave, and the operation is the same. The baud rate is programmed into and controlled by a baud-rate generator that is derived from the clock in the master.

## Asynchronous Serial Communications

Asynchronous serial communications between two USARTs is shown in *Figure 8-11*. There again is a master and a slave, and the data format is the same as *Figure 8-8b*, but the frames of data do not

 


**Figure 8-11: Two USARTs communicating in asynchronous mode**

*Courtesy of Texas Instruments Incorporated*

always arrive in regular periods. There may be significant random idle periods between frames (greater than 10 bit times) as shown in *Figure 8-12*. There is no physical interconnection of clock signals from master to slave. The programmed master clock sets the transmission asynchronous serial communications rate.

As shown in *Figure 8-11*, the master is the transmitter and the slave is the receiver. When the first signals are received, the receiver adjusts its clock to match the clock rate of the received signal and uses this clock

 

**Figure 8-12: Asynchronous serial communication**

to shift in the received data. Transmission in the asynchronous mode is only one way. In order for the slave to transmit to the master, the roles of the slave and master must be reversed. The slave becomes the master, that originates the clock, and the master becomes the slave. No interconnections need change, but control signals must change. Depending on the direction that the data is to flow, the roles of the master and slave reverse as the flow of data reverses.

### The UART Function with Software.

Subprogram No. 1 of *Chapter 7* essentially implemented a shift register using software. Expanding on the technique used there, the UART function can be implemented with software. It is not covered here, but this would be a challenging project for a team of students that come in contact with this book.

### Technology Advances


Two advances in technology will be cited to demonstrate new techniques that have been developed to increase the transfer rate of digital information using serial communications. The first is the Inter-IC serial bus.

#### I<sup>2</sup>C Bus

A serial communications proprietary protocol that was developed by Philips Semiconductor<sup>2</sup>, is the I<sup>2</sup>C bus. It was developed principally for inter-IC control, thus the name I<sup>2</sup>C. All ICs that are I<sup>2</sup>C-bus compatible have on-chip interfaces that communicate directly with other I<sup>2</sup>C-bus compatible devices. Serial, 8-bit, bi-directional data transfers can be made in three modes:

1. Standard—100 kbits/sec
2. Fast—400 kbits/sec
3. High-Speed—3.4 Mbits/sec

The two-line bus has a serial data line (SDA) and a serial clock line (SCL). It is a synchronous system and requires a clock. The unit that initiates the data transfer is the master. It also is the unit that generates the clock, and initiates, permits, and terminates the transfer. If the master wants to communicate with another unit, it sends the address of that unit on the data line. The unit that is addressed is called the slave. The master and the slave can be either a transmitter or a receiver. Examples are shown in *Figure 8-13*. *Figure 8-13a* shows a master transmitting to a slave receiver; and *Figure 8-13b* shows the slave transmitting back to the master, now used as a receiver. The bus design allows multiple masters and slaves on the bus.

 


**Figure 8-13: I<sup>2</sup>C master and slave can be transmitter or receiver**

### I<sup>2</sup>C Protocol

#### Electrical Connections

*Figure 8-14a* shows the interconnection of devices inside units connected to the bus. Essentially, the SDA line and the SCL line are held in the high level by pull-up resistors until control transistors are activated to pull the line low. It is a large wired AND connection with open collector (bipolar) or open drain (MOS) connections from the devices to the lines. As SDA is activated by data and SCL by clock pulses, the lines are pulled low by the active devices. A low level is defined as a maximum of  $0.3 V_{dd}$ , and a high level as a minimum of  $0.7 V_{dd}$ .  $V_{dd}$  is typically the T<sup>2</sup>L logic level of 5V.

<sup>2</sup> I<sup>2</sup>C-Bus Specification, V2.1, Philips Semiconductor.

 
Figure 8-14: I<sup>2</sup>C protocol

## Signal Timing

Figure 8-14b shows the necessary timing of information on the bus. To generate the necessary start bit, SDA must be pulled from high to low while the SCL line is high. Data on SDA is valid only while SCL is high, and data cannot change (without error) unless SCL is low. A stop bit is generated when SDA goes from low to high when SCL is high. Thus, the start bit, data bit and stop bit requirement of the serial format is satisfied.
 
### Example 5. I<sup>2</sup>C Data

Determine the data bits in the I<sup>2</sup>C waveform shown. See Figure 8-14b for signal protocol.



## Format

An example of the serial format for a master-transmitter to a slave-receiver is shown in *Figure 8-14c*. The format starts with a start bit, then the address from the master to identify the slave, then a low on the R/W bit, and finally the data. Data continues to be sent by the transmitter as acknowledgement bits (A) are placed on the bus by the receiver. When no acknowledgement is received, the master-transmitter sends a stop bit.

## USB

Another still more advanced serial data communications protocol is the universal serial bus (USB). It is being used extensively to communicate data from DTE to DTE, from DTE to DCE and from DCE to DTE. Using USB, serial data can be transferred at three different rates. Using USB low speed, the transfer rate is 1.5 million bits/sec; using USB full speed, the transfer rate increases up to 12 million bits/sec; and using USB high speed, the transfer rate is up to 480 million bits/sec. The discussions in this chapter center on USB low speed and full speed. The reader is left to investigate the specifications for USB high speed.

The connecting cable used is shown in *Figure 8-15*. It is a 4-wire system, using a twisted pair for D+ and D- data lines, and power lines of  $V_{BUS}$  and GND. It uses a unique feature of differential detection of data on the D+ and D- lines.

 


Figure 8-15: 4-wire USB cable

## USB Network

A typical USB network is shown in *Figure 8-16*. It consists of a host, which contains a host controller, and separate USB devices. These devices, as shown, can either be a function or a hub. A function is a USB device that is able to transmit or receive data or control information over the bus. It contains information about its capabilities and the resources that it needs. Examples of functions are mouse controllers, light pens, keyboards, printers, scanners, and so forth.

Hubs are USB devices that expand the USB bus interconnections. They allow the attachment of multiple USB devices. The host, as shown in *Figure 8-16*, can be connected to a function or a hub, and that hub can be connected to other hubs or other functions. In addition, there is overriding software that manages the bus. USB permits the host to configure a hub and monitor and control its ports.

The host is responsible for knowing when devices are connected or disconnected from the bus, for managing the data flow between USB devices, and for the status of the bus. The host assigns a unique address to a device attached to it. It determines if the new device is a hub or a function. If the device is a function, the host recognizes this and configures it. If the device is a hub, the host's software establishes the unique addresses and end points for all devices attached to the hub. All USB devices support a common means for accessing information to control the end points.

 


Figure 8-16: USB network



## USB Electrical Connections

Figure 8-17 shows the USB electrical interconnections of the bus. The host controller is required to have a root hub that contains a transceiver. All hubs, including the root hub, are required to support both full-speed and low-speed data transfers. Functions may just support low speed.

 


Figure 8-17: USB interconnections

Transmission from the host is called downstream; transmission to the host is called upstream. At the host, root hub, and any external hub, the D+ and D- lines at downstream ports each have a 15 k $\Omega$  pull-down resistor to ground. On a port feeding upstream from a device or hub, a 1.5 k $\Omega$  pull-up resistor is connected between the D+ line and a voltage supply from +3.0V to +3.6V. If it is a low-speed device, the 1.5 k $\Omega$  resistor is connected from the D- line to the voltage source. An external hub is a special case that has both 1.5 k $\Omega$  resistors on up-stream ports and 15 k $\Omega$  pull-down resistors on the downstream ports. The impedance of the USB cable is 90  $\Omega$ .  $V_{BUS}$  is nominally +5V at the source. The host supplies power to USB devices directly connected to it. A hub supplies power to its connected devices; however, some connected devices have internal power sources.

## Bus Transceivers

The details of the transceivers are shown in Figure 8-18. Note that there are differential receivers for the data lines, and also single-ended receivers, one for each data line. The single-ended receivers are used for control purposes. There are output buffers that drive the data lines when transmitting data. Each of the output buffers have an enable input because the buffers must have a 3-state high-impedance output when not enabled. This means the buffers, when not enabled, are no load on the bus. The output buffer for the function transceiver has another input to control whether it is operating at low speed or full speed.

 


Figure 8-18: A possible USB system showing receivers at host and function

When the host is transmitting, its output buffers are enabled and drive the data lines differentially; the function output buffers are disabled. When the function is transmitting, its output buffers are enabled and drive the data lines differentially; the host output buffers are disabled. When not transmitting the output buffers are disabled. At low speed, two changes occur—the 1.5 kΩ resistor’s termination is to the D– line instead of the D+ line, and the logic levels are reversed.

Data Line Waveforms

The differential signals plotted against time are shown in *Figure 8-19*. The data signals swing between 2.8V ( $V_{OH(min)}$ ) and 0.3V ( $V_{OL(max)}$ ). When D+ is greater than 2.8V and D– is less than 0.3V, the differential logic state is a 1; when D+ is less than 0.3V and D– is greater than 2.8V, the differential logic state is a 0. The point where the waveforms cross is called

$V_{CRS}$ , the voltage crossover point. It must be between 1.3V and 2.0V. The amplitude A should be approximately the same for each transition. The logic states are also called the J and K states. The J and K states are inverted, as shown in *Figure 8-19*, for low speed and full speed operation. This is the reason for the extra logic inverters in the function called for in *Figure 8-18*. The rise and fall times of the waveforms must be 75–300 nS for low-speed operation and 4–20 nS for full-speed operation.

 



Figure 8-19: Data line switching waveforms

USB Signal Protocol

The USB is a polled bus. The host controller initiates all data transfers. All bus transactions involve the transmission of three packets diagramed in *Figure 8-20*. Each transmission begins when the host controller, on a scheduled basis, sends a “token packet” describing the type and direction of the transmissions, the USB device address, and an end-point number. The USB device that is addressed selects itself by decoding the appropriate address fields.

 Example 6. USB Host-to-Function Addressing

A USB network has the host transmitting downstream to four functions with addresses as shown. The host transmits an address 0010. What happens?



In a given transaction, data is transferred either from the host to a device, or from a device to a host.

The direction of transfer is specified in the token packet. After the direction is set, the source sends data packets, or else indicates it has no data to transfer.

When a transfer is received, the destination, in general, responds with a “handshake” packet that indicates the transfer was successful. Each packet is preceded by sync signals, called a sync field, and includes a control portion, a data portion and an error-correction field. The error correction is for single and double bit errors. The sync field, which is really a clock signal, is transmitted and encoded along with the differential data, and allows the receiver(s) to synchronize their bit recovery clocks. After the last bit of the packet, as shown in *Figure 8-20*, both D+ and D–, as single-ended signals, are driven to 0.


The data line is then driven to the high level to indicate an end to the packet. The output buffers are then driven to their high-impedance state so that the data bus floats. There are limitations on the capacitance loading and propagation delays so that signal reflections can be controlled.

## Data Transfers


There are three types of information transfers: sync, control and data. The sync, control and data transfers between the host and a USB device can be one-way or two-way. The sync transfers synchronize the receivers. The control transfers configure devices when they are first connected or when there is any change in the device status. Data transfers are of three types: bulk, interrupt and real time. Bulk data transfers are for large amounts of data between a host and a printer or scanner that requires data accuracy. Interrupt transfers, as from a mouse for a computer, is for data that may be presented at random times. Real-time data transfers, such as voice transmissions, that need to occur in real time and have no error correction, but must continue to be transmitted, are called isochronous transfers.

## Data Encoding

The transfers are encoded using a “nonreturn-to-zero” encoding as detailed in *Figure 8-21*. If the data is 0, the encoding changes; if it is a 1, it does not change. This encoding, as shown in *Figure 8-22*, produces a clock type sync field at the beginning of a packet. This is the signal that synchronizes the receiver of the packet. The rules for

 


**Figure 8-20: Example of a possible packet and data format**

 

**Figure 8-21: Nonreturn-to-zero encoding**


the sync pulse preceding the packet are that seven 0s and a 1 are to be transferred as the sync field. When encoded it produces the sync field shown in *Figure 8-22*.

 

**Figure 8-22: Sync signals prefixed to packet**
 
### Example 7. NRZ Encoding

For the data waveform shown, what would the encoded waveform be when using nonreturn-to-zero (NRZ) encoding? The rules for encoding are: if data = 0, encoding waveform changes; if data = 1 encoded waveform does not change.



### Summary

Data communications using parallel and serial techniques has been the subject of this chapter. The protocols, data format and techniques showed that parallel communications are the fastest but most expensive. Advances in technology have caused the less expensive serial communications to keep pace with the requirements of the hardware. New transmissions using I<sup>2</sup>C and USB show how these protocols are keeping pace. In the next chapter, power systems and their control will be discussed.

## Chapter 8 Quiz

1. A digital data communication system is:
  - a. made up of a transmitter and a transmission medium.
  - b. made up of a transmitter, receiver and a transmission medium.
  - c. made up of a receiver and a transmission medium.
  - d. made up of just the transmission medium.
2. In digital communications, a parallel transfer means that:
  - a. digital data is transferred at a faster speed.
  - b. if bits in digital data change, they all change at the same time.
  - c. it is the most economical way of transferring data.
  - d. each bit of the digital data has a separate data line.
  - e. c only above is correct.
  - f. a, b and d above are correct.
3. In digital communications, a serial transfer means that:
  - a. it is the fastest way of transferring data.
  - b. the transfer of data is just on one line.
  - c. the digital data arrives one bit after another in sequence.
  - d. it cost less to transfer data than using parallel transfers.
  - e. a only above is correct.
  - f. b, c and d above are correct.
4. A communications protocol is:
  - a. a set of communication system schematics.
  - b. a set of rules that applies only to digital data communications hardware.
  - c. the hardware and software rules and procedures for making sure that transmission errors are detected.
  - d. a set of rules that applies only to digital data communications software.
5. Serial data communications is the prime digital data transfer method because:
  - a. advances in IC technology have kept up with the bit transfer rates required by industry.
  - b. it needs more equipment (hardware) than parallel transfers.
  - c. it is much more expensive than parallel transfers.
  - d. it is faster than parallel transfers.
6. In serial digital data communications, what must be added to the data?
  - a. Only start and stop bits.
  - b. Just parity bit.
  - c. Start, stop and parity bit for error detection and correction.
  - d. Some error-detection and error-correction scheme.
7. Odd parity:
  - a. is when an additional bit is added to the data to make the sum of the 1 bits odd.
  - b. means it is a strange set of rules.
  - c. is when an additional bit is added to the data to make the sum of the 1 bits even.
  - d. improves the baud rate.
8. A USART is:
  - a. a universal synchronous/asynchronous receiver/transmitter DCE.
  - b. a DCE used extensively for serial data communications.
  - c. a DCE that can only be used for synchronous transmissions.

- d. a DCE that can only be used for asynchronous transmissions.
  - e. only c above.
  - f. only a and b above.
9. When two USARTs communicate synchronously:
- a. there is no common clock.
  - b. the clock is generated externally.
  - c. there are two independent clocks, one in transmitter and one in the receiver.
  - d. there is a common clock either in the transmitter or the receiver.
10. When two USARTs communicate asynchronously:
- a. there is a common clock either in the transmitter or the receiver.
  - b. there is no physical interconnection of clock signals.
  - c. the clock is generated externally.
  - d. the frames of data arrive in regular periods.
11. I<sup>2</sup>C-Bus means:
- a. a combination of amplifier integrated circuits.
  - b. a current squared times a capacitor value.
  - c. a serial communications bus protocol developed for inter-IC control.
  - d. a bus used for parallel data transfers.
12. I<sup>2</sup>C is:
- a. a 2-line bus synchronous system that requires a clock.
  - b. a 2-line bus that has a master and a slave.
  - c. a 2-line bus where the transmitter or receiver can be the master or slave.
  - d. a 2-line bus where the master initiates the data transfer and generates a clock.
  - e. a 2-line bus where the unit that is addressed is the slave.
  - f. b, c and d only above.
  - g. all of a, b, c, d and e above.
13. The universal serial bus (USB) is:
- a. a 2-wire system with a twisted pair for the data lines.
  - b. a system that has all hubs in its network.
  - c. a 4-wire system with differential signal detection of data on the D+ and D– data lines.
  - d. a system that operates using +2.5V.
14. The four wires of the USB system are:
- a. D+, D–,  $V_{BUS}$  and GND.
  - b. GND,  $V_{DD}$ ,  $V_{OH}$  and  $V_{OL}$ .
  - c. GND,  $V_{CC}$ ,  $V_{OH(min)}$  and  $V_{OL(max)}$
  - d. D+, D–,  $V_{OH(min)}$  and  $V_{OL(max)}$
15. USB networks have:
- a. a host controller with a root hub and transceiver.
  - b. hubs or functions connected to the root hub.
  - c. a 90Ω transmission cable.
  - d. an upstream and downstream transmission direction.
  - e. all of the above.
  - f. only a and b above.
16. A USB transceiver has:
- a. three op amps and a power amplifier.

- b. two power amplifiers and three tuned-stage amplifiers.
  - c. a class C, a class A, a Class AB and a class B amplifier.
  - d. differential receivers, single-ended receivers, and output buffers.
17. A USB network:
- a. identifies a 1 or 0 of data using single-ended signals.
  - b. identifies a 1 or 0 of data using differential signals.
  - c. identifies a 1 or 0 of data using class AB amplifiers.
  - d. none of the above.
18. In the USB network:
- a. the transmitter sends a sync signal to synchronize the receiver.
  - b. the receiver runs freely at its own clock rate.
  - c. the receiver has a physical wire connection with the transmitter.
  - d. the USB device that is addressed selects itself.
  - e. a and b above.
  - f. a and d above.
19. At the end of a USB packet transmission:
- a. the transceivers buffers are still actively connected to the bus.
  - b. the D+ and D– lines are both at a 1 level.
  - c. the output buffers in the transceivers are put into their high-impedance state.
  - d. the sync signal is inserted.
20. In a USB packet transmission:
- a. there is no error-correction information.
  - b. there only is data in the packets.
  - c. the single-ended transmission is susceptible to noise.
  - d. seven 0s and a 1 are transmitted to develop sync pulses.

20.d.

Answers: 1.b, 2.f, 3.f, 4.c, 5.a, 6.c, 7.a, 8.f, 9.d, 10.b, 11.c, 12.g, 13.c, 14.a, 15.e, 16.d, 17.b, 18.f, 19.c,


# System Power and Control

## Introduction


All electronic systems require a source of power. In almost all cases the voltage and current values are specified. The current value is in amperes as a load on the supply, and the voltage value is to be held within a specified tolerance (usually a percentage of the nominal value) as the current value varies within specified limits as the load changes. The nominal value of voltage times the nominal value of current determines the watts of power required of the supply. In this chapter, not only will the source of the voltages and their regulation be discussed, but the way the supply voltages are distributed throughout a system. In addition, the sophisticated circuits that are now available to monitor, detect and protect systems from damage, errors and failure will be discussed.

## AC to DC Power Supplies


Figure 9-1a shows a general AC to DC power supply. Its source is the alternating current voltage of 120VAC or 250VAC, 60 Hz that is distributed commercially by the local power company. The alternating voltage varying plus and minus around zero is rectified into voltages that vary only above zero. The

 

a. AC to DC power system

 

 b. AC to DC power system isolated from AC line



c. AC to DC power system not isolated from AC line

Figure 9-1: Examples of AC to DC power supplies



half-alterations are passed through a filter that produces a DC voltage of designed amplitude. A small ripple voltage results from the amount of filtering compared to the input voltage variations. The ripple is superimposed on the DC voltage and represents a so-called noise. Because the output voltage must be controlled accurately within tight tolerances, a voltage regulator (or it could be a current regulator) is required. The voltage is held to within 1% to 10% of  $V_{OUT}$  over the specified load current and its changes depending on the application and type of regulator.

Many AC to DC power supplies must be isolated from the incoming AC line. *Figure 9-1b* shows such a design using a full-wave rectifier and transformer isolation. If the power supply need not be isolated, *Figure 9-1c* shows a design using a bridge rectifier supplied directly from the AC line.

## Voltage Regulators

### Zener Regulator

*Figure 9-2* shows different versions of linear voltage regulators. The simplest of these is shown in *Figure 9-2a*. It consists of a zener diode and a resistor connected to a voltage  $V_{IN}$ . A zener diode is a semiconductor diode designed to operate in the reverse-biased avalanche region (similar to breakdown) that has the characteristic of maintaining a constant voltage across it as the current through it varies. It must have a minimum current,  $I_{Z(min)}$ , through it to operate properly, and because of a power dissipation temperature limit, it can

 


Figure 9-2: Linear voltage regulators

TEAM LRN

handle only up to a maximum current,  $I_{Z(\max)}$ . Here is how it works as a regulator.  $I_Z$  can be any value from  $I_{Z(\min)}$  to  $I_{Z(\max)}$ , and  $V_O$  will remain within a specified percentage of  $V_O$ . Initially with no-load,  $I_L = 0$ , the series resistor is set so that the current is  $I_{Z(\max)}$ . When  $I_L$  is increased,  $I_Z$  decreases, but  $V_O$  will remain within specified limits until  $I_Z = I_{Z(\min)}$ . Thus,  $I_L$  varies over its range but  $V_O$  remains within specified limits. The zener diode is not a regulator for wide variations in current; it is more a regulator for a constant load with little variations. Currents that it can handle are usually less than 100 milliamperes (100 mA).

### Example 1. Zener Voltage Regulator

A Zener diode has the characteristics shown for points 1 and 2. What is the percent load regulation when the load changes between point 1 and point 2?

|         | $V_Z$ | $I_Z$  |                                 |
|---------|-------|--------|---------------------------------|
| Point 1 | 6.0V  | 1 mA   | (maximum current drawn by load) |
| Point 2 | 6.42V | 100 mA | (minimum current drawn by load) |

**Solution:**

$$\% \text{ Load Regulation} = \frac{V_{\text{NO LOAD}} - V_{\text{LOAD}}}{V_{\text{LOAD}}} \times 100$$

$$\% \text{ Load Regulation} = \frac{6.42 - 6.0}{6.0} \times 100 = 0.42/6 \times 100 = 0.07 \times 100$$

$$\% \text{ Load Regulation} = 7\%$$

### Shunt Regulator

The shunt regulator shown in *Figure 9-2b* also shunts current from the load but is designed to handle much larger currents. It duplicates the zener diode regulator. Initially,  $I_s$  is a maximum through the shunt. As  $I_L$  increases to a maximum,  $I_s$  will decrease to a minimum. It is packaged to handle much greater power dissipation, since the device power dissipation is  $V_O$  times  $I_s$ .

### Linear Series Voltage Regulators

A true feedback-type linear voltage regulator is shown in *Figure 9-2c*. All components operate in their linear mode. It is a simplified block diagram that does not have all the bells and whistles that are designed into IC regulators today, but the modern IC regulators are based on the same principles. The input voltage, a DC voltage, is separated from the load by a control element in series between  $V_{\text{IN}}$  and  $V_{\text{OUT}}$ . There is a voltage drop across the control element of  $V_{\text{REG}}$ . The series control element is controlled by an error amplifier. The error amplifier amplifies a voltage difference, called the error voltage, between a reference voltage and a sampled portion of the output voltage approximately equal to the reference voltage. Changes in the load current cause  $V_{\text{OUT}}$  to vary and the error voltage to change such that the series drop across the control element compensates for the change in  $V_{\text{OUT}}$ .

### Load Variations

The regulation works as follows: If  $I_L$  increases it will tend to reduce  $V_{\text{OUT}}$ . The reduction in  $V_{\text{OUT}}$  is fed through the sampling circuit to an input of the error amplifier. The reference voltage is on the other input. Since the reference voltage is constant, the error voltage decreases and causes the voltage across the control element to decrease. As a result,  $V_{\text{OUT}}$  increases to compensate for the initial decrease.

Likewise, if  $I_L$  decreases, it tends to increase  $V_{\text{OUT}}$ . Increasing  $V_{\text{OUT}}$  increases the error voltage, which increases the control element voltage,  $V_{\text{REG}}$  and reduces  $V_{\text{OUT}}$  to compensate for the initial increase. The stable operating point of the system is such that with  $V_{\text{IN}}$  a particular value and  $V_{\text{OUT}}$  a specified value, the error voltage is tending toward zero.

## Actual Linear Voltage Regulator Circuit

Figure 9-2d is a schematic of the interconnection of components for a linear series voltage regulator. The active devices shown are bipolar transistors, but MOS devices can (and are) used for the same design. NPN transistors and a positive output voltage are used in the design because the circuit is a bit easier to understand.

Note first that the series control element is just a NPN transistor. Note also that the reference voltage is really the zener voltage regulator that was discussed in Figure 9-2a. The only variations in the zener diode current will be those caused by variations in the input voltage,  $V_{IN}$ .  $Q_1$  and  $R_2$  form an inverting amplifier whose output drives the base of  $Q_2$ , the series control element. The input to the amplifier is the error voltage,  $V_{be}$  of  $Q_1$ . The sampled output voltage under the quiescent state is equal to a  $V_{be}$  voltage above  $V_Z$ , the reference voltage.

### Load Variations

The regulation proceeds as follows: When  $I_L$  increases and  $V_{OUT}$  tends to reduce due to the increased drop across  $Q_2$ , the  $V_{be}$  error voltage on  $Q_1$  reduces, reducing current through  $Q_1$  and  $R_2$ . The rise in the collector voltage of  $Q_1$  and base voltage of  $Q_2$  raises the emitter voltage of  $Q_2$ , increasing  $V_{OUT}$  to compensate for the initial reduction.

Likewise, for a decrease in  $I_L$ ,  $V_{OUT}$  tends to increase because of the decreased drop across  $Q_2$ . The  $V_{be}$  error voltage increases, which reduces the  $Q_1$  collector voltage and base voltage of  $Q_2$ , which reduces the emitter voltage to compensate for the initial rise in  $V_{OUT}$ .

### Line Variations

Similar regulation occurs for  $V_{IN}$  variations. If  $V_{IN}$  increases,  $V_{OUT}$  tends to increase, but the reference voltage,  $V_Z$ , changes very little. The error voltage increases because of an increase in  $V_{OUT}$ , which reduces the  $Q_1$  collector voltage and base voltage of  $Q_2$ , which reduces the emitter voltage,  $V_{OUT}$ , to compensate for the increase. Similar to load variations, a decrease in  $V_{IN}$  will be met with a compensating increase in  $V_{OUT}$  to complete the regulation.

### Higher-Current Regulators

In order to handle larger currents and, thus, more power dissipation for the regulator, external devices can be connected as shown in Figure 9-2e. Many IC regulators have the connections for the external devices provided in the design. Again, bipolar devices are used in the example, but MOS devices can be used just as well. Power devices with external heat sinks are usually required in order to satisfy the power dissipation requirements and keep the operating temperatures of the devices within specifications.

### Voltage Regulation

Return now to Figure 9-2c. The input voltage  $V_{DC}$  is the voltage out of the rectifier and filter of Figure 9-1. There is an impedance associated with the rectifier and filter. It is  $R_s$  shown in Figure 9-2c. As a result, the output voltage,  $V_{OUT}$ , is equal to:

$$\begin{aligned} V_{OUT} &= V_{DC} - I_L R_s - V_{REG} \\ &= V_{DC} - V_S - V_{REG} \\ &= V_{DC} - (V_S + V_{REG}) \end{aligned}$$

Using this information, the regulation can be explained as follows:  $V_{DC}$  is always considered constant. The regulator varies  $V_{REG}$  to keep  $V_{OUT}$  constant as  $I_L$  and  $V_S$  change. With an increase in  $I_L$  and thus  $V_S$ ,  $V_{OUT}$  would tend to decrease; however,  $V_{REG}$  is reduced to compensate and  $V_{OUT}$  remains constant.

A decrease in  $I_L$  causes a decrease in  $V_S$ , but regulation compensates by increasing  $V_{REG}$  so that  $V_{OUT}$  remains constant.  $V_{DC}$  was considered constant but if  $V_{DC}$  changes, either up or down, regulation follows to compensate by increasing or decreasing  $V_{REG}$  to keep  $V_{OUT}$  constant.

### Percent Regulation

The load regulation of a voltage regulator can be expressed as follows (where the load is some specified current value):

$$\% \text{ Load Regulation} = \frac{V_{NO \text{ LOAD}} - V_{LOAD}}{V_{LOAD}} \times 100$$

If  $V_{NO \text{ LOAD}} = 11\text{V}$  and, at a specified current,  $V_{LOAD} = 10\text{V}$  then

$$\% \text{ Load Regulation} = \frac{11 - 10}{10} \times 100$$

$$\% \text{ Load Regulation} = 10\%$$

Common percent load regulation for IC voltage regulators is from 1% to 5%.

#### Example 2. Voltage Regulation

To have 1% load regulation for the above supply where  $V_{NO \text{ LOAD}} = 11\text{V}$ , at the specified load, what does the  $V_{LOAD}$  have to be?

$$1\% = \frac{11 - V_{LOAD}}{V_{LOAD}} \times 100$$

$$0.01 = \frac{11 - V_{LOAD}}{V_{LOAD}}$$

$$V_{LOAD} (1 + 0.01) = 11$$

$$V_{LOAD} = \frac{11}{1.01} = 10.89\text{V}$$

### Power Dissipation

The power dissipation within an IC is a very important parameter because excessive temperature rise within a semiconductor junction can ruin the device. In linear series voltage regulators, the device that handles the most current is the series control element. The power dissipated in the control element is the product of the voltage across the unit times the current through the unit. The load is the current,  $I_{LOAD}$ , through the unit as shown in *Figure 9-2c and d*. The voltage across the series element is  $V_{REG}$ ; therefore, the power dissipation in the series element is:

$$P_D = V_{REG} \times I_{LOAD}$$

$V_{REG}$  is:

$$V_{REG} = V_{DC} - V_S - V_{OUT}$$

$V_S$  is usually very small compared to  $V_{OUT}$ , therefore, the series element power dissipation can be expressed as:

$$P_D = (V_{DC} - V_{OUT}) I_{LOAD}$$

**Example 3. Power Dissipation**

A voltage regulator has an input voltage of +12V and is regulating a +5V supply line. The load current is 100 mA. What is the power dissipation in the control element?

**Solution:**

$$P_D = (V_{DC} - V_{OUT})I_{LOAD}$$

$$P_D = (+12 - +5)V \times 0.1A$$


$$P_D = 7 \times 0.1 = 0.7 \text{ watts}$$

In many IC voltage regulators, especially the low-drop-out regulators, the  $V_{DC}$  is restricted to specified values so that the  $V_{REG}$  is not too great across the series element at the rated load current. This prevents exceeding the rated power dissipation of the device.

**Switching Voltage Regulators**

A regulator that has gained prominence as the requirements for load current increased is the switching voltage regulator. Standard linear regulators only have conversion efficiencies of less than 50%. Switching regulators can have efficiencies of up to 85%. This results in lower power dissipation, much smaller size components for a given power output, and operation over a wide range of voltage and current.

Figure 9-3 details a switching voltage regulator. One notes that there are similarities to a linear voltage regulator. There is the sampling of the output, the error amplifier, and the error voltage resulting from a comparison of a sample of the output voltage and the reference voltage.

 

**Figure 9-3: Switching voltage regulator (step-down)**

Here are the differences between the two regulators:

1. The error amplifier output controls a switch whose ratio of open to closed is varied.
2. Since the control element is a switch rather than a linear element, there is considerable difference in the regulator action.

**The Control Element**

Instead of a series element operating in the linear mode, the control element is a switch that is in series with a temporary energy storage element, an inductor. The switch is opened and closed at a very rapid rate, and the ratio of the time it is closed to the time it is opened is varied to accomplish the regulation. There is no linear control element operation; it is all digital, either open or closed. When the switch is closed, it charges the inductor with energy by creating a field of magnetic flux around the inductor. When the switch is opened, the magnetic flux collapses across the inductor and returns the energy to the circuit. As the energy is returned, the inductor uses  $D_1$ , shown in Figure 9-3, to complete the circuit and keep current,  $I_L$ , through the load.

## Actual Regulation

Producing more or less voltage across the load is based upon modulating the time that the control element is closed. This is accomplished by the pulse-width modulator (PWM) driven by the error amplifier. An oscillator produces the start of pulses at a constant rate, but the end of the pulse is determined by the voltage supplied by the error amplifier. The relationship of the control voltage from the error amplifier to the pulse width that turns on the switch is shown in *Figure 9-4*. Note the center of the figure has a line that represents a constant level of the control voltage B that is the nominal voltage level at the rated current output. The pulse width for this control voltage is shown as width C.

 


Figure 9-4: Switching regulator waveforms

Courtesy of Master Publishing, Inc.

When the demand for current increases, the pulse width increases because the ON time of the pulse is increased. More energy is stored in the inductor so that the increased current can be supplied and the voltage maintained. The integration of the current pulses by the output filter establishes the output voltage level. More ON time in the pulses produces a higher voltage, less ON time in the pulses produces a lower voltage. As shown in *Figure 9-4*, when minimum current is required the pulse width is narrow with a short ON time. Likewise, when maximum current is required the pulse width is wide with a long ON time.

Here is a description of the regulation in simple terms. When the load demands more current the output voltage tends to decrease. This voltage decrease is sampled and converted to an error voltage that increases the control voltage B and increases the ON time of the pulses. The increase in ON time supplies the increased current and raises the output voltage to its required value.

A load that demands less current would tend to increase the output voltage. The voltage increase is sampled and converted to an error voltage that decreases the control voltage B and decreases the ON time of the pulse. The decrease in ON time of the pulses lowers the voltage and satisfies the demand for less current.

Switching regulators operate at frequencies from 100 kHz to several million cycles/sec. Because of the range of frequencies and the switching action, there is some concern about RFI energy; and attention must be paid to the shielding of sensitive circuits.

## Step-Up and Inverting Switching Regulators

The switching regulator shown in *Figure 9-3* is a step-down regulator— $V_O$  is smaller in value than  $V_{IN}$ . *Figure 9-5* shows two other types of regulators, a step-up and an inverting regulator. The step-up regulator produces a regulated voltage  $V_O$  that is greater in value than  $V_{IN}$ , while the inverting regulator produces a  $V_O$  that is inverted in polarity from  $V_{IN}$ . A positive  $V_{IN}$  produces a negative  $V_O$ .

## Switching Regulator Design

The design of switching regulators can be accomplished in a number of ways, but they all include the inductor as the temporary energy storage element and large storage capacitors. The inductor and capacitor(s) cannot be integrated into ICs; therefore they are external to any ICs used. Any of the other components,

 


Figure 9-5: Different kinds of switching regulators

depending on the current and voltage requirements, can at least be partially integrated circuits. For example, if the current handling is within the range of 1–2 amperes, all of the error amplifier, PWM circuit, oscillator, and the control element can be one IC. With higher current requirements, external heat-sinked driver packages can be used for the control element. Resistor dividers are always used to sample the output voltage to feed back to the error amplifier.

### Transformed PWM Regulators

In a different design than that shown in *Figure 9-3*, the PWM circuit, which contains the error amplifier, oscillator, voltage reference and some protection circuits, is used as an AC source. This AC source is transformed to the desired voltage, filtered, and fed back to the error amplifier to close the regulation loop. Such a regulator is similar to the ones described because it uses PWM pulses for regulation control, but it does not utilize the inductor as a temporary storage element. An increased pulse width (larger ON time) will increase the voltage out from the transformed source; while a decreased pulse width decreases the voltage output.

### Summary of Regulators

Nothing has been said in the discussion on regulators about all of the protection techniques that can be used in the regulator circuit. For example, protection for maximum current, for short-circuits, for exceeding temperature limits, for over voltage, for under voltage, controlling the power-up or power-down sequence are all protection features that regulators may contain. Some of the features may be built into the IC regulator itself, while others may be separate ICs designed specifically to provide the protection function.

Many IC voltage regulators that handle low power requirements may have two separate individual regulators in a package, or the regulator may be one that has been designed to regulate two different voltages at the same time. As mentioned previously, many regulators have external connections provided so that higher current control elements can be driven as was shown in *Figure 9-2e*.

Switching regulators normally handle larger currents and voltage than fully-integrated regulators. Great care must be taken to keep regulators within temperature limits by the use of heat sinks and proper ventilation. The switching elements of switching regulators can be subjected to rather extreme current spikes and/or voltage spikes because of the nature of the operation; therefore, careful design is required to manage these concerns.

As mentioned previously, because switching is occurring at relatively high frequencies, and because the magnitude of currents switched are high, there is significant RF energy generated. Thus, a major concern is the circuit layouts and shielding of sensitive circuits due to the RF energy present.

## Power Supply Distribution

Figure 9-6a shows an electronic system that needs regulated voltages of +5V, +3.3V, +3V, and +1.8V. The source for the system is a filtered DC of  $V_{DC}$  obtained from one of the rectifier and filter systems of Figure 9-1. One of the simplest ways to provide the system voltages is shown in Figure 9-6b. A regulated +5V line is used as the source, and resistor dividers with bypass capacitors are used to provide the required voltage supply lines. However, such a system is not satisfactory for many systems because the load current changes cause voltage variations that are not acceptable for proper operation of the system. The supply lines must be regulated voltages held to tight tolerances, much tighter tolerances than the resistor divider and capacitor by-pass can provide. In addition, the +5V regulator must be able to handle the total current required of the system.

A very acceptable system is shown in Figure 9-6c. Here individual linear regulators designed to operate with low  $V_{REG}$  voltages for low power dissipation (called LDO regulators) are used to provide the regulated voltages in steps. Regulator A provides a +5V rail from which regulator B and C provide +3.3V and +3.0V rails, respectively. Instead of regulator D deriving its source voltage from the +5V rail, it uses the +3.0V rail to provide the +1.8V rail. This keeps the power dissipation in each regulator at a low level, and also doubles the regulation for the stepped down rails. Regulator A must be able to supply the current used by the +3.3V, the +3.0V


 
 


Figure 9-6: Power distribution system  
TEAM LRN

 

and the +1.8V rails. This is the reason regulator A' is included. It supplies all the remaining current for the main +5V rail. If it is determined that the current supplied by regulator A is small enough that regulator A' would be able to handle the load and still hold the regulation percentage, then regulator A can be eliminated. Of course, on all rails, capacitor bypass should be provided where the circuits tap off for power.

## Dual-Output Regulators

Many times circuits inside microprocessors operate at different voltage levels to save power dissipation. *Figure 9-7* shows the use of a regulator that can supply two different voltages from the same input voltage. Obviously, two separate regulator packages could be used, but with the one-chip package, variations with temperature will track better and “loss-of-power” protection for circuits will be better.

 


Figure 9-7: Dual regulator for microprocessors

## DC/DC Converters

*Figure 9-8* shows a power distribution system that requires, beside the +5V for logic circuits and other computing circuits, +12V, +24V and +3V. DC/DC converters are used for the +12V, +24V and +3V rails. The A and B converters are stepping up the voltage from +5V, while the C converter steps down the voltage. The schematic of the DC/DC converter is shown in *Figure 9-9*. The basic circuit of oscillator, pulse-width modulator, error amplifier and reference voltage are used to provide a varying ON-time pulse to the control element, in this case a power MOS. The varying pulse width pulses, transformed, rectified and filtered, provide the output voltage  $V_o$ . The ratio of the secondary turns to the primary turns on the output transformer determine if the voltage steps up or steps down. The sensing of  $V_o$  in this case is out at the load, and current sensing circuits provide protection if the current output exceeds a set limit.

 


Figure 9-8: DC/DC converters for higher or lower voltages

 



Figure 9-9: DC/DC converter schematic

### Example 4. Power Distribution

Given the system specifications for the power supply rails required, design the power distribution for the system.

| Voltage | Current | W    | Comment                                 |
|---------|---------|------|-----------------------------------------|
| +12V    | 7 A     | 84   | 2% regulation, small current variations |
| +5V     | 2 A     | 10   | 1% regulation, moderate current changes |
| +3.3V   | 0.5 A   | 1.65 | 1% regulation, large % current changes  |
| +3V     | 10 mA   | 0.03 | 2% regulation, no current variations    |

**Solution:**

 

A  $V_{DC}$  of +8V from a filtered DC output of a full-wave rectifier is chosen as the main source. The +5V and +3.3V rails, because of the 1% regulation needed with moderate current changes, linear voltage regulators are selected. The +3.3V rail, since it has current changes that are a large % of the total current of 0.5A nominal value, uses the regulated +5V as its supply rail. The +5V LDO regulator must be able to supply the 2.5A requirements of the +5V and +3.3V rails. The high-current +12V rail needs only 2% regulation with small current variations; therefore, a DC/DC converter is used to supply the +12V. As a result, another source besides the +8V is not required. The +3V rail with 2% regulation and no current variations from the low current of 10 mA is regulated with a zener diode.

### Power System Supervisors

Power system supervisors are circuits that watch over the power distribution system to detect variations in system power that may cause failure, faulty operation, or damaged circuitry. Figure 9-10 shows a supervisor that is watching over three power rails. A is a main system processor. It is the heart of a system. If it were to lose its operating point, data and memory, it would be a catastrophe. The supervisor watches the supply voltage and anticipates power failure. By doing so, it allows the processor to terminate main operations, save data and enter a proper shut-down procedure.

At B are circuits that need time to stabilize—like a clock generator in a processor. The supervisor provides a time delay before the circuits operate which allows the power to be at it stabilized value and the circuits up and running properly.

 


Figure 9-10: Power system supervisor

The supervisor for the circuits of C provides a gated chip enable. If the power supply voltage were to go below a critical value, sensitive circuits of C would not operate properly. The supervisor senses the power supply voltage, and if it goes below a critical set threshold, the supervisor disables the circuit with the chip enable line.

### Summary

The basics of power supply regulation and some techniques used for distribution have been covered. A subject that is somewhat beyond the scope of this book is called “power management.” It covers many exciting innovations such as, loadsharing, swapping boards in computers while power is ON, and many other protection techniques—for example, current limiting power switches, and watchdog timers. To equalize current in parallel power supplies, to have a technician replacing boards while the system runs, to turn ON or OFF a power supply at a current limit, and to reset a system if it doesn’t respond after a given time should be subjects that wet one’s interest to investigate further power management techniques.

### Chapter 9 Quiz

1. An AC to DC regulated power supply for electronic systems consists of:
  - a. a transformer, a rectifier and a filter.
  - b. a rectifier, a filter and a voltage or current regulator.
  - c. a transformer, a full-wave rectifier and a load.
  - d. a bridge rectifier and a voltage or current regulator.
2. Common solid-state rectifiers for AC to DC power supplies are:
  - a. single vacuum tube rectifiers.
  - b. bridge rectifiers.
  - c. full-wave rectifiers.
  - d. all of above.
  - e. b and c above.
  - f. a above.
3. A zener diode is a semiconductor diode that:
  - a. is forward biased in normal operation.
  - b. can handle tens of amperes of current.
  - c. doesn’t have to be concerned about power dissipation.
  - d. is designed to maintain a constant voltage across it as the current through it varies.

4. In linear series voltage regulators:
  - a. all components operate within their linear range.
  - b. the series control element operates in a switching mode.
  - c. the error voltage is quite large at the stable operating point.
  - d. the reference voltage source handles large currents.
5. The efficiency of linear series voltage regulators is:
  - a. less than 50%.
  - b. less than 75%.
  - c. less than 35%
  - d. less than 10%.
6. In a quiescent linear series voltage regulator using a zener diode reference voltage:
  - a. the sampled output voltage is equal to the zener reference voltage.
  - b. with  $V_{IN}$  constant, there will be large changes in the zener reference voltage.
  - c. the sampled output voltage is a  $V_{be}$  voltage above the zener reference voltage.
  - d. there is no limit on the current through the series control element.
7. A linear series voltage regulator can regulate output voltage:
  - a. when load current changes occur.
  - b. when input line variations occur.
  - c. when the input voltage source is removed.
  - d. when there is a short-circuit load.
  - e. a and b only.
  - f. none of the above.
8. To obtain higher current regulation from a linear series voltage regulator:
  - a. more zener diodes are added.
  - b. another higher-current transistor is added in parallel with the series control element.
  - c. more heat sinks are added to the series control element.
  - d. larger resistors are added to the sampled voltage resistor chain.
9. The component(s) in a linear series voltage regulator that must be protected from excessive temperature rise is(are):
  - a. the zener diode.
  - b. the error amplifier transistor(s).
  - c. the series control element transistor(s).
  - d. the sampled output voltage resistor string.
10. A switching voltage regulator is used instead of a linear series voltage regulator because:
  - a. it has efficiencies up to 85%.
  - b. it has lower power dissipation.
  - c. it has smaller sized components for the output power required.
  - d. all of the above.
  - e. a only above.
  - f. b and c only above.
11. What components, along with a switch, provide the basic circuit for a switching voltage regulator?
  - a. an inductor, diode and capacitor.
  - b. two inductors.
  - c. an inductor and a capacitor.
  - d. two capacitors.

12. The control element in a switching voltage regulator is:
  - a. an inductor.
  - b. a capacitor.
  - c. a switch.
  - d. a resistor.
13. An inverting switching voltage regulator:
  - a. uses inverting logic circuits for its control.
  - b. produces an output voltage that is inverted in polarity to that of the input voltage.
  - c. uses a bridge rectifier in its control circuit.
  - d. operates at 10 Hz.
14. Power distribution systems can:
  - a. use linear series voltage regulators operating from a regulated rail to provide the desired output voltages.
  - b. use switching voltage regulators operating from a regulated rail to provide the desired output voltages.
  - c. use a combination of linear series and switching regulators to provide the desired output voltages.
  - d. use DC to DC converters operating from a regulated rail to provide step-up and/or step-down regulated output voltages.
  - e. all of the above.
  - f. a only.
  - g. a and c only.
15. Power system supervisors:
  - a. contain circuits that watch over the power distribution system so variations do not occur that cause system failures.
  - b. contain circuits that can detect low voltages, provide time delays, and provide signals that enable or disable system circuits.
  - c. shuts down everything in the system without notice.
  - d. all of the above.
  - e. a and b only.
  - f. a only.

Answers: 1.b, 2.e, 3.d, 4.a, 5.a, 6.c, 7.e, 8.b, 9.c, 10.d, 11.a, 12.c, 13.b, 14.e, 15.e.

# A Microcontroller Application

## Introduction

The thrust of this chapter is to provide the reader with the opportunity to actually build and implement an application using a microcontroller. The microcontroller that will be used is the same one that was chosen to describe assembly-language programming in *Chapter 7*. This should provide continuity from what was learned in *Chapter 7* to applying it to a working application. The microcontroller used is the MSP430F1232. The application is explained, and then the reader is given the opportunity to gather the parts, interconnect them, and with the help of a development kit for the microcontroller used, to program the microcontroller with the program provided to complete the application.

## Application Block Diagram

The block diagram of the application is shown in *Figure 10-1*. It consists of a PT-100 resistive sensor whose resistance change with temperature is quite linear. The signal from the sensor is conditioned (amplified) by the TLV2451 operational amplifier. The output of the op amp is fed to the TLV1549, a 10-bit ADC, to convert the analog voltage into a digital code. The digital code representing the temperature sensed by the PT-100 is inputted to the MSP430F1232, the microcontroller. The microcontroller decodes the temperature code, and converts it to signals that drive the display to indicate the temperature in either °F and °C. In addition, the microcontroller uses its clock and counters to produce the timing pulses that produce the time, date, and year outputs that are then decoded for display. In sequence, the time, the date, the year, and the

 


Figure 10-1: Block diagram

temperature in °F and then °C is displayed. The display is four digits with each digit having seven segments. Each segment is an LED diode that has an anode and a cathode and must be connected between  $V_{CC}$  and ground to pass current through the forward-biased diode. The microcontroller connects the cathode of the diodes to ground and the grounding is timed by the microcontroller to energize the correct digit as the selected anodes of the segments, a through g, are timed and energized by the microcontroller to produce the correct number or letter. Also included in the display are small LEDs that represent colons, decimal points, and AM and PM indicators. Their cathodes must be connected to ground and their anodes energized to produce their outputs at the correct time.

### The Auto-Toggling State Diagram

A diagram that shows the sequence of what is to be displayed is shown in *Figure 10-2*. It is called a state diagram. The sequence begins at **Clock** where the digits for the hour(s) and minute(s) are displayed with a colon between them. If the time is after 12:00 noon, the PM LED is energized. After two seconds, the **Date** is displayed. The month digits and the day digits are energized with a period between them. Two seconds pass and the **Year** digits are energized. Two seconds pass and the temperature in °F, **Temp °F**, is displayed, and two seconds later the temperature in °C, **Temp °C**, is displayed. If the temperature is negative, the g-segment LED is energized to produce a minus sign to indicate the negative value. Two seconds later the display is back at the start, **Clock**, displaying the time.

### The Manual-Toggling State Diagram

In the block diagram of *Figure 10-1* there are three push-button switches. One is a black reset button; the other two—one red and the other black—are used in *Figure 10-3* while manually toggling through the same states as in *Figure 10-2*. The diagram shown in *Figure 10-3* is called the manual-toggling state diagram. The red button is used to move manually through the states shown in *Figure 10-2*. At each state, the black button is used to manually move to a quantity displayed in different modes in the particular state. Pushing the red button then increments the quantity. As a result, using these two buttons, the correct time, date, and year are set and the temperature checked for calibration at known points—freezing water and boiling water. They are also used to switch between the manual toggling of the states and the sequencing or auto-toggling of the states.

At startup, the system will be in the **Clock** state with the time 12:00 midnight. This is the start of the

 


Figure 10-2: Auto toggling through states

 


Figure 10-3: Manual toggling through states

manual-toggling. Pressing the black button will put the system in the “set hour” mode. Pressing the red button will increase the hour display from midnight to one o’clock. Further pressing advances the hour digits from one o’clock to 12 o’clock, and then the numbers start over for the PM hours. After the hour digits are set, pressing the black button puts the system in the “set minute” mode, and pressing the red button advances the minute digits from 1 to 59 and back to 1. Setting the minutes digits completes manually setting the modes in the clock state. Pressing the black button returns the system to the **Clock** state.

Pressing the red button will move the system to the **Date** state. Pressing the black button puts the system in the “set month” mode. Pressing the red button increases the month digits from 1 to 12 and back to 1. When the month digits are correct, pressing the black button puts the system in the “set day” mode. Here pressing the red button increases the day digits from 1 to 31 and back to 1 again until the day digits are set correctly. Now pressing the black button returns the system to the **Date** state.

Pressing the red button will move the system to the **Year** state. Pressing the black button puts the system in the “set year” mode, and pressing the red button advances the year. It starts at the initial year of 2000. After setting the year, pressing the black button returns the system to the **Year** state.

Pressing the red button moves the system to the **Temp** state, either **Temp °F** or **Temp °C**, and pressing the black button toggles the display from °F to °C. Temperature can be checked at the points of boiling water (212°F) and at freezing water (32°F). Pressing the red button returns the system to the **Clock** state. Thus, all the modes in each state that are to be manually set have been stepped through.

### Switching Modes

Holding the red button for two seconds will put the system into auto-toggling. Manual toggling can be entered from any of the states that the system is in. If in the auto toggling sequence, which holds each state for two seconds before advancing to the next state, and in the **Date** state, pressing the red button will put the system in the **Year** state and manual setting mode so that the year can be set. If in the **Temp** state, pressing the red button will put the system in the **Clock** state and manual setting mode for the clock. Pressing the red button and holding the button for two seconds again puts the system into auto-toggling.

### The Sleep Mode

There is a sleep mode used to conserve power and extend the life of the batteries. This is one of the significant advantages of using the MSP430 microcontroller. It operates at very low power and can be put into a sleep mode to significantly reduce the average power consumed. If the system is left on continuously, the battery drain is 25–30 mA, and the batteries would last only 2–3 days. Being able to put the system into a sleep mode and waking it to update the one second count, or waking it to sequence through time, date, year and temperatures reduces the current drain. This procedure can extend the battery life to around a year. *The sleep mode is entered if none of the buttons have been pressed for 15 seconds.*

The system is awakened by pressing the red or black button, or by a timer signal that is initiated every 20 minutes, on the 20-minute, 40-minute and 60-minute mark of the hour. The system goes through one cycle of the auto-toggle sequence and then goes back to sleep. When the system awakens, it returns to the state that it was in before it went to sleep. If it was sequencing, then it returns to sequencing; if it was in manual, then it returns to manual. When in the sleep mode, the 32,786 Hz crystal oscillator and the Timer\_A used as a counter are the only circuits operating in the microcontroller.

In summary, starting with the system in the sleep mode, assuming it was in the auto-toggling mode when it went to sleep, pressing the red or black button awakens the system in the auto-toggling mode. Pressing the red button will put the system into manual toggling. Pressing the black button will put the system in a manual set mode; if in the **Clock** state, then the black button will move the system to be able to set the hour



and minutes with the red button. Correspondingly for **Date** and **Year** states, setting month and day, and the year, respectively. Pressing the red button in any of these modes and holding it for two seconds puts the system in the auto-toggling mode. Pressing no buttons for 15 seconds puts the system in the sleep mode.

In the sleep mode, an internal timer is keeping track of time from the top of the hour. At the 20-minute after the hour point, or at the 40-minute point, or at the 60-minute point, a signal awakens the system, it cycles through one cycle of the auto-toggling mode, and returns to the sleep mode. The system will ignore the 20, 40, or 60-minute mark signal if the system is already awake.

## System Schematic

A schematic is a diagram that shows all the package pins of the devices that are used in the system and all the electrical connections between the devices, resistors, capacitors, transistors, diodes and display elements that make up the system. It is shown in *Figure 10-4*. It represents the components with the respective accepted symbols, and all of the respective package connections are included, even the open or unconnected pins. It uses the block diagram of *Figure 10-1* as a base, but includes all the detail electrical connections including the components and connections needed to supply power to the system.

## The Display

### The Seven Segments

The system requires that four digits be displayed. The display shown in *Figure 10-1*, *Figure 10-4* and *Figure 10-5* is made up of digits that have seven segments and some additional small LEDs in between.

 


Figure 10-4: System schematic  
TEAM LRN  
177

The unit, which has four digits packaged together, has 24 pins, and *Figure 10-5* shows the 4-digit display connections. As shown in *Figure 10-6a*, each digit is made up of seven LED segments that each have an anode and a cathode. The segments are identified with the letter a through g, and will be energized when a positive voltage is applied to the anode and the cathode is grounded. The anodes of the segments are connected in parallel across the digits (a to a, b to b, and so on), while the cathodes for each digit are all tied together and identified with CDig1, CDig2, CDig3 and CDig4 for the four digit connections. This allows only one digit to be excited at a time.

As shown in *Figure 10-6b*, codes determine which segments are energized with a positive voltage. For example, the code for digit 1 segments a through g is 1101101 which means that segments a, b, d, e and g are energized when CDig1 is grounded. This displays 2 as digit 1. Since all the segments of all the digits are energized in parallel, the only digit that will be displayed is the one that has its cathode line grounded. The microcontroller controls the time that the cathodes of the desired digit to be displayed are grounded. Just to give a small example of the circuit connections to the display, *Figure 10-7* details a portion of the connections from the microcontroller to CDig1 and CDig2 to ground the cathodes for digit 1 and digit 2 and excite the anodes of segments a, b, c, d. Similar connections are made to CDig3, CDig4 and the segments e, f and g as shown in *Figure 10-4*.

Referring back to *Figure 10-6b*, the code for digit 2 changes to 1011011, which means that segments a, c, d, f and g are energized and digit 2 displays a 5 when its cathodes are grounded. Correspondingly,


 


Figure 10-5: Connections to 7-segment display

 

a. Diode interconnections

b. Segment codes

 


Figure 10-6: 7-segment LED detail

digit 3 displays a 1 when the code 0110000 energizes the segments; and digit 4 displays a 4 when the code 0110011 energizes the segments. The microcontroller grounds the cathode connection and excites the anodes at the proper time to display the respective digit.

### The Additional Small LEDs

There are several other small LEDs included in the display. When the system is in the **Clock** state, the hour digits are separated from the minutes digits by a colon (Figure 10-2). The colon is displayed by energizing the anodes of the LEDs identi-

fied as the upper colon and lower colon and grounding their cathodes. The cathodes are tied together at the connection “cathode colon.” In similar fashion, when the system is in the **Date** state or the **Temp** state, a decimal point separates the month and day digits, or identifies tenths of a degree for temperature. The decimal point is displayed by energizing the anode of the lower colon, depending on the position required, at the same time grounding the cathodes through cathode colon. One other small LED that is used is the PM LED. The PM LED is energized when the hours exceed 12 noon, to indicate the hours displayed are in the PM. A positive voltage is placed on the PM anode while the cathodes of both the AM and PM LEDs, which are tied together, are grounded by the microcontroller. As noted previously, the segment g LED is energized when the temperature values are negative. The cathode, CDig1, is grounded by the microcontroller. Pins 4(Adp1), 9(Adp2), 12(Aalrm), 13(Cfma), 14(AFM), 16(Cdp2), 21(Ddp1) and 23(AAM) are not used.

### The Microcontroller

Return to the system schematic in Figure 10-4. The microcontroller used is the MSP430F1232 out of the MSP430 family of microcontrollers, the same family used for Chapter 7 to explain assembly-language programming. The MSP430F1232 has three I/Os, 8 kB + 256B of Flash memory, 256 bytes of SRAM, a watchdog timer, a Timer\_A, and the brownout feature. It is packaged in a 28-pin package. It uses the same assembly-language instruction set used in Chapter 7, which is included in the Appendix.

### The I/O Ports

The port 3 I/O pins P3.0, P3.1, P3.2, P3.3, P3.4, P3.5, P3.6, are configured as outputs and drive the anodes of display segments a through g through 33  $\Omega$  resistors between the output pin and the pin to the anode. The P3.0, P3.1, P3.2 and P3.3 connections were shown in Figure 10-7. Port 1 I/O pins P1.0, P1.1 and P1.2 are also configured as outputs to drive the anodes, through 33  $\Omega$  resistors, of display segments upper colon, lower colon and PM, respectively. The port 1 I/O pins P1.6 and P1.7 are configured as inputs and receive the signals from the red and black push buttons, respectively. A 470 k $\Omega$  resistor from V<sub>CC</sub> connected to P1.6

 


Figure 10-7: LED segment driver

or P1.7 is pulled to ground when the black or red button, respectively, is pushed. The ground signal on P1.6 or P1.7 initiates microcontroller action as previously described in the discussion on the state diagrams. In addition, a black push button grounds pin 7, RST/NMI, through a 68 k $\Omega$  resistor to  $V_{CC}$  to reset the system. A detail of the push button connections is shown in Figure 10-8.

 


Figure 10-8: Push buttons

The port 2 I/O pins P2.0, P2.1, P2.2, P2.3, P2.4, P2.5 are configured as inputs and ground the cathodes CDig1, CDig2, CDig3, CDig4, Ccolon, and CAM/PM, respectively. The remaining port 1 and port 3 I/O pins are configured as follows:

| Pin  | Configured as: | Connected to:        |
|------|----------------|----------------------|
| P1.3 | output         | CS of TLV1549        |
| P1.4 | output         | Analog $V_{CC}$      |
| P1.5 | output         | I/O CLOCK of TLV1549 |
| P3.7 | input          | DATA OUT of TLV1549  |

P1.3 outputs the low-level chip select to the TLV1549 to initiate the analog-to-digital conversion. P1.5 outputs a clock to the TLV1549. P3.7 inputs to the microcontroller the digital code data output from the TLV1549. P1.4 is configured as an output that provides the power to the analog portion of the system—the sensor, op amp and the ADC. When the system is awake,  $V_{CC}$  for these circuits is provided on P1.4 by the microcontroller; when the system is asleep, there is no power provided on P1.4. Thus, with this power control, as well as disconnecting power from circuits inside the microcontroller, the system consumes very little power in the sleep mode.

Here are the remaining connections to the microcontroller. Pin 1 is a TEST pin, pin 2 connects to the main  $V_{CC}$ , pin 4 is  $V_{SS}$  or main system GND, and pin 5 and pin 6 are the connections to the watch crystal (32,768 kHz) which provides the precision clocks generated in the microcontroller for the system.

The Analog Circuitry

The Sensor and Op Amp

The analog portion of the system schematic, as mentioned previously, consists of the PT-100 sensor, the TLV2451 op amp, the TLV1549 ADC. There is another separate analog circuit, U4, a low-voltage drop voltage regulator used for power control that will be discussed later. Pin 2 (inverting input) of the op amp has a 1 k $\Omega$  resistor to ground and a 100 k $\Omega$  feedback resistor from the output pin 6 to set the op amp gain. The noninverting input, pin 3, is connected to the intersection of the PT-100 sensor and a 15 k $\Omega$  resistor that connects to the power line Analog  $V_{CC}$ . The other end of the PT-100 sensor is connected to ground. The op amp power is supplied through pin 7, which is connected to Analog  $V_{CC}$ , and completed through pin 4 that is connected to ground.

ADC

The output of the op amp (pin 6) is connected to pin 2 (the analog input) of the TLV1549 ADC. The output digital data from the ADC is coupled to the microcontroller from output pin 6. The data is shifted out on

the data line using the clock on pin 7, I/O Clock from Port 1 pin P1.5 of the microcontroller. The conversion process begins when the chip select input (pin 5) coupled from the microcontroller Port 1 pin P1.3 is brought low. Pin 1, REF+, and pin 8,  $V_{CC}$ , are connected to Analog  $V_{CC}$ . Pin 3, REF-, and pin 4, GND, are connected to GND.

### Power and Power Control

The schematic of *Figure 10-4* shows several variations for supplying the main system  $V_{CC}$ . The first of these is when the complete system is assembled on a printed-circuit board (PCB). The  $V_{CC}$  of +3.3V is supplied from pin 5 of a TPS71533 low-voltage drop (LDO) voltage regulator; the U4 analog circuit mentioned previously. The input to the LDO on pin 4 is +4.5V supplied by three AAA batteries in series. The LDO keeps the +3.3V output constant as the batteries lose voltage, and thus, extends the battery life of the system. Pin 2 of the LDO is connected to GND, and pin 4 and pin 5 are bypassed by capacitors C1 (0.1  $\mu$ F) and C2 (0.47  $\mu$ F). There is a series jumper to disconnect the +4.5V battery source.

In the second variation, the system is in breadboard form and has the main system  $V_{CC}$  of +3V supplied by two AA batteries in series. There is no LDO. There is a series jumper to disconnect the battery source. The system stands alone operating from +3V battery power.

In the third variation, the main system  $V_{CC}$  is supplied from a PC (personal computer) through the JTAG connector on the evaluation board. There are no batteries and no voltage regulator. The system operates from the PC's  $V_{CC}$ . This is the usual connection used when programming the system.

### Brown Out

The MSP430F1232 microcontroller has a system power protection circuit built in. This feature means that if the  $V_{CC}$  supply goes below a voltage level between 1.1V and 1.7V the system is reset. The actual trigger voltage varies with the device. When the  $V_{CC}$  voltage is restored above the trigger level, it will start at ground zero (time of 12:00) and run properly. Without brown out, if  $V_{CC}$  falls below the trigger level, the system would not operate properly and would be unpredictable when  $V_{CC}$  is restored. This feature requires the MSP430F1232, which has no comparator. If a comparator is required, the MSP430F123 is used without the brownout feature.

### JTAG

There is a connector on the schematic that is on the evaluation board that sockets the microcontroller. It is a 14-pin connector called out as JTAG. It is used to connect the evaluation board to the PC development system, and supply  $V_{CC}$  to the breadboard. The development system is used to load the program software into the microcontroller and for debugging the system. Here are the connections from the JTAG connector to the microcontroller:

| JTAG Pin       | Microcontroller Pin |
|----------------|---------------------|
| 1 (TDO)        | 28 – TDO            |
| 2 ( $V_{CC}$ ) | 2 – $V_{CC}$        |
| 3 (TDI)        | 27 – TDI            |
| 4              | NC                  |
| 5 (TMS)        | 26 – TMS            |
| 6              | NC                  |
| 7 (TCK)        | 25 – TCK            |
| 8 (TEST)       | 1 – TEST            |
| 9 (GND)        | GND – $V_{SS}$      |
| 10             | NC                  |
| 11 (RST)       | 7 – RST/NMI         |
| 12 – 14        | NC                  |

## Summary of Schematic

The sensor, PT-100, changes resistance linearly with temperature as discussed in *Chapter 3, Sensors*. At the junction of the sensor to ground and a resistor to  $V_{CC}$ , a voltage that varies with temperature is coupled to the noninverting input of the op amp. A positive input voltage produces a positive-going output voltage. The gain of the op amp, as discussed in *Chapter 4*, is set by the ratio of  $R_f/R_i$  ( $R_{14}/R_{15}$ ), the ratio of the feedback resistor from the output to the inverting input, and the resistor from the inverting input to ground. The op amp output voltage is fed to the input of the ADC. The ADC, a switched capacitor, successive approximation ADC, produces a 10-bit digital code from its analog input. The 10-bit code is shifted out of the ADC into a data register in the microcontroller by a clock signal to the ADC from the microcontroller. The switched capacitor, successive approximation (SAR) ADC was discussed in *Chapter 5*. The shifting out of the data from the ADC to the microcontroller was discussed as one of the subprograms of *Chapter 7*.

The clocks are produced from a watch crystal oscillator with a frequency of 32,786 Hz. Counters in the microcontroller count the crystal oscillator clocks and produce a one-second pulse that then is counted to produce the time in minutes and hours, days, months and years. The counter initial conditions are set manually to adjust the system to present-day time. The program is installed in the microcontroller using a development system, and after all interconnections on the schematic are made, the system should operate properly.

## System Development

There are three stages of system development—two breadboard stages and a final PCB stage.

1. The first stage is shown in *Figure 10-9*. The MSP430F1232 microcontroller is connected in a socket on the evaluation board (Texas Instruments MSP-TS430DW28) that is connected through the JTAG connector by cable to the Flash Emulator Tool. The Flash Emulator Tool is connected by cable to the parallel 25-pin input connector on a PC. This configuration, which uses the development system software in the PC to load the program software into the microcontroller and to debug the system, has the circuit interconnected in breadboard form. As shown in *Figure 10-9*, the breadboard consists of an analog board on one side of the evaluation board and a display board on the other side. Recall that the system is powered from the PC.
2. The second stage is shown in *Figure 10-10*. In this configuration, the breadboard stands alone powered by two AA batteries. The microcontroller is still plugged into the evaluation board, but the JTAG connector is disconnected. There is no longer any need for the PC development system; the system runs stand-alone.
3. The third stage is shown in *Figure 10-11*. This stage has the system assembled completely on a PCB. The parts used are now parts that are capable of being mounted on a PCB. There is an op amp in a smaller package, there is

 


Figure 10-9: Breadboard powered by PC

the LDO voltage regulator, and there is a MSP430F1232 in a smaller package. The majority of the parts are assembled to the board using surface-mount technology. Power is supplied by three AAA batteries in a holder on the back of the PCB. It is a self-contained system. Such a system could be mounted in a separate case, or included as part of other equipment.


## The Breadboard Circuit

The breadboard circuit shown in *Figure 10-9* and *Figure 10-10* is built using readily available parts. The main components of the breadboard are the MSP430 evaluation board, which contains a socket for the MSP430 microcontroller, and two IC breadboard sockets. One IC breadboard socket, called the display board, contains the 7-segment display, the red and black toggling and mode push button switches, and the associated resistors and connecting wires. The other IC breadboard socket, called the analog board, contains the analog devices and associated circuitry, the op amp, the ADC, the black RESET push button, and connecting wires. The evaluation board is in the development system from Texas Instruments (MSP-FET430P120), which contains the following:


1. The evaluation board (MSP-TS430DW28).
2. The microcontroller (MSP430F1232).
3. A MSP430 Flash Emulation Tool (MSP-FETP430IF).
4. Cable from JTAG to Flash Emulation Tool.
5. Cable from Flash Emulation Tool to parallel LPT (printer port) on PC.
6. Two 14-pin cable connectors for wiring to J1 and J2 on evaluation board.
7. PC software and instructions.

Here are the main sources for the parts:

- a. Samples of the op amp and the ADC can be obtained online from Texas Instruments.
- b. The 4-digit LED display and the 32-kHz crystal can be ordered online from Digi-Key.
- c. The PT-100 sensor can be obtained online from Omega Engineering.
- d. The IC breadboard sockets, the jumper wire kit, the push-button switches, and the resistors are all available from RadioShack or other electronic parts distributors. The resistors and capacitors can be ordered from Digi-Key Corporation at the same time as the display and the crystal if one wants to order online.

 

**Figure 10-10: Stand-alone breadboard powered by +3V battery (two AA cells)**

 

**Figure 10-11: PCB powered by three AAA batteries (+4.5V)**



It is assumed that the reader will have available:

1. Long-nose pliers
2. Diagonal cutter
3. Wire stripper
4. Small soldering iron
5. Solder

If these are not available, they are easily purchased at RadioShack or any other electronic parts distributor.

### Parts List for the Breadboard

Here are the parts required of the breadboard:

| <u>Part</u>                                          | <u>Part No.</u> | <u>Quantity</u> |
|------------------------------------------------------|-----------------|-----------------|
| MSP430 Development System                            | MSP-FET430P120  | 1               |
| Sensor (PT100 – RD)                                  | 1PT100KN815     | 1               |
| Op Amp ( $V_{CC} = +3V$ )                            | TLV2451CP       | 1               |
| ADC (Analog-to-Digital Converter)                    | TLV1549CP       | 1               |
| 4-Digit 7-segment LED Display                        | LN543RKN8       | 1               |
| 32 kHz Watch Crystal                                 | X802 – ND       | 1               |
| IC Breadboard Socket                                 | RS 276-175      | 2               |
| Pair (Red and Black) SPST Momentary Push-button Sw.  | RS 275-1556     | 2               |
| Jumper Wire Kit                                      | RS 276-173      | 1               |
| Battery Clip for two AA Batteries                    | RS 270-0414     | 1               |
| DIP Shunt Shorting Jumpers for AA battery connection | RS 276-1512     | 1               |
| AA Battery (1.5V)                                    | RS 23-872       | 2               |
| R1 – R10 33 $\Omega$ 1/2W 5% resistor                | RS 271-1104     | 10              |
| R11, R12 470 k $\Omega$ 1/2W 5% resistor             | RS 271-1133     | 2               |
| R13A 4.7 k $\Omega$ 1/4W 5% resistor                 | RS 271-1330     | 1               |
| R13B 10 k $\Omega$ 1/4W 5% resistor                  | RS 271-1335     | 1               |
| R14 100 k $\Omega$ 1/4W 5% resistor                  | RS 271-1347     | 1               |
| R15 1 k $\Omega$ 1/4W 5% resistor                    | RS 271-1321     | 1               |
| R16A 47 k $\Omega$ 1/2W 5% resistor                  | RS 271-1130     | 1               |
| R16B 22 k $\Omega$ 1/2W 5% resistor                  | RS 271-1128     | 1               |
| C3 0.1 $\mu F$ 50V capacitor                         | RS 272-135      | 1               |

\*The 15 k $\Omega$  R13 is made up of a 4.7 k $\Omega$  and a 10 k $\Omega$ , standard values readily available.

\*\*The 68 k $\Omega$  R16 is made up of a 47 k $\Omega$  and a 22 k $\Omega$ , standard values readily available.

### Obtaining the Parts

The details that follow were current at the time of publication. Obviously, Web sites change, and so does the information presented and the procedures to be followed. However, as the reader becomes familiar with the Web sites and by checking Readme.txt files, they will be able to arrive at the desired outcome even though the Web site has changed.



**MSP430 Development System**—It may be purchased from Texas Instruments (\$99.00) by calling the American Products Information Center at 972-644-5580. The board will be shipped directly to a home or business.

**Op Amp and ADC**—Samples of the Texas Instruments TLV2451CP and TLV1549CP can be obtained online via TI's Web site: <http://www.ti.com>. If this is the first time visiting the TI Web site, nonmembers of *my.ti* may have to register by using an e-mail address and choosing a password. On the Web site page there is a part number search window. Enter the part number—TLV2451CP—and click on “Go.” A window displaying the results of the search shows a description of the TLV2451CP. Click on TLV2451 and a listing of TLV2451 products appears. On the left side of the product list there is a link that reads “samples.” Click on it and a sample list of the TLV2451 products is displayed. Select the TLV2451CP and follow the prompts to register and fill out the shipping information. Repeat for the TLV1549CP. The parts should be received in a few days. When the TLV2451 or TLV1549CP product list is displayed, if a complete data sheet is required, clicking on the “Data Sheet” box will print out the data sheet if an Acrobat Reader is available on your computer.

**Watch Crystal and Display**—The watch crystal and the 4-digit LED display can be purchased online from Digi-Key at the Web site <http://www.digikey.com>. Digi-Key Corporation is an online distributor of electronic parts. Enter the part number (LN543RKN8 for the display; X802-ND for the crystal) in the part number search window and click on “Go.” Enter the quantity on the “Add to Order” line, then follow the prompts to supply shipping and payment information. The watch crystal is about \$0.30 and the display is about \$10.00, plus shipping.

**Sensor**—The sensor, PT100-RD, is purchased online from Omega Engineering at its Web site <http://www.omega.com>. Omega fulfills all their small purchases online. Enter the part number, 1PT100KN815, in the part number search window and click “Go.” A part description window appears. Enter quantity and click “Add to Cart.” Follow the prompts to supply shipping and payment information. The sensor should be under \$20.00.

**Remaining Parts**—All the remaining parts are available from RadioShack or other electronic parts distributors. The part numbers given are RadioShack part numbers. Note that for R13 and R16 two resistors are placed in series to make up the total resistance because the values for the two-resistor combination are more readily available. The push-button switches come two in a pack—one black and one red. Two of the IC breadboard sockets are required for the system breadboard. As mentioned previously, resistors, capacitor(s) and push button switches may be obtained online from Digi-Key. RadioShack was chosen as the source because of the nationwide outlets, and immediate access to the parts.

### ***Breadboard Construction—Powered by the PC***

Cables for J1 and J2, the connections on the evaluation module, are constructed first. There are two connectors supplied in the development system for each of the J1 and J2 connections. One is a male, and the other a female. The female is attached to the PCB; the male is used as a jumper cable connector. Use the jumper wire kit to construct the cables. Use the solid-color red, green, yellow and orange wires and solder them to the male connectors provided as shown in *Figure 10-12*. The wire colors refer to the ones that are in the RadioShack kit. The reader may choose to use another wire supply with different colors. Use the text as a guide to assign the wire colors. If the RadioShack kit is used, the wires marked with an asterisk in *Figure 10-12* need to be extended by soldering a like color wire to them and insulating the solder joint with electrical tape. Solder the female connectors, also provided, to the evaluation module PCB in the J1 and J2 positions shown on the PCB. There are Rd/Blk and Or/Blk wires required. Take three red wires and two orange wires and mark across them with a marker to make the dual-colored wires. Make sure all connections are physically and electrically sound. When the cables are completed, plug the male connector into the female to connect the cables to the evaluation module.

 


Figure 10-12: Cables for J1 and J2

## Display Board

The display board is constructed using one of the IC breadboard sockets (RS 276-175). Plug the 4-digit LED display (LN543RKN8) into the breadboard socket in the position shown in *Figure 10-13*. The pins 13 through 24 plug into the bottom horizontal row of the upper portion of the IC breadboard, and the pins 1 through 12 plug into the second horizontal row of the lower portion of the breadboard. Pin 1 of the display is in vertical row 1 of the lower portion; pin 24 of the display is in vertical row 1 of the upper portion. The upper and lower portions of the breadboard are configured the same. There are 23 vertical rows with five connection points in each row. All five connection points, A, B, C, D, and E, in the upper portion vertical rows are connected together; all the connection points, F, G, H, I, and J, in the lower portion vertical rows are connected together. Each vertical row is electrically isolated from any of the other vertical rows. At the top of the upper portion is a horizontal row, X, of 20 connections all connected together. This row of connections will be used for V<sub>CC</sub>. A similar horizontal row, Y, of 20 connections is at the bottom of the lower portion. This row of connections will be used for the ground (GND) of the circuit.

Note that in the block diagram of *Figure 10-1* and the schematic of *Figure 10-4* there are 10 33 Ω resistors that are connected from the microcontroller drive pin to the anode of the LED segments of the four digits of the display. Connect these resistors by pushing the wires of the resistors into the connection points as shown in *Figure 10-13*. For example, one end of R1 is connected to pin 15 of the display (vertical row 10 of upper portion), and the other end to vertical row 19. A green wire from pin 11 of the microcontroller connector J1, to be connected later, will connect to vertical row 19 to drive anode a. Plugging in R2 through R10 in a similar fashion will provide the drive for anodes b through g, PM, lower and upper colon.

To connect the push buttons, solder a short piece of wire to each push button terminal. Insert one terminal wire of the black push button into vertical row 20 of the lower portion of the socket and the other terminal wire into Y, the GND row of connections. Insert one end of R12 (470 kΩ) into the same vertical row 20 and the other end into the top row X of V<sub>CC</sub> connections. Refer to *Figure 10-13* to check the connections. Later a red wire from pin 27 of J2, TD1, will also be connected to vertical row 20.

 


Figure 10-13: Display board

A similar connection pattern is followed for the red push button; one terminal wire is connected to vertical row 23 of the lower portion and the other terminal wire to GND. One end of R11 (470 kΩ) is inserted into vertical row 23 and the other end into the  $V_{CC}$  connections. Later a red wire from pin 28 of J2, TD0, will also be connected to vertical row 23. The grounding of TD0 and TD1 by the push buttons sends signals to the microcontroller to toggle, change modes, or to set a parameter.

## The Analog Board

The analog board is constructed on the second IC breadboard socket as shown in *Figure 10-14*. Both the TLV2451CP op amp and the TLV1549CP ADC are packaged in 8-pin DIP packages. They are both plugged into horizontal connection rows, as shown in *Figure 10-14*, that span the upper and lower portions of the breadboard. For the TLV2451, vertical rows 1 through 4 of the lower portion are used for pin connections 1, 2, 3 and 4, respectively, and vertical rows 1 through 4 of the upper portion are used for pin connections 8, 7, 6, and 5, respectively. Pin 7 is connected to the top row, X, of connections, which are now identified as “Analog  $V_{CC}$ ” because this  $V_{CC}$  is being switched on and off by the microcontroller.

The noninverting input, IN+, pin 3, (vertical row 3) has one end of the PT-100 sensor connected to it, as well as one end of R13B. The other end of R13B is connected in series with R13A to Analog  $V_{CC}$ . To make sure that the connections from the PT-100 sensor are good electrically, solder short pieces of wire to the very fine wire of the sensor before inserting the connections into the breadboard. It is even best to put a blob of silicone or plastic sealer (one that solidifies) around the wires to hold them in place, otherwise the

 


Figure 10-14: Analog breadboard

wires will break and ruin the PT100. One connection of the sensor is to vertical row 3 of the lower portion, and the other connection is to Y, the GND row of connections at the bottom of the breadboard.

Resistor R14 (100 k $\Omega$ ) is connected from the output, pin 6, vertical row 3 of the upper portion, back to the inverting input, IN-, pin 2, vertical row 2 of the lower portion. Vertical row 2 also has one end of R15 (1 k $\Omega$ ) connecting from it to the GND line of connections. The ratio of the 100 k $\Omega$  R14 to the 1 k $\Omega$  R15 sets the gain of the op amp at 100. The output of the op amp, pin 6, is coupled to the input of the ADC, pin 2.

The ADC's pin 1, 2, 3 and 4 are connected to vertical rows 20, 21, 22 and 23, respectively, of the lower portion of the breadboard. Vertical rows 20, 21, 22 and 23 of the upper portion are connected to pins 8, 7, 6 and 5, respectively. Pin 1 and pin 8 are connected to X the V<sub>CC</sub> line "Analog V<sub>CC</sub>." Pin 3 and pin 4 are connected to Y the GND line. I/O Clock, Data Out, and Chip Select will be connected from the microcontroller to complete the ADC connections.

The RESET circuit from the black RESET push-button switch is connected as follows: One end of resistor R16A (47 k $\Omega$ ) is connected to vertical row 17 of the upper portion of the breadboard, and the other end is connected to vertical row 17 of the lower portion. One end of R16B (22 k $\Omega$ ) is also connected to vertical row 17, lower portion. The other end of R16B is connected to vertical row 13, lower portion. Again, short wires are soldered to the terminals of the black RESET push button to make it easy to connect them to the breadboard. Insert one terminal wire into vertical row 13, lower portion and the other end into the bottom horizontal row GND line Y. A RST/NMI wire from the microcontroller will connect to vertical row 13, lower portion, to input the RESET signal to the microcontroller when the black button is pushed. To assure

the RESET signal input is clear of noise, capacitor C3 is added from vertical row 13, lower portion to END at line Y.

### Completing the System Connections

The system power connections come from the J1 connector on the evaluation board.  $V_{CC}$  is connected to the display board by inserting the OR/BLK wire from pin 2 of J1, shown in *Figure 10-12*, to the  $V_{CC}$  line X of the display board. GND is connected by inserting the OR/BLK wire from pin 4 of J1 into the Y GND line of the analog board. A GRN/BLK wire is connected from the Y GND line connections of the analog board to the Y GND line connections of the display board to complete the system GND.

Return to *Figure 10-12* and note that most of the remaining wires from J1 and J2 are either yellow or green wires. The green wires will be connected to the upper portion of the display board, and the yellow wires to the lower portion of the display board.

### The Display Board

The green wires from J1 are connected first:

1. Pin 3 (Cathode AM/PM) is connected to pin 24 (vertical row 1) of the LED display.
2. Pin 11 (Anode a) is connected to vertical row 19, upper portion, one end of R1.
3. Pin 12 (Anode b) is connected to vertical row 17, upper portion, one end of R2.
4. Pin 13 (Anode c) is connected to vertical row 16, upper portion, one end of R3.

The green wires from J2 are connected next (also to upper portion):

1. Pin 16 (Anode f) is connected to vertical row 18, one end of R6.
2. Pin 17 (Anode g) is connected to vertical row 15, one end of R7.
3. Pin 20 (Cathode colon) is connected to vertical row 8, pin 17 of display.

The yellow wires from J1 are connected next (they all go to the lower portion of the breadboard):

1. Pin 8 (Cathode Dig1) is connected to vertical row 2, pin 2 of display.
2. Pin 9 (Cathode Dig2) is connected to vertical row 5, pin 5 of display.
3. Pin 10 (Cathode Dig3) is connected to vertical row 8, pin 8 of display.
4. Pin 14 (Anode d) is connected to vertical row 16, one end of R4.

The yellow wires from J2 are connected next (also to lower portion):

1. Pin 15 (Anode e) is connected to vertical row 19, one end of R5.
2. Pin 19 (Cathode Dig4) is connected to vertical row 10, pin 10 of display.
3. Pin 21 (Anode UC) is connected to vertical row 18, one end of R8.
4. Pin 22 (Anode LC) is connected to vertical row 17, one end of R9.
5. Pin 23 (Anode PM) is connected to vertical row 15, one end of R10.

The red-wire push-button inputs TD1 and TD0 from J2 are connected next:

1. Pin 27 (TD1) is connected to vertical row 20, one end of R12.
2. Pin 28 (TD0) is connected to vertical row 23, one end of R11.

All connections to the display board should be complete.

## The Analog Board


The connections to the analog board start with connecting a RD/BLK wire from vertical row 17, upper portion, one end of R16A, to the  $V_{CC}$  line on the display board; and an orange wire (Analog  $V_{CC}$ ) from pin 25 of J2 to the “Analog  $V_{CC}$ ” line.

The remaining orange lines from J2 to the upper portion are connected next:

1. Pin 26 (I/O Clock) is connected to vertical row 21, pin 7 of TLV1549.
2. Pin 24 (Chip Select) is connected to vertical row 23, pin 5 of TLV1549.
3. Pin 18 (Data Out) is connected to vertical row 22, pin 6 of TLV1549.
4. One remaining wire—a RD/BLK wire from pin 7 of J1 (RST/NMI)—is connected to vertical row 13, lower portion to input the RESET push-button signal to the microcontroller. This completes the connections to the analog board.

## Breadboard Construction Completion

The breadboard construction is essentially complete; however, several items need clarification. First is the connection of the watch crystal. The connections to the watch crystal,  $X_{OUT}$  and  $X_{IN}$ , are made on the evaluation board, as shown in *Figure 10-15*, rather than with wires from pin 5 and 6 of J1. The connections for the crystal on the evaluation board PCB are connected to pin 5 and pin 6 of J1. Carefully (the wires are very delicate) insert the wires into the holes in the evaluation board PCB, as shown in *Figure 10-15a*, and solder the wires to the PCB; then solder the case of the crystal to the PCB pad provided. Before soldering to the pad, tin the case of the crystal with a small dab of solder. Do this quickly so the crystal will not overheat.

 

**Figure 10-15: Evaluation board connections for watch crystal and battery clip for stand-alone breadboard**

Second, when the breadboard is to stand alone—disconnected from the PC—+3V power is provided by two AA batteries. The batteries are connected in series in a battery clip which is wired through shorting jumpers to  $V_{CC}$  and GND on the evaluation board as shown in *Figure 10-15b*. This power connection is normally used only when the JTAG connector from the development system is disconnected from the evaluation board. Shorting jumpers are used so that the batteries can be disconnected if the application is not being used. However, some computer power supplies cannot handle the load, especially when the red and black buttons are pushed. In these cases, connect the battery.

## The Application Program

With the construction of the breadboard complete, the application program—a listing of the program in C language is included in the Appendix—must be loaded into the microcontroller. The most recent version is contained online; it may vary from what is printed in the Appendix. The development system is used for this purpose, and the connections for the system are shown in *Figure 10-9*. The first step is to load the software that comes with the development system, MSP-FET430P120.

### Installing the Development System Software

Following are the steps to install the development system software:

1. Insert the CD-ROM that is contained in the MSP-430P120 development system in the CD-ROM drive of a computer. It should start automatically. If it does not, use a browser to open a file “index.htm” that is located in the root directory of the CD-ROM. The MSP430 start page will be displayed.
2. Click on “Tool Software.”
3. Select the MSP430P120 Flash Evaluation Tool.
4. Click “Save” to download the file “FET\_RXXX.exe”. The file gets updated as time progresses.
5. A “Save As” window appears. Select a directory path to store the download. For example: C:/My Computer/MSP430 Rel X.X (D:). Click “Save.” Note: *The hard drive in this directory path is identified with the letter C. If another letter is used for the hard drive designation, substitute that letter in the directory path.*
6. Use Windows Explorer to follow the directory path to the window that contains and displays “FET\_RXXX.exe”. Click on it to execute the program.
7. The IAR Embedded Workbench window appears which has a welcome message to IAR Systems Product Setup. IAR Systems are the developers of the software.
8. Follow the prompts to install the FET software. The IAR Systems software licensing agreement must be accepted.
9. Turn off computer and reboot.
10. There should be an icon on your desktop that says “IAR Embedded Workbench.”

### Downloading the Application Software

The software program for the application can be downloaded from the Internet as follows. It is a file programmed in C:

1. Go to <http://www.ti.com/MSP430university>.
2. Click on “MSP430 Textbooks.”
3. Click on *Analog and Digital Circuits for Control System Applications: Using the TI MSP430 Microcontroller* by Jerry Luecke. A web page for the book appears.
4. Select “TimeDateTemp Application” and a window opens that has “Save” or “Cancel” across the bottom. Click on “Save.”
5. Choose a directory path to store the download. For example: C:/My Documents/MSP430Applications.
6. The file is a Zip file that contains the application program written in the C language. Name the file “TimeDateTemp.zip.”
7. Click on “Save.”



## **Unzipping the Application Software**

1. Open Windows Explorer.
2. Navigate through the directory C:/MyDocuments/MSP430Applications to the MSP430Applications folder.
3. Select “Time,Date,Temp.zip.”
4. Double clicking on “Time,Date,Temp.zip” will unzip the file if a WinZip program is installed on the computer used. If no WinZip program is installed, go to [www.winzip.com](http://www.winzip.com) on the Web and download the software to unzip the file.
5. In the WinZip window go to “Extract.”
6. Select “all files” and extract to the “MSP430Applications” folder at C:/MyDocuments/MSP430Applications.
7. In the “MSP430 Applications” folder there will be the “Time,Date,Temp.c” file and a “Readme.txt” file. The “Readme.txt” file will have the latest information on revisions or changes.

## **Loading Application Program in Microcontroller**

Follow these steps to load the application program (TimeDateTemp.c) into the microcontroller: (Note: These instructions are based on the latest version of the IAR Workbench at the time of publication. Variations may occur in these instructions as the software is updated. See the “Readme.txt” for the latest information.)

## **Creating a Project in IAR Workbench©**

1. On the PC desktop, click the IAR Embedded Workbench icon. A IAR Systems window appears.
2. Click File menu and then “New.”
3. In the “New” window highlight “Workspace” and click “OK.”
4. Choose directory C:/My Documents/430Applications and click “Open.”
5. Enter TimeDateTemp.eww in the file window and click “Save.”
6. A TimeDateTemp workspace window appears on the IAR workbench.
7. Click Project menu and then “Create New Project.”
8. Choose directory C:/My Documents/430Applications and click “Open.”
9. Enter TimeDateTemp.ewp in the file window and click “Create.”
10. TimeDateTemp will appear in your workspace window.
11. Click on “TimeDateTemp \_ Debug” in the workspace window then click the Project menu and then click “Add Files.”
12. Choose directory C:/My Documents/430Applications and click “Open.”
13. Select “TimeDateTemp.c” that you unzipped and click “Open.”
14. “TimeDateTemp.c” will appear in the workspace window under the TimeDateTemp Project.
15. Click on “TimeDateTemp \_ Debug” in the workspace window once again, then click the Project menu and now click “Options.”
16. An “Options for node - TimeDateTemp \_ Debug” window appears. Highlight the “General” category, then select msp430F1232 in the Target, Device box.
17. Click “OK” to set the options for the project.
18. Click on “TimeDateTemp \_ Debug” in the workspace window once again, then click the Project menu and click “Options” again.



19. Highlight the “C-Spy” category, then select “Flash Emulation Tool” in the driver box and click on “OK” to set the options for the project.

### **Compiling the Program**

20. Select Project menu and highlight “Build All.” Click on it. The “Rebuild All” command executes compiling the C code file into assembly-language and links it with the specific MSP430 descriptor files which were defined by the project options.
21. A message window appears that gives the status of the programming. If it is successful, here is an example of a window that appears:

Messages

Rebuilding configuration: TimeDateTemp - Debug

0 file(s) deleted.

TimeDateTemp.c

```
icc430.exe -I C:\Program Files\IAR Systems\Embedded Workbench
3.2\430\INC\ -I C:\Program Files\IAR Systems\Embedded Workbench
3.2\430\INC\CLIB\ -o C:\
Documents and Settings\A0193378\My Documents\430Applications\Debug\Obj\
-z2 --no_cse --no_unroll --no_inline --no_code_motion --debug -e
--double=32 C:\
Documents and Settings\A0193378\My
Documents\430Applications\TimeDateTemp.c
```

```
IAR MSP430 C Compiler V2.21A/W32 [Kickstart]
Copyright 1996-2003 IAR Systems. All rights reserved.
```

```
3 258 bytes of CODE memory
116 bytes of CONST memory
168 bytes of DATA memory (+ 19 bytes shared)
```

Errors: none

Warnings: none

Linking

```
xlink.exe C:\Documents and Settings\A0193378\My
Documents\430Applications\Debug\Obj\TimeDateTemp.r43 -o C:\Documents and
Settings\A0193378\My
Documents\430Applications\Debug\Exe\TimeDateTemp.d43 -rt -IC:\Program
Files\IAR Systems\Embedded Workbench 3.2\430\LIB\ -f C:\Program
Files\IAR Systems\
Embedded Workbench 3.2\430\config\lnk430F123.xcl C:\Program Files\IAR
Systems\Embedded Workbench 3.2\430\lib\cl430f.r43
-e_small_write=_formatted_write
-e_medium_read=_formatted_read -f C:\Program Files\IAR Systems\Embedded
Workbench 3.2\430\config\compactmath.xcl
```

```
IAR Universal Linker V4.56D/386
Copyright 1987-2003 IAR Systems. All rights reserved.
```

```
3 412 bytes of CODE memory
```

```
248 bytes of DATA memory (+ 19 absolute )
144 bytes of CONST memory
```

```
Errors: none
Warnings: none
```

```
Total number of errors: 0
Total number of warnings: 0
```

### Loading the Program

22. Select the Project menu, then click on “Debug.” The program will be loaded through the JTAG connector onto the MSP430, and the Debugging interface will be shown.
23. Click “Debug,” then “Go” and the program will begin to run on your breadboard.

The system comes up in the **Clock** state at 12:00. It can be set to the present hour and minutes by pushing the black button and adjusting the quantity with the red button. Pressing the black button after adjustments are finished returns to the **Clock** state. Pushing the red button toggles to the next state. Then the date and the year can be set in the same manner. Calibration can then occur for the temperature. Refer to the manual-toggling state diagram shown in *Figure 10-3* for guidance. Sometimes pushing the buttons causes current surges that take the system out of its sequence or shuts it down. If this persists, connect the battery shown in *Figure 10-15*.

### Troubleshooting

If the breadboard does not function, look first at the construction. Most problems will occur because of a wrong connection or a connection that is not electrically sound—shorts, opens, broken wires, intermittent connections. One of the first considerations is that the MSP430 microcontroller is not securely in its socket. Check it carefully. It may require a magnifying glass to see it clearly. The second consideration is the interconnection of the wires. Be sure they are inserted properly and are making correct connection. It is less likely that the software is to blame, especially if the loading sequence has been followed and the windows and clicking followed religiously. The software has been and will be continually checked by the users to verify its authenticity. It may change but any changes should be in the “Readme.txt” file. However, if after following Steps 20 through 23, a “Failed to get target information” message is received, it indicates that the communication to the device has failed. Do the following procedure after checking again the wiring connections and the socket connections.

1. Disconnect the J-TAG connector to the evaluator board.
2. Disconnect the battery if connected.
3. Short out the two power connections, “V<sub>CC</sub>” and “GND.” This discharges all capacitors and resets the microcontroller.
4. Reconnect the J-TAG connector and the battery, and redo Steps 1 through 23.

### The Stand-Alone Breadboard

To make the breadboard stand alone, the separate battery supply shown in *Figure 10-15b* is added. Connect the shorting jumpers to the GND terminals and the V<sub>CC</sub> terminal on the evaluation module. Disconnect the JTAG connector from the evaluation module *before* connecting the shorting jumpers. Disconnecting the JTAG connector removes the V<sub>CC</sub> power that has been supplied by the PC. The program remains stored in the microcontroller and will not be destroyed while the stand-alone V<sub>CC</sub> and GND are established.

To return to the JTAG connection and supplying power from the PC, remove the shorting jumpers from the AA batteries to the V<sub>CC</sub> and GND terminals on the evaluation module. Reconnect the JTAG connector.

 


Figure 10-16: PCB layout and interconnections

## The PCB Circuit

For those readers that prefer to have a very compact, portable unit, the layers for a printed circuit layout are shown in *Figure 10-16*. There is a different parts list for the PCB because the circuit is laid out for surface-mount components. For example, the package notations change for the ICs to identify them for surface mounting. And recall that a different power supply for  $V_{CC}$  is added, so there are additional components. The same MSP430 Development System, MSP-FET430P120, is needed. Here is the parts list:


| Part                                   | Part No.             | Quantity |
|----------------------------------------|----------------------|----------|
| <b>Available from www.ti.com:</b>      |                      |          |
| Microcontroller                        | MSP430F1232PW        | 1        |
| ADC Data converter (A – D)             | TLV1549CD            | 1        |
| Op Amp                                 | TLV2451CDBVT         | 1        |
| LDO (Voltage Regulator)                | TPS71533DCKR         | 1        |
| <b>Available from www.omega.com:</b>   |                      |          |
| Sensor (PT-100 RTD)                    | 1PT100KN815          | 1        |
| <b>Available from www.digikey.com:</b> |                      |          |
| 4-digit LED Display                    | LN543RKN8            | 1        |
| 32 kHz watch crystal                   | X802-ND              | 1        |
| 14-pin JTAG connector                  | H2902-ND             | 1        |
| Push buttons                           | 401-1096-2-ND        | 3        |
| Jumper                                 | 99911-21011000000-ND | 1        |
| 3-cell AAA battery holder              | 2479K-ND             | 1        |
| C1, C3 0.1uF capacitor                 | C1206C104J5RACTU     | 2        |
| C2 0.47uF capacitor                    | ECJ-3VB1C474K        | 1        |
| R1 – R10 33-Ω resistor                 | 9C12063A33R0FKHFT    | 10       |
| R11, R12 470 KΩ resistor               | 9C12063A4703FKHFT    | 2        |
| R13 15KΩ resistor                      | 9C12063A1502FKHFT    | 1        |
| R14 100KΩ resistor                     | 9C12063A1003FKHF     | 1        |
| R15 1KΩ resistor                       | 9C12063A1001FKHFT    | 1        |
| R16 68KΩ resistor                      | 9C12063A6802FKHFT    | 1        |
| <b>Any Local Supply</b>                |                      |          |
| AAA battery                            |                      | 3        |

The parts may be obtained from the sources listed, or any other electronic parts distributor, and, especially, one that handles surface-mount components.


Refer back to the schematic, *Figure 10-4*, and note, again, that there are part changes and additions for the PCB circuit. The first is the op amp package. It is changed to a 5-pin surface-mount package TLV2451CDBVT. The pin connections are shown on *Figure 10-4*. The second is the addition of an LDO voltage regulator, TPS71533, so that the circuit has an extended battery life by operating from three AAA batteries. The regulator supplies +3.3V. In addition to the regulator, three capacitors— $C_1$  (0.1  $\mu\text{F}$ ),  $C_2$  (0.47  $\mu\text{F}$ ) and  $C_3$  (0.1  $\mu\text{F}$ ) are added to the circuit.

One must have dexterity, patience, and skill to mount the components on the PCB. Search out a person who has experience with such surface-mount circuits to help in the construction. When completed, it results in a neat, self-contained unit that resides easily on the desk, in a briefcase, or on a shelf. *Figure 10-17a* is a photograph of a completed breadboard, and *Figure 10-17b* is the PCB circuit.

An additional word on programming the microcontroller when it is on the PCB. Make sure the power jumper shown on the *Figure 10-4* schematic that is in the LDO circuit block is disconnected while the microcontroller is being programmed. Let the PC power the circuit until the programming is complete, then reconnect the power jumper so the circuit can be powered from the AAA batteries through the LDO.

 

a. Breadboard circuit

 

b. PCB circuit

**Figure 10-17: System in breadboard and PCB form**  
TEAM LRN

## Summary

This completes the discussion of the functions and the electronic circuits that make up a system that inputs analog signals, converts them to digital, manipulates them digitally, converts them back from digital to analog and outputs them to productive tasks in the human world. Providing understanding and learning has been the major goal; it is hoped that this goal has been achieved.

## Chapter 10 Quiz

1. The application that is implemented in this chapter:
  - a. really doesn't do anything but provide exercises in programming.
  - b. can't be built. It is just a paper exercise.
  - c. requires no hardware, just software.
  - d. displays the time, date, year and temperature in °F and °C in sequence.
2. For the application, a diagram that shows the sequence of what is displayed is called:
  - a. a state diagram.
  - b. a schematic.
  - c. a logic diagram.
  - d. a memory map.
3. In the application, the three modes of operation are:
  - a. the running mode, the setting mode, and quiet mode.
  - b. auto toggling, manual toggling and sleep modes.
  - c. the ON, OFF and toggling modes.
  - d. the logic, the arithmetic and the memory modes.
4. When the system is in the sleep mode:
  - a. everything in the system is inactive.
  - b. all circuits are active except the display.
  - c. the crystal oscillator and Timer\_A are the only circuits active.
  - d. the microcontroller is fully active.
5. When in the sleep mode, a signal awakens the system:
  - a. every 10-minute point in the hour.
  - b. at the 20-minute, 40-minute and 60-minute point in the hour.
  - c. every half hour.
  - d. every hour.
6. What segments of the 7-segment LED display need to be energized to make the number 9?
  - a. a, b, d, f and g.
  - b. b, c, d, e and g.
  - c. a, b, c, f and g.
  - d. a, b, e, f and g.
7. Of the 24 pins on the 7-segment display, which ones are not used in the chapter application?
  - a. 4, 9, 13, 14, 16, 21 and 23.
  - b. 9, 12, 13, 14, 16, 21 and 23.
  - c. 12, 13, 14, 16, 21, 23 and 24.
  - d. 4, 9, 12, 13, 14, 16, 21 and 23.

8. On the schematic of *Figure 10-4*, what are the three push button switches used for?
  - a. Red turns on power, black turns on power, and black resets the system.
  - b. Red starts the microcontroller and black shuts it down.
  - c. Red is for toggling, black is for changing modes, and black is for reset.
  - d. Red selects the I/O, black selects the frequency of the clock, and black resets the system.
9. Which control register configures the Port 3 I/O pins as outputs?
  - a. P3DIR.
  - b. P3SEL.
  - c. P3IN.
  - d. P3OUT.
10. Which control register configures the Port 2 I/O pins as inputs?
  - a. P2SEL.
  - b. P2DIR.
  - c. P2IN.
  - d. P2OUT.
11. Which MSP430F1232 pin is configured as an output to provide the chip select –CS, to the TLV1549 ADC?
  - a. P1.4.
  - b. P2.6.
  - c. P2.7.
  - d. P1.3.
12. Which MSP430F1232 pin is configured as an input to receive the output data from the TLV1549 ADC?
  - a. P2.6.
  - b. P2.7.
  - c. P3.7.
  - d. P1.4.
13. MSP430F1232 pin 1.4 is configured as an output to supply  $V_{CC}$  to the analog circuits so that:
  - a. the  $V_{CC}$  supplies are isolated.
  - b. the system will consume very little power in the sleep mode.
  - c. the  $V_{CC}$  to the analog circuits can be bypassed.
  - d. noise is reduced on the analog  $V_{CC}$  line.
14. The breadboard system is made up of:
  - a. the display board, the JTAG connector and a PC.
  - b. the evaluation board and a PC.
  - c. the evaluation board, the display board and the analog board.
  - d. the analog board and the evaluation board.
15. In the breadboard system, the connector used to connect the system to a PC is:
  - a. the MSP430F1232 socket.
  - b. the LED display socket.
  - c. the JTAG connector.
  - d. the battery connector.
16. What are the three stages of developing the MSP430F1232 system?
  - a. Breadboard powered by a PC, stand-alone breadboard powered by batteries, a PCB circuit powered by batteries.

- b. Evaluation board powered by batteries, an analog  $V_{CC}$  breadboard, and a PCB circuit powered by batteries.
  - c. a stand-alone breadboard powered from a PC, a JTAG breadboard, and a PCB circuit powered by batteries.
  - d. a stand-alone breadboard powered by batteries, and two PCB circuits powered by batteries.
17. The analog board contains:
- a. the display, the sensor, and the ADC.
  - b. the sensor, the signal-conditioning amplifier and the ADC.
  - c. the signal conditioning amplifier and the display.
  - d. Only the sensor and the display.
18. The display board contains:
- a. the display and the resistors to energize the LED anodes.
  - b. the sensor, the signal-conditioning amplifier and the ADC.
  - c. the resistors to set the gain of the signal-conditioning amplifier.
  - d. none of the above.
19. The stand-alone breadboard:
- a. operates by itself on battery power.
  - b. is made up of a display board, an evaluation board, and an analog board.
  - c. operates stand alone after being programmed from a PC.
  - d. all of the above.
  - e. only a above.
20. The PCB system:
- a. is a complete system assembled on a printed-circuit board.
  - b. must be programmed by a PC after assembly on a PCB.
  - c. must operate from a PC at all times.
  - d. only c above.
  - e. only a and b above.
  - f. none of the above.

Answers: 1.d, 2.a, 3.b, 4.c, 5.b, 6.c, 7.d, 8.c, 9.a, 10.b, 11.d, 12.c, 13.b, 14.c, 15.c, 16.a, 17.b, 18.a, 19.d, 20.e.